



Behzad Razavi

# The Active Inductor

The active inductor is an inductor-less circuit whose impedance rises with frequency across some frequency range. Occupying much less area than a passive inductor and offering tunability, such a circuit proves useful in broadening the bandwidth or realizing other functions that require an inductive element.

As an example of early active inductors, we refer to a 1964 patent by Christensen [1], in which he proposes the circuit shown in Figure 1, where the capacitor at the collector of the transistor drops the gain at high frequencies, weakening the Miller effect of the feedback resistor and hence raising the input impedance. In this article, we study various implementations of active inductors.

## Basic Active Inductors

Consider the negative-feedback system shown in Figure 2(a), where the feedback network,  $K$ , returns a current to the input. We recognize that

Digital Object Identifier 10.1109/MSSC.2020.2987500  
Date of current version: 24 June 2020

feedback lowers the input impedance from  $Z_1$  to

$$Z_{in} = \frac{Z_1}{1 + KH(s)}. \quad (1)$$

Thus, if  $H(s)$  falls as the frequency increases, we expect  $Z_{in}$  to rise. While appealing, this intuition is not accurate because  $H(s)$  takes on a complex value and does not simply fall. Nevertheless, we proceed with this view for now and conclude that a low-pass  $H(s)$  or, more generally, a low-pass  $KH(s)$  yields an inductive input impedance. Note that the output of  $H(s)$  can be a voltage quantity or a current quantity.

Let us implement the topology of Figure 2(a) at the circuit level. As depicted in Figure 2(b), we can realize  $H(s)$  simply by a first-order low-pass filter and  $K$  by a single MOS device. As explained in the following, proper choice of the element values leads to an inductive  $Z_{in}$ .

We should note that the impedance of interest need not appear at the input port of a negative feedback system; the output port is equally qualified. As illustrated in

Figure 2(c), if the feedback network senses the output voltage, then the output impedance drops from  $Z_2$  to

$$Z_{out} = \frac{Z_2}{1 + KH(s)} \quad (2)$$

and behaves inductively for a low-pass  $KH$ . The signal returned by  $K$  to the input can be a voltage or current quantity.

The forward transfer function,  $H(s)$ , in Figure 2(a) can itself be an active circuit. For example, a low-pass function can be formed by means of a transconductance ( $G_m$ ) stage and a capacitor. Depicted in Figure 3, the resulting active inductor exhibits certain superior properties compared

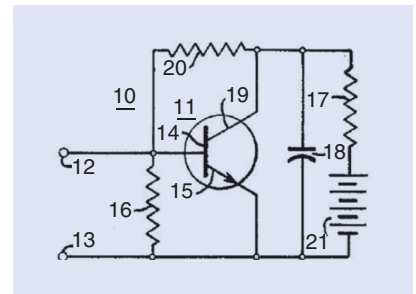


FIGURE 1: The active inductor described by Christensen.

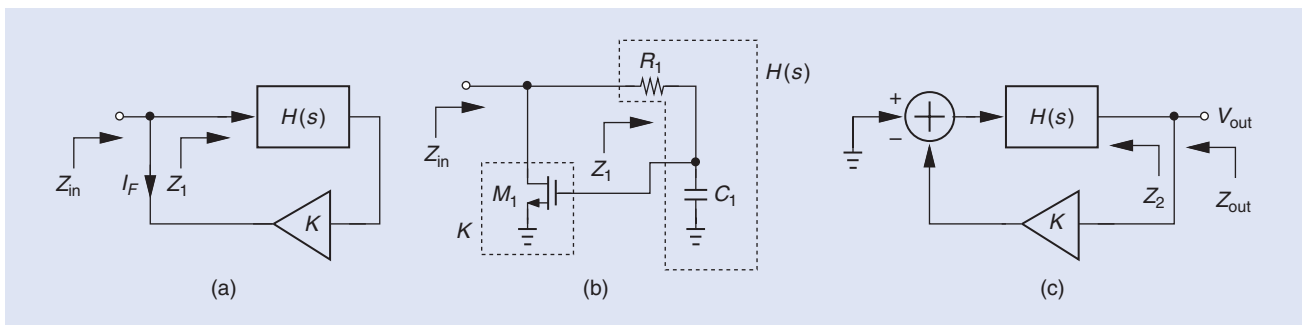


FIGURE 2: A negative-feedback system: its (a) input impedance, (b) circuit implementation, and (c) output impedance.

to that in Figure 2(b). We analyze this topology subsequently, but should remark that  $G_{m1}G_{m2}$  must be negative. Also, the loop consisting of  $G_{m1}$  and  $G_{m2}$  is called a *gyrator*, as it rotates the impedance of  $C_1$  (by 90°), transforming it to inductance.

In the spirit of Christensen's topology, we can construct the circuit shown in Figure 4, where  $C_1$  creates low-pass action at the drain of  $M_1$ . We can also view  $M_1$  as a transconductance stage,  $G_{m1}$ , and  $R_1$  as a "poor man's" approximation of a feedback transconductance stage,

$G_{m2}$ , concluding that the circuit gyrates  $C_1$  to an inductor.

There is yet another perspective for creating active inductance. Let us suppose the feedback in Figure 2(c) is positive and write

$$Z_{out} = \frac{Z_2}{1 - KH(s)}. \quad (3)$$

We surmise that, in this case, a high-pass  $KH(s)$  causes  $Z_{out}$  to rise with frequency. The high-pass  $KH(s)$  also avoids latch-up (which can occur in the presence of positive feedback) by suppressing the loop gain at low frequencies. As illustrated in Figure 5, this topology can be realized by a source follower. Interestingly, here  $H(s)$  is not a high-pass function, but

$K$  is. Of course, if  $M_1, R_1$ , and  $C_1$  are viewed as forming a two-terminal impedance, the two circuits in Figures 2(b) and 5 are equivalent. We reexamine both later in this article.

### Properties of Active Inductors

As our first step toward quantifying the impedance of active inductors, we return to Figure 2(b) and, from the open-loop circuit shown in Figure 6, write

$$Z_1 = R_1 + \frac{1}{C_1 s}, \quad (4)$$

where channel-length modulation is neglected. Also, since the small-signal drain current of  $M_1$  entirely flows through  $C_1$ , the loop gain (loop transmission) is given by

$$KH(s) = -\frac{V_F}{V_t} \quad (5)$$

$$= \frac{g_m}{C_1 s}. \quad (6)$$

It follows from (1) that the closed-loop input impedance is equal to

$$Z_{in} = \frac{R_1 C_1 s + 1}{C_1 s} \quad (7)$$

$$= \frac{R_1 C_1 s + 1}{C_1 s + g_m}. \quad (8)$$

This result agrees with our intuition in Figure 2(b). At low frequencies,  $C_1$  acts as an open circuit and  $M_1$  as a diode-connected device, yielding  $Z_{in} \approx 1/g_m$ . At high frequencies, the gate of  $M_1$  is at ac ground, and  $Z_{in} \approx R_1$ . Sketched in Figure 7,  $|Z_{in}|$  rises with frequency if  $1/g_m < R_1$ , i.e., if the zero of  $Z_{in}$ ,  $\omega_z$ , has a lower magnitude than its pole,  $\omega_p$ . The circuit thus behaves inductively between  $\omega_z$  and  $\omega_p$ .

We wish to formulate the equivalent inductance of this topology. As an approximation, we can find the slope of  $|Z_{in}|$  in Figure 7 between  $\omega_z$  and  $\omega_p$ . But an exact expression is also possible. Since  $Z_{in}$  reduces to  $1/g_m$  at low frequencies and to  $R_1$  at high frequencies, we envision the arrangement shown in Figure 8. Let us first subtract the series element,  $1/g_m$ , from  $Z_{in}$ :

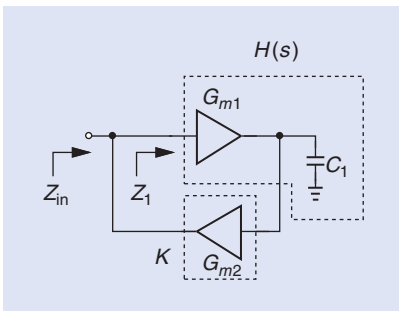


FIGURE 3: An active inductor incorporating a gyrator.

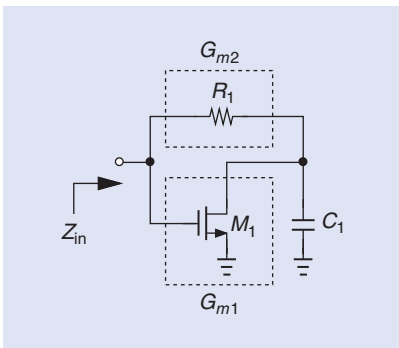


FIGURE 4: A MOS implementation of Christensen's circuit.

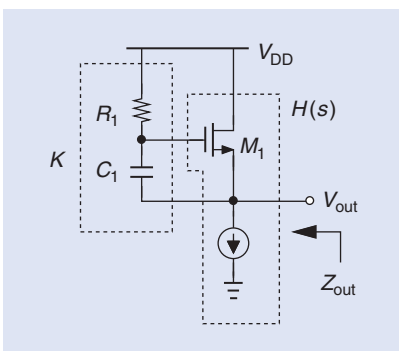


FIGURE 5: A source follower providing an inductive output impedance.

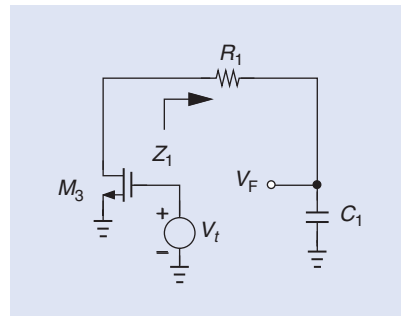


FIGURE 6: The open-loop circuit of an active inductor.

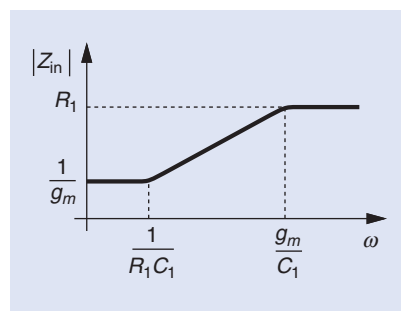


FIGURE 7: The frequency response of an active inductor.

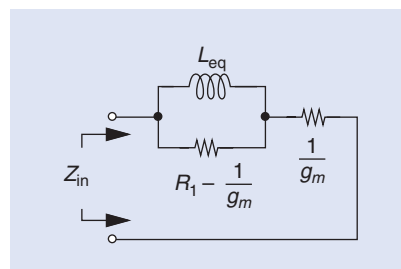


FIGURE 8: The equivalent circuit of an active inductor.

$$Z_{in} - \frac{1}{g_m} = \frac{\left(R_1 - \frac{1}{g_m}\right)C_1 s}{C_1 s + g_m}. \quad (9)$$

Inverting this impedance and decomposing the result into a sum,

$$\left(Z_{in} - \frac{1}{g_m}\right)^{-1} = \frac{1}{\left(R_1 - \frac{1}{g_m}\right)\frac{C_1}{g_m}s} + \frac{1}{R_1 - \frac{1}{g_m}}, \quad (10)$$

we identify two elements in parallel. The first term on the right represents the admittance of an inductor having a value of

$$L_{eq} = \left(R_1 - \frac{1}{g_m}\right)\frac{C_1}{g_m}, \quad (11)$$

and the second term corresponds to the inverse of a resistance equal to  $R_1 - 1/g_m$ , both of which confirm the topology predicted in Figure 8. As expected, we must have  $R_1 > 1/g_m$  to obtain an inductance. In practice, we choose  $R_1 \gg 1/g_m$ , obtaining

$$L_{eq} = \frac{R_1 C_1}{g_m}. \quad (12)$$

The circuits of Figures 4 and 5 follow these results as well. We can thus select  $R_1, C_1$ , and  $g_m$  to obtain a desired inductance, and we can make them programmable so as to tune  $L_{eq}$ .

The two resistive components in Figure 8 imply a finite quality factor ( $Q$ ) for the active inductor. Returning to  $Z_{in}$  in (8), we can define the  $Q$  as the desirable (imaginary) part of  $Z_{in}$  divided by the undesirable (real) part. It follows that

$$Q = \frac{\text{Im}\{Z_{in}\}}{\text{Re}\{Z_{in}\}} \quad (13)$$

$$= \frac{(g_m R_1 - 1)C_1 \omega}{g_m + R_1 C_1^2 \omega^2}. \quad (14)$$

If  $R_1 \gg 1/g_m$ ,

$$Q = \frac{\frac{g_m}{C_1 \omega} R_1 C_1 \omega}{\frac{g_m}{C_1 \omega} + R_1 C_1 \omega} \quad (15)$$

$$= \left(\frac{g_m}{C_1 \omega}\right) \parallel (R_1 C_1 \omega). \quad (16)$$

We note that the first term on the right corresponds to the  $Q$  of  $L_{eq}$  if only the parallel resistance,  $R_1 - 1/g_m \approx R_1$ ,

is considered, and the second term represents the  $Q$  only if the series resistance,  $1/g_m$ , is taken into account. The maximum  $Q$  occurs if  $g_m/(C_1 \omega) = R_1 C_1 \omega$  and is equal to  $g_m/(2C_1 \omega)$ . However, the  $Q$  is also limited by the output resistance of  $M_1$ .

For the gyrator-based circuit of Figure 3, one can readily show that

$$Z_{in} = -\frac{C_1}{G_{m1} G_{m2}} s. \quad (17)$$

(Recall that  $G_{m1} G_{m2}$  must be negative.) The equivalent inductance is therefore equal to  $-C_1/(G_{m1} G_{m2})$  and can be set to relatively large values (e.g., in the microhenry range) by selecting a small  $G_{m1} G_{m2}$  product. Since the  $G_m$  blocks can incorporate multiple stages, this structure can achieve higher inductance values than that in Figure 2(b).

In contrast to the topology of Figure 2(b), the gyrator-based inductor appears to exhibit an infinite  $Q$  as (17) does not contain a real part. But the output resistances of  $G_{m1}$  and  $G_{m2}$  must be considered. Referring to Figure 9, we write  $I_F$  as

$$I_F = -G_{m1} \frac{r_{O1}}{r_{O1} C_1 s + 1} G_{m2} V_X, \quad (18)$$

and hence

$$\frac{V_X}{I_F} = \frac{-C_1}{G_{m1} G_{m2}} s - \frac{1}{G_{m1} G_{m2} r_{O1}}. \quad (19)$$

The equivalent inductor thus suffers from both a series resistance equal to  $-1/(G_{m1} G_{m2} r_{O1})$  and a parallel resistance equal to  $r_{O2}$ .

### Applications and Design Issues

Active inductors have found a multitude of applications in circuit de-

sign. In this section, we study a few and describe their tradeoffs.

In a manner similar to their passive counterparts, active inductors can create shunt peaking, thus widening the bandwidth of amplifiers. Illustrated in Figure 10(a) is an example [2] where  $M_1$  along with  $R_1$  and the gate-source capacitance,  $C_{GS} = C_1$ , acts as an inductance in series with  $R_D$ . This branch exhibits a higher impedance as the frequency increases, partially counteracting the effect of  $C_L$ .

*In a manner similar to their passive counterparts, active inductors can create shunt peaking, thus widening the bandwidth of amplifiers.*

The speed improvement afforded by  $M_1$  is limited by its gate-drain and source-bulk capacitances. We can quantify the effect of the former by redrawing the active inductor as in Figure 10(b), where  $C_2$  denotes the gate-drain capacitance. Opening the feedback loop, noting that the loop gain is still equal to  $g_m/(C_1 s)$ , and finding the overall impedance, we have

$$Z_{in} = \frac{R_1 (C_1 + C_2) s + 1}{C_1 s + g_m} \cdot \frac{1}{R_1 C_2 s + 1}. \quad (20)$$

Compared to (8), this impedance exhibits a lower zero frequency and


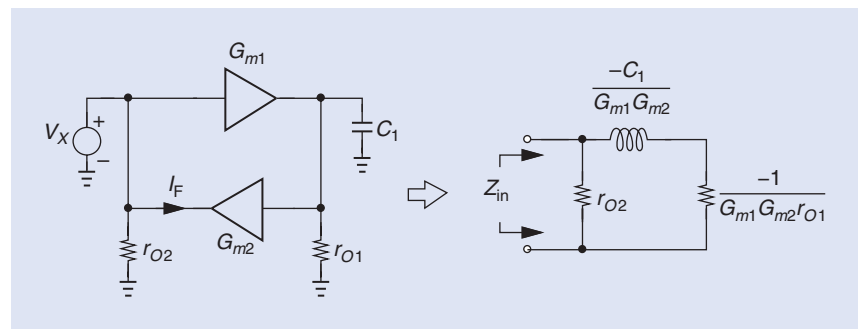


FIGURE 9: A gyrator circuit with finite output impedances.

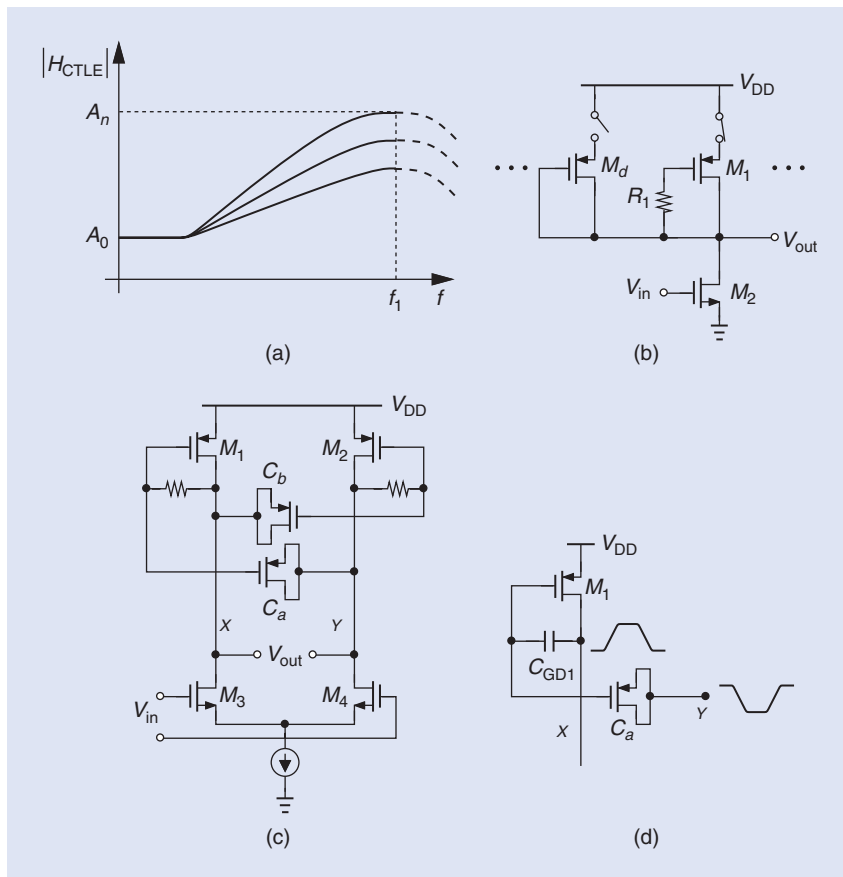



**FIGURE 14:** CTLE application of active inductors: (a) the typical CTLE frequency response, (b) the CTLE implementation using active inductors, (c) cancellation of gate-drain capacitance in a differential topology, and (d) an illustration of the capacitors' role.

example [4] where a differential pair delivers a large voltage swing to a transmission line and the network comprising  $M_1$ - $M_6$  serves as a tunable inductive load. We recognize that  $M_1$  and  $M_2$  play the same role as  $M_1$  in Figure 11 and  $M_5$  and  $M_6$  the same role as  $R_1$ . Moreover, source followers  $M_3$  and  $M_4$  act as level shifters, allowing the gate voltages of  $M_1$  and  $M_2$  to be lower than their respective drain voltages by  $V_{GS3,4}$ . This structure therefore lends itself to low supply voltages. The on-resistance of  $M_5$  and  $M_6$  can be adjusted by means of their gate voltage, thus providing a variable boost factor [4].

Another interesting application of active inductors is in continuous-time linear equalizers (CTLEs) used in wireline receivers. A CTLE must

provide a high-pass response to partially compensate for the high-frequency loss of the channel through which the data travels [Figure 14(a)]. We say the CTLE provides a “boost factor,”  $A_n/A_0$ , and we make it programmable so as to accommodate different channel losses.

We can envision the CTLE as a simple common-source stage and implement the responses in Figure 14(a) by means of a variable load impedance; specifically, since the slope of the load must be programmable, we surmise that a variable inductance can serve this purpose. The tunability afforded by (12) thus proves useful here, leading to the CTLE topology shown in Figure 14(b) [5]. The inductance is tuned by varying the PMOS load's transconductance. This device is decomposed into a number of

units, each of which can participate in the active inductor environment. But, to ensure a constant low-frequency gain,  $A_0$ , when some of these units turn off, additional diode-connected transistors are turned on [5]. This approach must still deal with the voltage headroom consumed by the PMOS transistors.

Recall from Figure 10(c) that the gate-drain capacitance of the core transistor in an active inductor degrades the performance. This issue can be resolved in a differential topology by adding compensating capacitors [Figure 14(c)] [5]. Here,  $C_a$  and  $C_b$  are chosen equal to the PMOS gate-drain capacitances. As illustrated in Figure 14(d), the gate voltage of  $M_1$  is now unaffected by  $C_{GD1}$  because this capacitance and  $C_a$  inject equal and opposite amounts of charge.

Active inductors can also serve in analog filter design. In fact, some classic filters were based on “simulated inductors” [6], circuits that used op-amps and capacitors to emulate an inductive behavior.

## References

- [1] B. Christensen, “Monolithic semiconductor circuit with energy storage junction and feedback to active transistor to produce two terminal inductance,” U.S. Patent 3 160 835, Dec. 8, 1964.
- [2] E. Sackinger and W. Fischer, “A 3 GHz, 32 dB CMOS limiting amplifier for SONET OC-48 receivers,” in *Proc. IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, Feb. 2000, pp. 158–159. doi: 10.1109/ISSCC.2000.839730.
- [3] J. Im et al., “A 112-Gb/s PAM4 long-reach wireline transceiver using a 36-way time-interleaved SAR ADC and inverter-based RX analog front end in 7-nm FinFET,” in *Proc. IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, Feb. 2020, pp. 116–117.
- [4] Y.-S. Lee, S. Sheikhaei, and S. Mirabbasi, “A 10 Gb/s active-inductor structure with peaking control in 90-nm CMOS,” in *Proc. Asian Solid-State Circuits Conf.*, Nov. 2008, pp. 229–232. doi: 10.1109/ASSCC.2008.4708770.
- [5] P. A. Francese et al., “Continuous-time linear equalization with programmable active-peaking transistor arrays in a 14-nm FinFET 2-mW/Gb/s 16-Gb/s 2-tap speculative DFE receiver,” in *Proc. IEEE Int. Solid-State Circuits Conf. (ISSCC) Dig. Tech. Papers*, Feb. 2015, pp. 186–187. doi: 10.1109/ISSCC.2015.7062988.
- [6] A. Sedra and K. Smith, *Microelectronic Circuits*, 5th ed. London, Oxford Univ. Press, 2004.

SSC