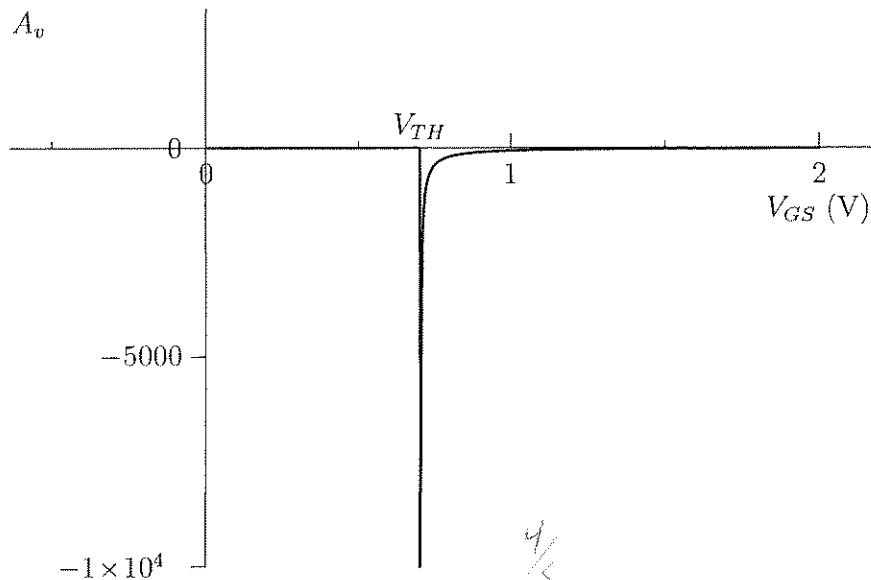


3.6 (a)

$$\begin{aligned}
 A_v &= -g_m r_o \\
 &= -\frac{2I_D}{V_{GS} - V_{TH}} \frac{1}{\lambda I_D} \\
 &= -\frac{2}{\lambda(V_{GS} - V_{TH})}
 \end{aligned}$$

Using the values from Table 2.1 ( $\lambda = 0.1 \text{ V}^{-1}$ ,  $V_{TH} = 0.7 \text{ V}$ ), we get the following plot:




(b)

$$\begin{aligned}
 A_v &= -g_m r_o \\
 &= -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \frac{1}{\lambda I_D} \\
 &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \frac{2}{\lambda \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2} \\
 &= -\frac{2}{\lambda(V_{GS} - V_{TH})}
 \end{aligned}$$


Note this is identical to part (a) since the intrinsic gain does not depend on either  $I_D$  or  $W/L$  (hence keeping one or the other constant makes no difference).

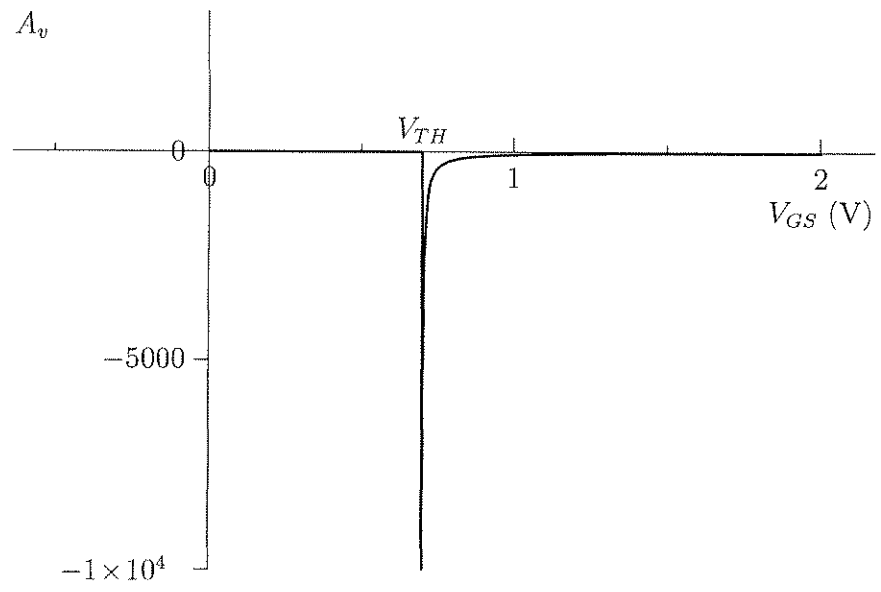Handwritten notes:  $4/5$  and  $v_s$  different  $I_D, \frac{W}{L}?$



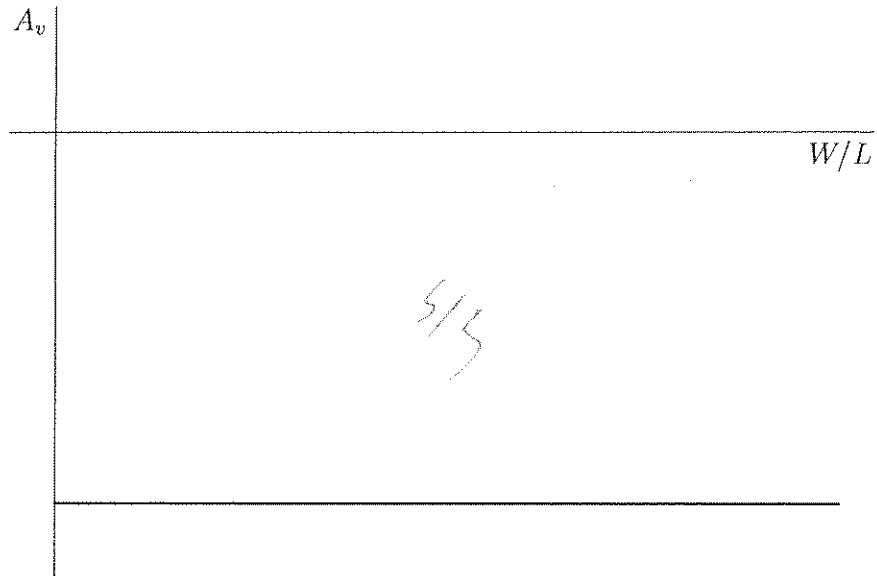
3.7 (a)

$$\begin{aligned}
 A_v &= -g_m r_o \\
 &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \frac{1}{\lambda I_D} \\
 &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \frac{2}{\lambda \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2} \\
 &= -\frac{2}{\lambda (V_{GS} - V_{TH})}
 \end{aligned}$$



(b)
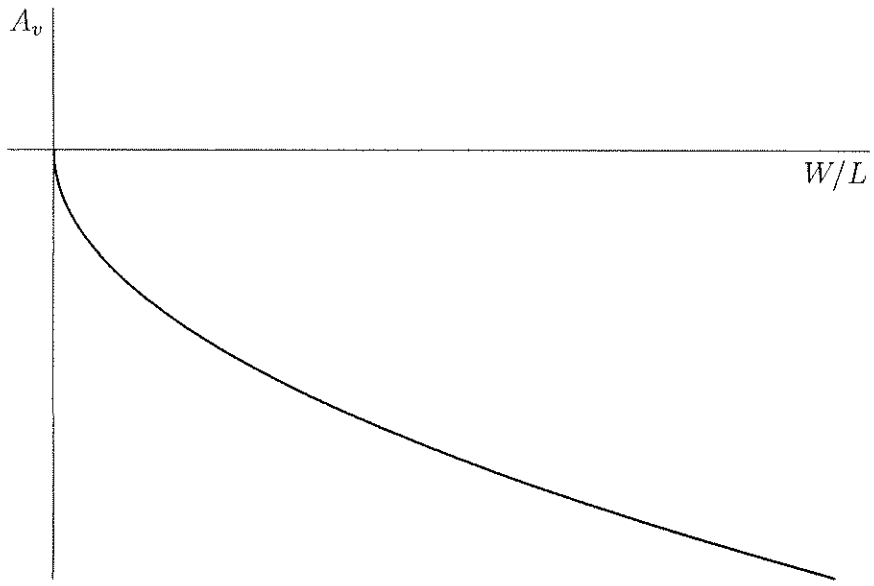
$$\begin{aligned}
 A_v &= -g_m r_o \\
 &= -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \frac{1}{\lambda I_D} \\
 &= -\frac{1}{\lambda} \sqrt{\frac{2\mu_n C_{ox} \frac{W}{L}}{I_D}}
 \end{aligned}$$



4/15


3.9


$$g_m = \mu_n C_{ox} \frac{W}{L} \left[ V_{GS} - V_{TH0} - \gamma \left( \sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F} \right) \right]$$

$$r_o = \frac{1}{\lambda I_D}$$

$$= \frac{2}{\lambda \mu_n C_{ox} \frac{W}{L} \left[ V_{GS} - V_{TH0} - \gamma \left( \sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F} \right) \right]^2}$$
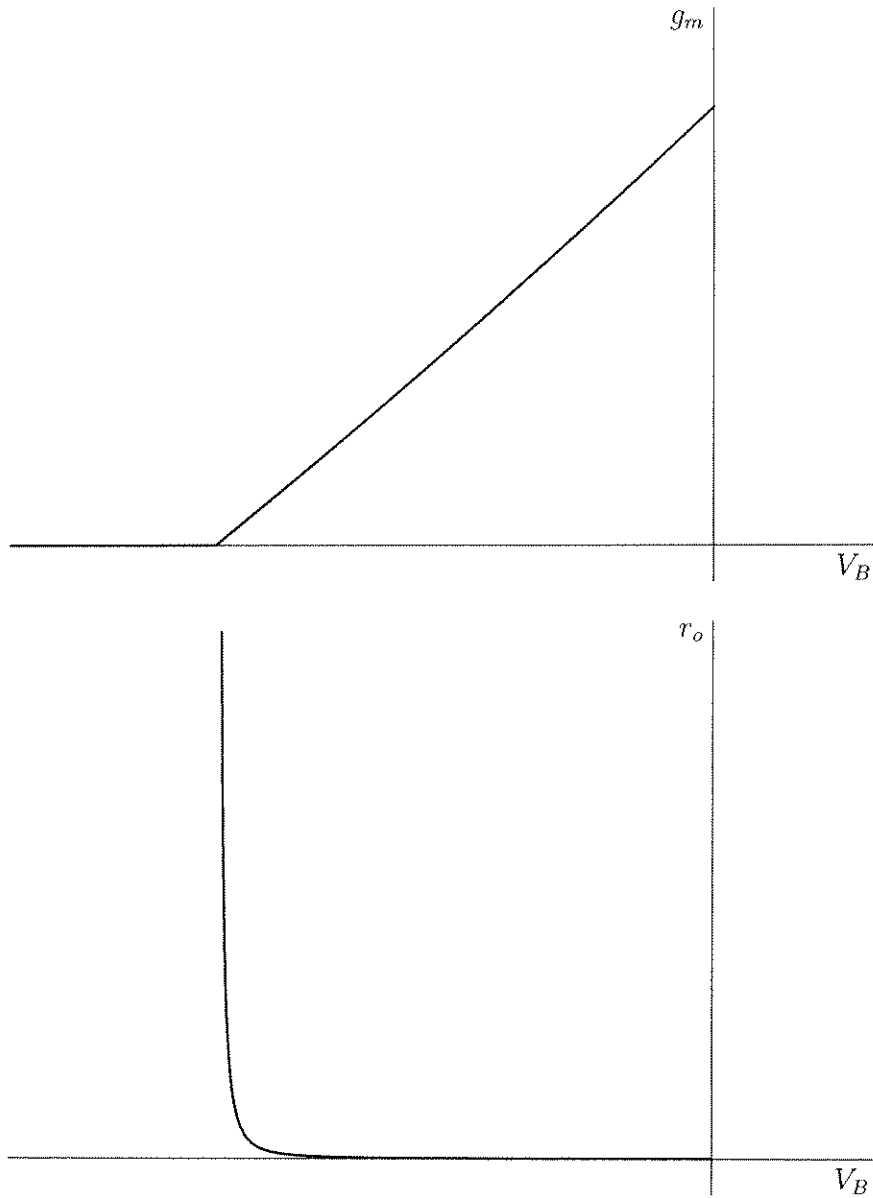
$$g_m r_o = \frac{2}{\lambda \left[ V_{GS} - V_{TH0} - \gamma \left( \sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F} \right) \right]}$$



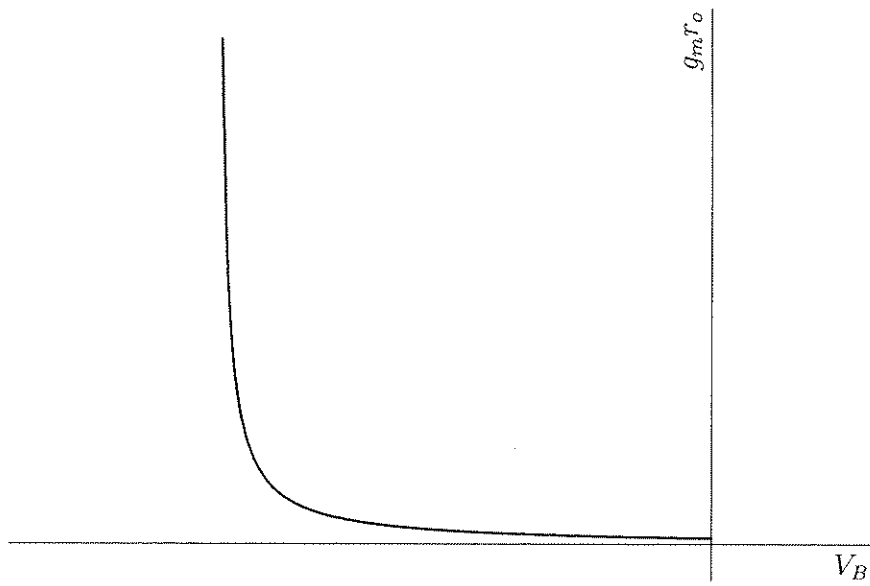

Note that the sudden changes in each graph occur where  $V_{TH}$  increases to the point where  $V_{GS} = V_{TH}$ .

5/5

3.16 (a)

$$V_{out} = V_{DD} - (I_{D1} - I_{D2}) R_D$$

For  $V_{in} < V_{TH1}$ ,  $I_{D1} = I_{D2} = 0$  and  $V_{out} = V_{DD}$ . Once  $V_{in} > V_{TH1}$ ,  $M_1$  enters saturation and  $M_2$  enters triode.

$$V_{out} = V_{DD} - \left\{ \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 - \mu_n C_{ox} \left( \frac{W}{L} \right)_2 \left[ 2(V_{DD} - V_b - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \right\} R_D$$


Once  $V_{out} < V_b + |V_{TH2}|$ ,  $M_2$  enters saturation.

$$V_{out} = V_{DD} - \left\{ \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 - \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_b - |V_{TH2}|)^2 \right\} R_D$$

Finally, once  $V_{out} < V_{in} - V_{TH}$ ,  $M_1$  enters triode.

$$V_{out} = V_{DD} - \left\{ \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 \left[ (V_{in} - V_{TH1})^2 V_{out} - V_{out}^2 \right] - \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_b - |V_{TH2}|)^2 \right\} R_D$$

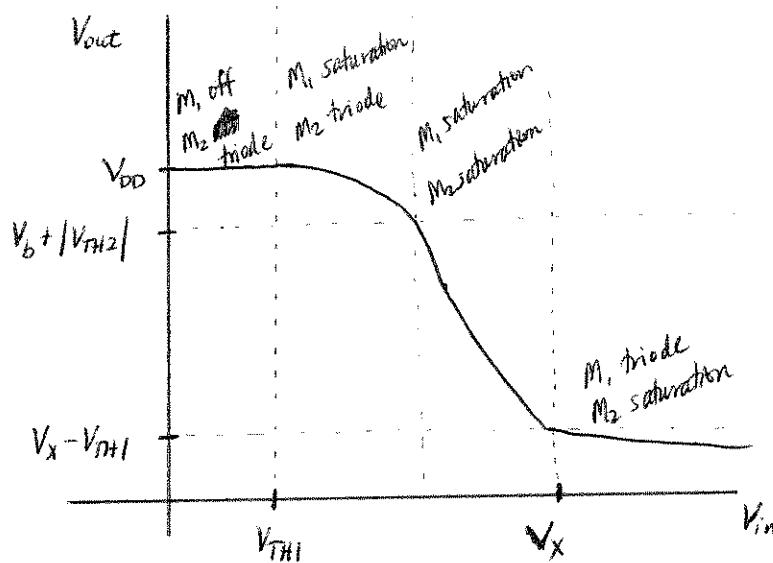Solving these equations analytically is impractical, so below is a qualitatively drawn plot based on the regions of operation of  $M_1$  and  $M_2$ .



S/S

3.18 (c)

$$\begin{aligned}
V_{GS} &= V_b - V_X \\
V_{DS} &= V_{DD} - I_D R_D - V_X \\
V_{GS} &> V_{TH} \\
\Leftrightarrow V_b - V_X &> V_{TH} \\
\Leftrightarrow V_X &< V_b - V_{TH} \\
V_{DS} &> V_{GS} - V_{TH} \\
\Leftrightarrow V_{DD} - I_D R_D &> V_b - V_{TH} \\
\Leftrightarrow V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_X - V_{TH})^2 R_D &> V_b - V_{TH} \\
\Leftrightarrow \sqrt{\frac{2(V_{DD} - V_b + V_{TH})}{\mu_n C_{ox} \frac{W}{L} R_D}} &> V_b - V_X - V_{TH} \\
\Leftrightarrow V_X &> V_b - V_{TH} - \sqrt{\frac{2(V_{DD} - V_b + V_{TH})}{\mu_n C_{ox} \frac{W}{L} R_D}} \\
I_X &= \frac{V_X}{R_S} - I_D
\end{aligned}$$

$$I_D = \begin{cases} 0 & V_X > V_b - V_{TH} \\ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 & V_b - V_{TH} - \sqrt{\frac{2(V_{DD} - V_b + V_{TH})}{\mu_n C_{ox} \frac{W}{L} R_D}} < V_X < V_b - V_{TH} \\ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2] & V_X < V_b - V_{TH} - \sqrt{\frac{2(V_{DD} - V_b + V_{TH})}{\mu_n C_{ox} \frac{W}{L} R_D}} \end{cases}$$


$$I_X = \begin{cases} \frac{V_X}{R_S} & V_X > V_b - V_{TH} \\ \frac{V_X}{R_S} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 & V_b - V_{TH} - \sqrt{\frac{2(V_{DD} - V_b + V_{TH})}{\mu_n C_{ox} \frac{W}{L} R_D}} < V_X < V_b - V_{TH} \\ \frac{V_X}{R_S} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2] & V_X < V_b - V_{TH} - \sqrt{\frac{2(V_{DD} - V_b + V_{TH})}{\mu_n C_{ox} \frac{W}{L} R_D}} \end{cases}$$

When in triode,  $I_X$  depends on  $V_{DS} = V_{DD} - I_D R_D - V_X$ , so we must re-arrange the triode expression to find  $I_X$  explicitly as a function of  $V_X$ .

$$I_{D,tri} = \mu_n C_{ox} \frac{W}{L} \left[ 2(V_{GS} - V_{TH})(V_{DD} - I_{D,tri} R_D - V_X) - (V_{DD} - I_{D,tri} R_D - V_X)^2 \right]$$

Let  $K = \mu_n C_{ox} \frac{W}{L}$ . Using Maxima, we have
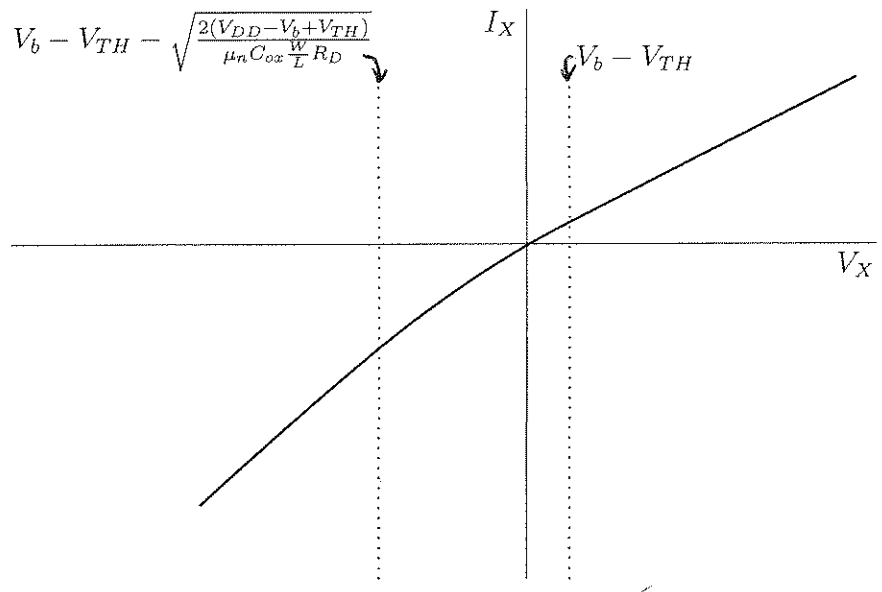
$$\begin{aligned}
I_{D,tri} = & \frac{\sqrt{(K R_D V_X)^2 + (2K^2 R_D^2 V_{TH} - 2K^2 R_D^2 V_b) V_X + K^2 R_D^2 V_{TH}^2 - (2K^2 R_D^2 V_b + 2K R_D) V_{TH} - 2K R_D V_{DD} + K^2 R_D^2 V_b^2 + 2K R_D V_b + 1}}{K R_D^2} + \\
& + \frac{K R_D V_{TH} + K R_D V_{DD} - K R_D V_b - 1}{K R_D^2}
\end{aligned}$$




5/13

3.19 (d)

$$\begin{aligned}
 I_X &= I_{D1} - I_{D2} \\
 V_{GS1} &= V_X \\
 V_{GS1} &< V_{TH1} \\
 \Leftrightarrow V_X &< V_{TH1} \\
 V_{SG2} &= V_{DD} - V_X \\
 V_{SG2} &< |V_{TH2}| \\
 \Leftrightarrow V_X &> V_{DD} - |V_{TH2}| \\
 V_{DS1} &= V_X = V_{GS1} \\
 V_{SD2} &= V_{DD} - V_X = V_{SG2}
 \end{aligned}$$


Since  $V_{DS1} = V_{GS1}$  and  $V_{SD2} = V_{SG2}$ , both  $M_1$  and  $M_2$  are always either in saturation or cutoff.

$$I_X = \begin{cases} -\frac{1}{2}\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG2} - |V_{TH2}|)^2 & V_X < V_{TH1} \\ \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH1})^2 - \frac{1}{2}\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG2} - |V_{TH2}|)^2 & V_{TH1} < V_X < V_{DD} - |V_{TH2}| \\ \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH1})^2 & V_X > V_{DD} - |V_{TH2}| \end{cases}$$

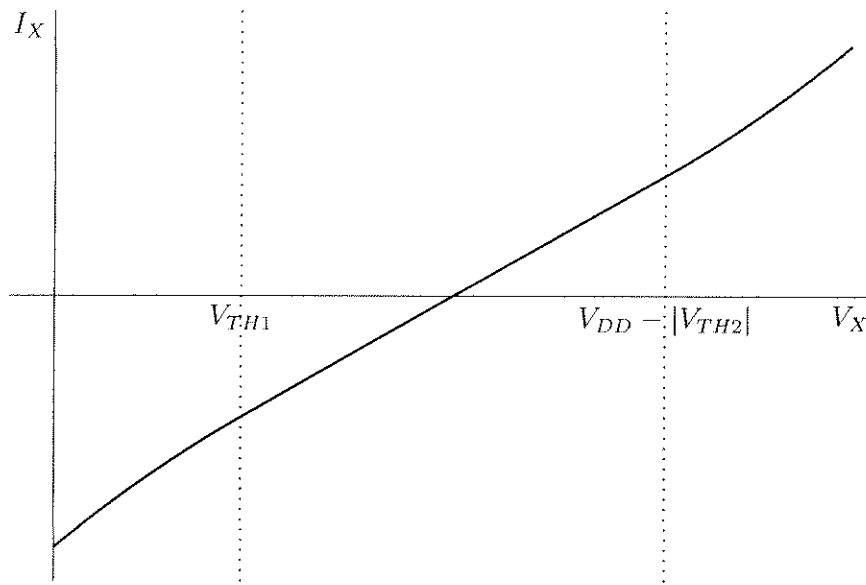

3/15

3.20 (e)

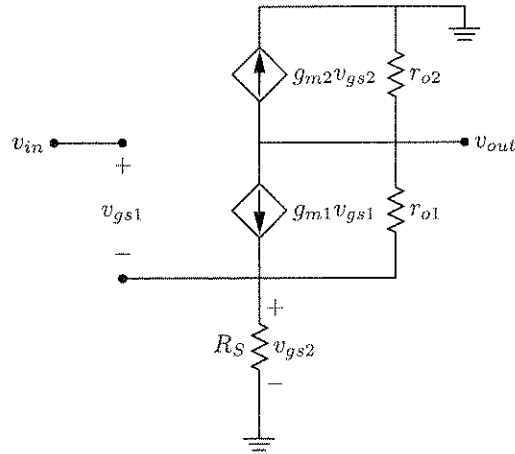


$$\begin{aligned}
 g_{m2}v_{gs2} + \frac{v_{out}}{r_{o2}} + g_{m1}v_{gs1} + \frac{v_{out} - v_{gs2}}{r_{o1}} &= 0 \\
 -g_{m1}v_{gs1} + \frac{v_{gs2} - v_{out}}{r_{o1}} + \frac{v_{gs2}}{R_S} &= 0 \\
 v_{gs2} &= v_{in} - v_{gs1} \\
 g_{m2}(v_{in} - v_{gs1}) + \frac{v_{out}}{r_{o2}} + g_{m1}v_{gs1} + \frac{v_{out} - (v_{in} - v_{gs1})}{r_{o1}} &= 0 \\
 -g_{m1}v_{gs1} + \frac{v_{in} - v_{gs1} - v_{out}}{r_{o1}} + \frac{v_{in} - v_{gs1}}{R_S} &= 0 \\
 v_{gs1} \left( g_{m1} + \frac{1}{r_{o1}} + \frac{1}{R_S} \right) &= \frac{v_{in} - v_{out}}{r_{o1}} + \frac{v_{in}}{R_S} \\
 v_{gs1} &= \left( \frac{v_{in} - v_{out}}{r_{o1}} + \frac{v_{in}}{R_S} \right) \left( \frac{1}{g_{m1}} \parallel r_{o1} \parallel R_S \right) \\
 v_{gs1} \left( g_{m2} - g_{m1} - \frac{1}{r_{o1}} \right) &= g_{m2}v_{in} + \frac{v_{out}}{r_{o2}} + \frac{v_{out} - v_{in}}{r_{o1}} \\
 \left( \frac{v_{in} - v_{out}}{r_{o1}} + \frac{v_{in}}{R_S} \right) \left( \frac{1}{g_{m1}} \parallel r_{o1} \parallel R_S \right) \left( g_{m2} - g_{m1} - \frac{1}{r_{o1}} \right) &= g_{m2}v_{in} + \frac{v_{out}}{r_{o2}} + \frac{v_{out} - v_{in}}{r_{o1}}
 \end{aligned}$$

$$v_{in} \left[ \frac{1}{r_{o1}} - g_{m2} + \left( \frac{1}{r_{o1}} + \frac{1}{R_S} \right) \left( \frac{1}{g_{m1}} \parallel r_{o1} \parallel R_S \right) \left( g_{m2} - g_{m1} - \frac{1}{r_{o1}} \right) \right] = v_{out} \left\{ \frac{1}{r_{o1}} \left[ 1 + \left( \frac{1}{g_{m1}} \parallel r_{o1} \parallel R_S \right) \left( g_{m2} - g_{m1} - \frac{1}{r_{o1}} \right) \right] + \frac{1}{r_{o2}} \right\}$$

$$\frac{v_{out}}{v_{in}} = \frac{\frac{1}{r_{o1}} - g_{m2} + \left( \frac{1}{r_{o1}} + \frac{1}{R_S} \right) \left( \frac{1}{g_{m1}} \parallel r_{o1} \parallel R_S \right) \left( g_{m2} - g_{m1} - \frac{1}{r_{o1}} \right)}{\frac{1}{r_{o1}} \left[ 1 + \left( \frac{1}{g_{m1}} \parallel r_{o1} \parallel R_S \right) \left( g_{m2} - g_{m1} - \frac{1}{r_{o1}} \right) \right] + \frac{1}{r_{o2}}}$$

Σ/3

3.21 (h)

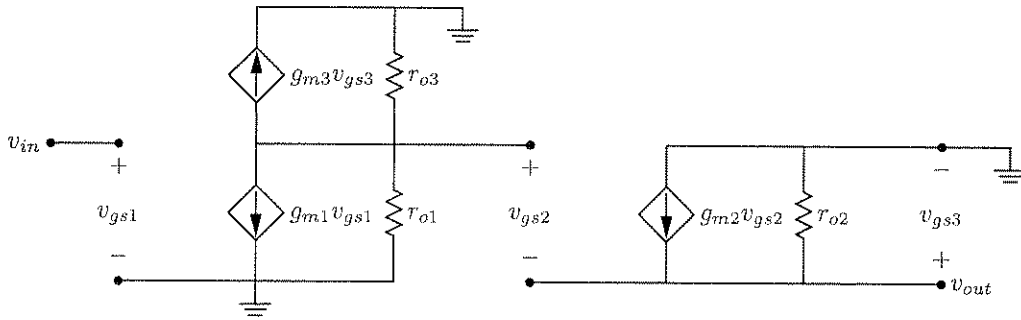

$$v_{gs1} = v_{in}$$

$$v_{gs3} = v_{out} = g_{m2}v_{gs2}r_{o2}$$

$$g_{m3}v_{gs3} + \frac{v_{gs2} + v_{gs3}}{r_{o3}} + \frac{v_{gs2} + v_{gs3}}{r_{o1}} + g_{m1}v_{gs1} = 0$$

$$g_{m3}v_{out} + \frac{v_{gs2} + v_{out}}{r_{o3}} + \frac{v_{gs2} + v_{out}}{r_{o1}} + g_{m1}v_{in} = 0$$

$$v_{gs2} \left( \frac{1}{r_{o1}} + \frac{1}{r_{o3}} \right) = -g_{m1}v_{in} - v_{out} \left( g_{m3} + \frac{1}{r_{o1}} + \frac{1}{r_{o3}} \right)$$

$$v_{gs2} = - \left[ g_{m1}v_{in} + v_{out} \left( g_{m3} + \frac{1}{r_{o1}} + \frac{1}{r_{o3}} \right) \right] (r_{o1} \parallel r_{o3})$$

$$= - \left[ g_{m1}v_{in} + \frac{v_{out}}{\frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o3}} \right] (r_{o1} \parallel r_{o3})$$

$$v_{out} = -g_{m2}r_{o2} \left[ g_{m1}v_{in} + \frac{v_{out}}{\frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o3}} \right] (r_{o1} \parallel r_{o3})$$

$$v_{out} \left[ 1 + \frac{g_{m2}r_{o2} (r_{o1} \parallel r_{o3})}{\frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o3}} \right] = -g_{m1}g_{m2}r_{o2} (r_{o1} \parallel r_{o3}) v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1}g_{m2}r_{o2} (r_{o1} \parallel r_{o3})}{1 + \frac{g_{m2}r_{o2}(r_{o1} \parallel r_{o3})}{\frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o3}}}$$

5/5

3.22 (b) Since  $M_1$  and  $C_1$  form a closed loop, no current can flow through  $M_2$ . Assuming  $V_{b2} > V_{TH2}$ ,  $V_X = 0$  always. This means that at time  $t = 0$ ,  $V_Y = V_{DD}$ . Initially,  $M_1$  is in saturation.

$$\begin{aligned}
 I_{C_1} &= -C_1 \frac{dV_Y}{dt} \quad (\text{since } V_X = 0) \\
 &= I_{D_1} \\
 &= \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b1} - V_{TH1})^2 \\
 \int_{V_{DD}}^{V_Y} dV_Y &= - \int_0^t \frac{1}{C_1} \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b1} - V_{TH1})^2 dt \\
 V_Y - V_{DD} &= \frac{t}{C_1} \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b1} - V_{TH1})^2 \\
 V_Y &= V_{DD} - \frac{t}{C_1} \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b1} - V_{TH1})^2
 \end{aligned}$$


Once  $V_Y = V_{b1} - V_{TH1}$ ,  $M_1$  goes into triode. We can find the transition point as follows:

$$\begin{aligned}
 V_Y &= V_{DD} - \frac{t}{C_1} \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b1} - V_{TH1})^2 = V_{b1} - V_{TH1} \\
 t &= \frac{2(V_{DD} - V_{b1} + V_{TH1})}{\mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b1} - V_{TH1})^2}
 \end{aligned}$$

Now we have to solve the differential equation for this case:

$$-C_1 \frac{dV_Y}{dt} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 [2(V_{b1} - V_{TH1}) V_Y - V_Y^2]$$

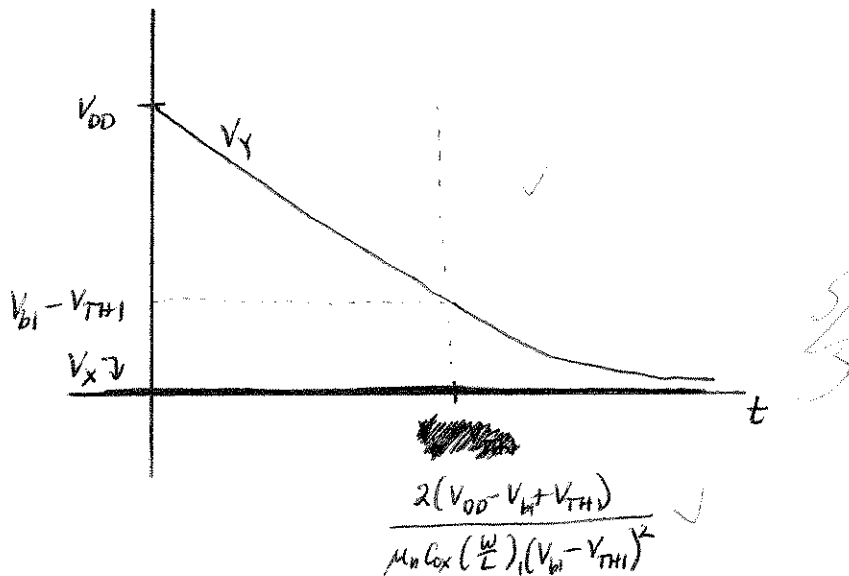Since this is again difficult to solve analytically, here is a qualitative plot.



2. (a) We can extract some parameters from the SPICE model. For simplicity, assume that  $M_2$  and  $M_3$  have their thresholds modified by 0.05 V due to the body effect.

$$\begin{aligned}
 V_{TH4} &= 0.480 \text{ V} \\
 \mu_n C_{ox} &= 261.2 \text{ } \mu\text{A}/\text{V}^2 \\
 V_{TH1} &= -0.500 \text{ V} \\
 \mu_p C_{ox} &= 108.0 \text{ } \mu\text{A}/\text{V}^2 \\
 \frac{W}{L} &= \frac{25}{0.18} \\
 \lambda_n &= 0.323 \text{ V}^{-1} \\
 \lambda_p &= 0.324 \text{ V}^{-1} \\
 V_{GS5} = V_{GS4} = V_{TH5} + \sqrt{\frac{2I_{D5}}{\mu_n C_{ox} \frac{W}{L} (1 + \lambda_n V_{DS5})}} \\
 V_{DS5} &= V_{GS5} \\
 V_{GS4} &= 0.631 \text{ V} \\
 V_{DS4} &= V_{GS4} - V_{TH4} \text{ (since } M_4 \text{ is at the edge of saturation)} \\
 &= 0.151 \text{ V} \\
 I_{D4} = I_{D1} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS4} - V_{TH4})^2 (1 + \lambda_n V_{DS4}) \\
 &= 436 \text{ } \mu\text{A} \\
 V_{SG1} &= |V_{TH1}| + \sqrt{\frac{2I_{D1}}{\mu_p C_{ox} \frac{W}{L} (1 + \lambda_p V_{SD1})}} \\
 V_{SD1} &= V_{SG1} - |V_{TH1}| \text{ (since } M_1 \text{ is at the edge of saturation)} \\
 V_{SG1} &= |V_{TH1}| + \sqrt{\frac{2I_{D1}}{\mu_p C_{ox} \frac{W}{L} [1 + \lambda_p (V_{SG1} - |V_{TH1}|)]}} \\
 V_{SG1} &= 0.732 \text{ V} \\
 V_{SD1} &= 0.232 \text{ V} \\
 V_{out} &= V_{DD} - V_{SG1} = 1.068 \text{ V} \\
 V_{DS3} &= V_{out} - V_{DS4} = 0.916 \text{ V} \\
 V_{GS3} &= V_{TH3} + \sqrt{\frac{2I_{D3}}{\mu_n C_{ox} \frac{W}{L} (1 + \lambda_n V_{DS3})}} \\
 V_{GS3} &= 0.666 \text{ V} \\
 V_{b2} &= V_{GS3} + V_{DS4} = \boxed{0.817 \text{ V}} \quad \checkmark \\
 V_{SD2} &= V_{DD} - V_{SD1} - V_{out} \\
 &= 0.500 \text{ V} \\
 V_{SG2} &= |V_{TH2}| + \sqrt{\frac{2I_{D2}}{\mu_p C_{ox} \frac{W}{L} (1 + \lambda_p V_{SD2})}} \\
 &= 0.774 \text{ V} \\
 V_{b1} &= V_{DD} - V_{SD1} - V_{SG2} = \boxed{0.794 \text{ V}} \quad \checkmark
 \end{aligned}$$

- (b) In order for all transistors to remain in saturation, we require  $V_{out} > V_{b2} - V_{TH3}$  and  $V_{out} < V_{b1} + |V_{TH2}|$ . Thus, the swing is  $\boxed{0.264 \text{ V} < V_{out} < 1.367 \text{ V}}$ .
- (c) The SPICE model does not provide a value of  $\gamma$  or  $\eta$ , so let's simply assume that  $\eta = 0.3$  for  $M_2$

and  $M_3$  as an approximation.

$$\frac{V_{out}}{V_A} = -g_{m1} \{ [r_{o1} + r_{o2} + (1 + \eta) g_{m2} r_{o1} r_{o2}] \parallel [r_{o3} + r_{o4} + (1 + \eta) g_{m3} r_{o3} r_{o4}] \}$$

$$g_{m1} = \mu_p C_{ox} \frac{W}{L} (V_{SG1} - |V_{TH1}|) = 3.48 \text{ mS}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda_p I_D} = 7.085 \text{ k}\Omega$$

$$g_{m2} = \mu_p C_{ox} \frac{W}{L} (V_{SG2} - |V_{TH2}|) = 3.36 \text{ mS}$$

$$g_{m3} = \mu_n C_{ox} \frac{W}{L} (V_{GS3} - V_{TH3}) = 4.93 \text{ mS}$$

$$g_{m4} = \mu_n C_{ox} \frac{W}{L} (V_{GS4} - V_{TH4}) = 5.48 \text{ mS}$$


$$r_{o3} = r_{o4} = \frac{1}{\lambda_n I_D} = 7.107 \text{ k}\Omega$$

$$\frac{V_{out}}{V_A} = \boxed{-480} \quad \checkmark$$

$$G_m = 3.48 \text{ mS}$$

$$R_{out} = 137.9 \text{ k}\Omega$$

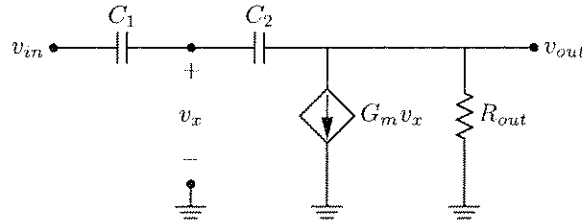To find the closed-loop gain, we can model the open-loop amplifier using the values of  $G_m$  and  $R_{out}$  found above, then add the feedback network in separately.



$$v_x = v_{out} + (v_{out} - v_{in}) \frac{C_1}{C_1 + C_2}$$

$$G_m v_x + \frac{v_{out}}{R_{out}} + (v_{out} - v_{in}) s (C_1 \parallel C_2) = 0$$

$$G_m v_{out} + G_m (v_{in} - v_{out}) \frac{C_1}{C_1 + C_2} + \frac{v_{out}}{R_{out}} + (v_{out} - v_{in}) s (C_1 \parallel C_2) = 0$$

$$v_{out} \left[ (sC_2 - G_m) \frac{C_1}{C_1 + C_2} + G_m + \frac{1}{R_{out}} \right] = v_{in} (sC_2 - G_m) \frac{C_1}{C_1 + C_2}$$

$$\frac{v_{out}}{v_{in}} = \frac{(sC_2 - G_m) \frac{C_1}{C_1 + C_2}}{(sC_2 - G_m) \frac{C_1}{C_1 + C_2} + G_m + \frac{1}{R_{out}}}$$

Let  $s \rightarrow 0$  to get:

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \frac{-G_m \frac{C_1}{C_1 + C_2}}{-G_m \frac{C_1}{C_1 + C_2} + G_m + \frac{1}{R_{out}}} \\ &= \frac{-4/5 G_m}{1/5 G_m + \frac{1}{R_{out}}} \\ &\approx \boxed{-4} \quad \checkmark \end{aligned}$$

S/B

The approximation in the last step comes from assuming  $1/5G_m \gg 1/R_{out}$ , which is true for the values derived earlier.

- (d) Simulating the circuit in SPICE using  $V_{b1}$  and  $V_{b2}$  as derived, it turns out that  $M_1$  and  $M_4$  are just slightly in linear (which is likely a consequence of designing for them to be at the edge of saturation). In order to correct for this, I've lowered  $V_{b1}$  to 0.730 V and increased  $V_{b2}$  to 0.830 V, which puts all transistors in saturation. The resulting netlist is as follows:

```
* HW2

.inc 'ee215a.mod'

vin  vin    gnd  ac 1V
c1   vin    vg1  4pF
m1   vd1    vg1  vdd vdd CMOSP W=25u L=0.18u
m2   vout   vb1  vd1 vdd CMOSP W=25u L=0.18u
c2   vg1    vout 1pF
m3   vout   vb2  vd4 gnd CMOSN W=25u L=0.18u
m4   vd4    vg4  gnd gnd CMOSN W=25u L=0.18u
m5   vg4    vg4  gnd gnd CMOSN W=25u L=0.18u
vdd  vdd    gnd  1.8V
i1   vdd    vg4  500uA
r1   vg1    vout 10MEG
vb1  vb1    gnd  0.730V
vb2  vb2    gnd  0.830V


.op
.ac dec 500 10 1T
.option post=2 nomod

.end
```

The output from the operating point analysis shows that all transistors are saturated with a bias current of 394  $\mu\text{A}$ , which is close to the calculated value of 436  $\mu\text{A}$ :

element	0:m1	0:m2	0:m3	0:m4	0:m5
model	0:cmosp	0:cmosp	0:cmosn	0:cmosn	0:cmosn
region	Saturati	Saturati	Saturati	Saturati	Saturati
id	-393.6548u	-393.6548u	393.6548u	393.6548u	500.0000u

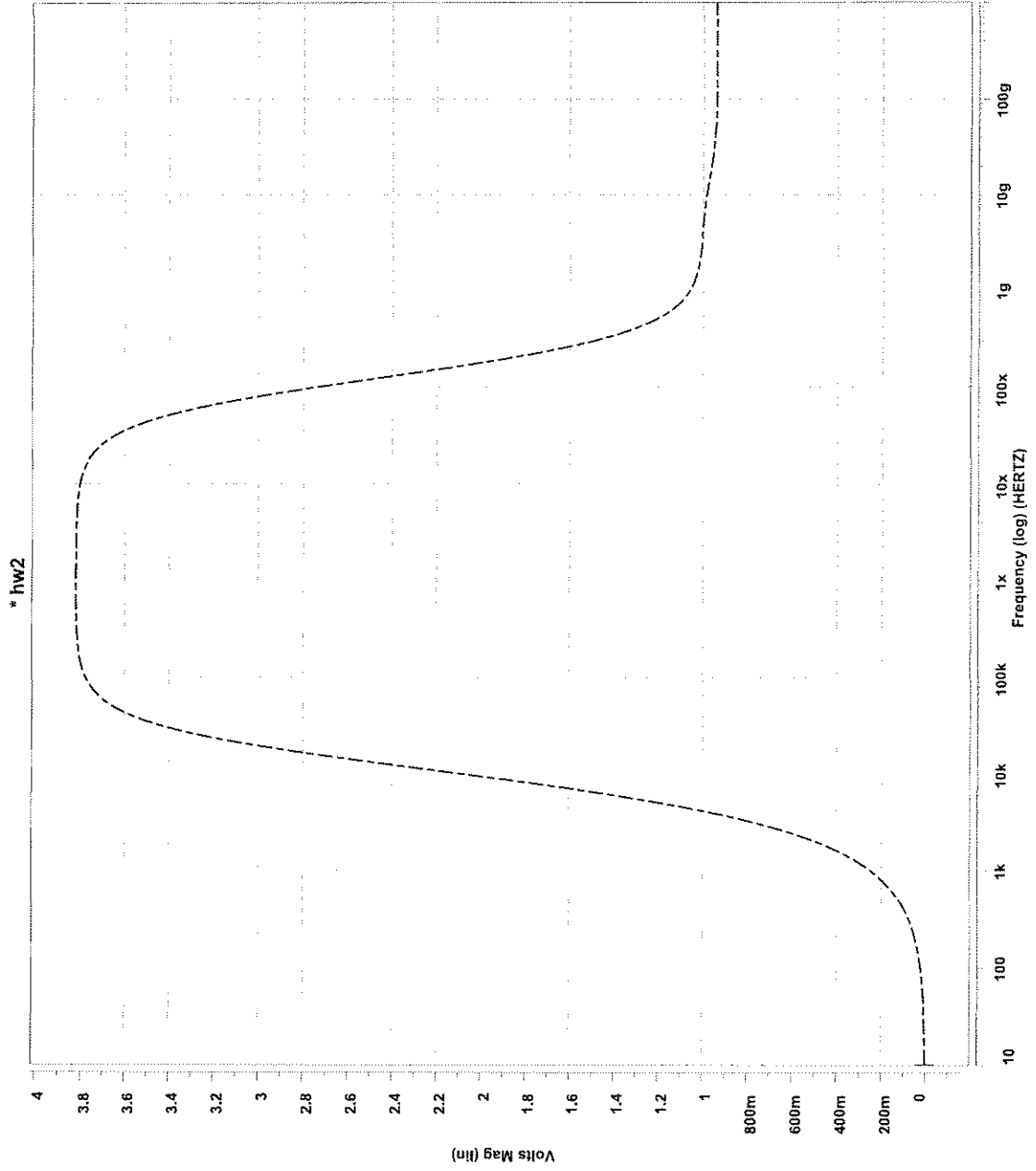The gain plot shows the magnitude of the midband gain is 3.8, which is very close to the calculated value of 4.



5/3

