
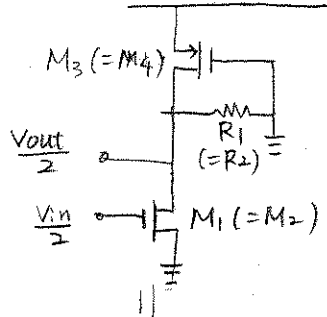


Name: Jin Hwan Jeon.

40/40

#1.

<4.18> $\lambda \neq 0$

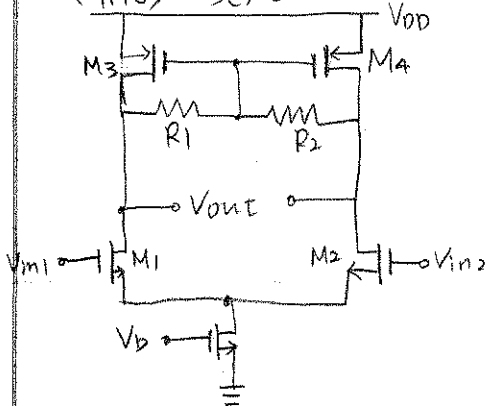

<4.38(d)>


$M_1 = M_2, M_3 = M_4$

$R_1 = R_2$


Assumption: All transistors (and resistors) are identical.
That is, no process variation is considered.

$$A_v = -g_{m1} (Y_{01} \parallel Y_{03} \parallel R_1)$$

5/5

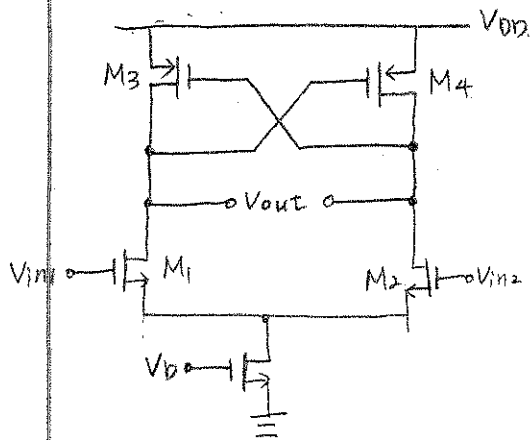

<4.39(c)>

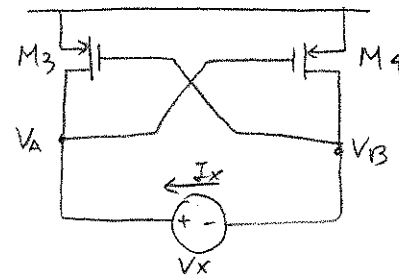

Find impedance (looked up from two output node) ($\lambda = 0$)


$$V_x = V_A - V_B$$

$$\begin{aligned} I_x &= g_{m3} V_B \\ I_x &= -g_{m4} V_A \end{aligned} \Rightarrow 2I_x = g_{m3} V_B - g_{m4} V_A \quad \textcircled{1}$$

Assume $g_{m3} = g_{m4}$


$$\begin{aligned} \textcircled{1} \text{ becomes, } 2I_x &= -g_{m3,4} (V_A - V_B) \\ &= g_{m3,4} V_x \end{aligned}$$
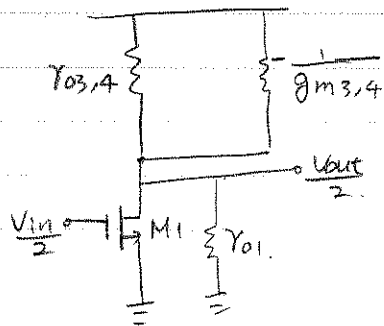
$$\therefore \frac{V_x}{I_x} = \frac{-2}{g_{m3,4}}$$




$$A_v = -g_{m1} (Y_{01} \parallel Y_{03,4} \parallel -\frac{1}{g_{m3,4}})$$

#2. <4.21> $\lambda=0, r \neq 0$

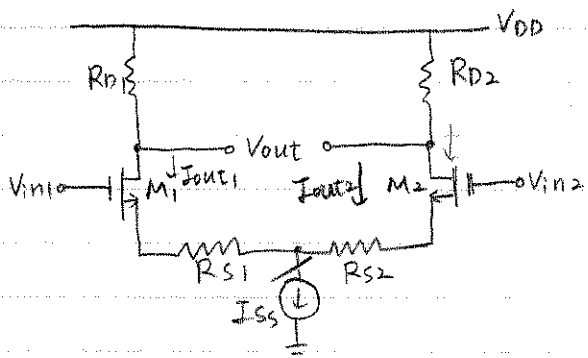

Using superposition

i) V_{in2} is grounded.

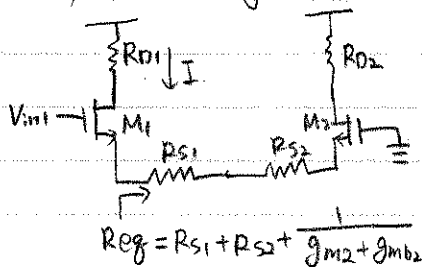

$$G_{m1} = \frac{g_{m1}}{1 + (g_{m1} + g_{mb1})(R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}})}$$

$$R_{eq} = R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}}$$

ii) V_{in1} is grounded, G_{m2} is exactly same as G_{m1} except

$$G_{m2} = \frac{g_{m2}}{1 + (g_{m2} + g_{mb2})(R_{S1} + R_{S2} + \frac{1}{g_{m1} + g_{mb1}})}$$


$g_{m1} \rightarrow g_{m2}, g_{mb2} \rightarrow g_{mb1}$

$$\Rightarrow I_{out1} = I_1 - I_2 \quad I_{out2} = I_2 - I_1$$

$$V_{out} = -R_{D1} I_{out1} + R_{D2} I_{out2} = -R_{D1}(I_1 - I_2) - R_{D2}(I_1 - I_2) = -(R_{D1} + R_{D2})(I_1 - I_2)$$

$$\therefore V_{out} = -(R_{D1} + R_{D2})(G_{m1} V_{in1} - G_{m2} V_{in2})$$

#3. <4.26>

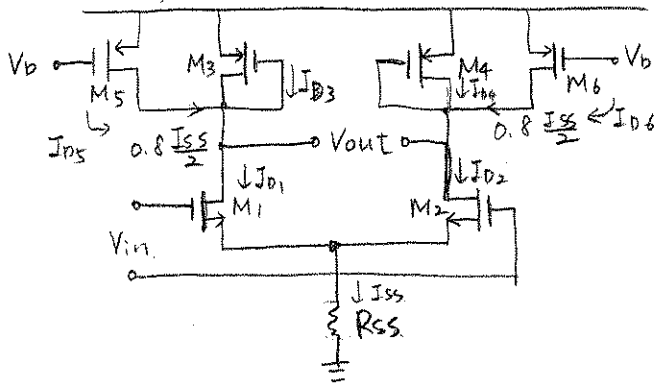

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

$$R_D = \frac{1}{g_{m4}} \parallel (r_{o1} \parallel r_{o3} \parallel r_{o5}) \approx \frac{1}{g_{m4}} \quad (\because r_o \text{ is usually large})$$

$$I_{D5} + I_{D3} = \frac{I_{SS}}{2} = I_{D4} + I_{D6}$$

$$I_{D6} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_6 (|V_{GS6}| - |V_{TH,p}|)^2$$

$$\Rightarrow \frac{\partial I_{D6}}{\partial V_{TH,p}} = -\mu_p C_{ox} \left(\frac{W}{L}\right)_6 (|V_{GS6}| - |V_{TH,p}|)$$

$$\Rightarrow \partial I_{D6} = -\mu_p C_{ox} \left(\frac{W}{L}\right)_6 (V_{DD} - V_b - |V_{TH,p}|) \cdot \partial V_{TH,p}$$

$$\Rightarrow \Delta I_{D6} = \mu_p C_{ox} \left(\frac{W}{L}\right)_6 (V_{DD} - V_b - |V_{TH,p}|) \cdot \Delta V_{TH,p}$$

$$g_{m4} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_4 I_{D4}}$$

$$\frac{\partial g_{m4}}{\partial I_{D4}} = \sqrt{\frac{\mu_p C_{ox} \left(\frac{W}{L}\right)_4}{2 I_{D4}}} \Rightarrow \Delta g_{m4} = \sqrt{\frac{\mu_p C_{ox} \left(\frac{W}{L}\right)_4}{2 I_{D4}}} \Delta I_{D4}$$


$$\frac{\partial R_D}{\partial g_{m4}} = -\frac{1}{g_{m4}} \quad \frac{\Delta R_D}{R_D} = -\frac{\Delta g_{m4}}{g_{m4}} \quad (\because R_D = \frac{1}{g_{m4}})$$

$$\frac{\Delta R}{R_D} = \frac{I_{D6}}{I_{D4}} \cdot \frac{V_{TH,p}}{V_{DD} - V_b - |V_{TH,p}|} \cdot \frac{\Delta V_{TH,p}}{V_{TH,p}}$$

$$CMRR = \frac{1 + 2 g_{m1} R_{SS}}{\Delta R_D / R_D} = \frac{1 + 2 g_{m1} R_{SS}}{4} \cdot \frac{(V_{DD} - V_b - |V_{TH,p}|)}{V_{TH,p}} \cdot \frac{V_{TH,p}}{\Delta V_{TH,p}}$$


3/3

#4 <5.10(a)>

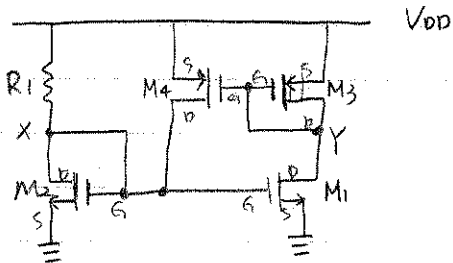

Assume M_1 and M_2 are identical
 M_3 and M_4 are identical.

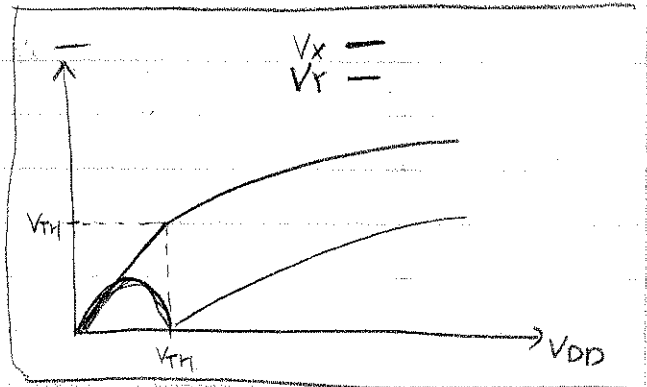- i) $V_{DD} < V_{TH1,2}$
 All transistors are off.
 $\therefore V_X = V_{DD}$
 V_Y is floating





- ii) $V_{DD} > V_{TH1,2}$
 M_2 turns on, so M_1 turns on.
 (saturation) (triode)
 M_3 : saturation, M_4 : triode region.

$$V_X = V_{GS2} \quad V_Y = V_{DD} - |V_{GS3}| \approx V_{DD} - V_{GS2} \quad (\text{due to } I_{D2} = I_{D1} = |I_{D3}|)$$

$$V_X > V_Y$$

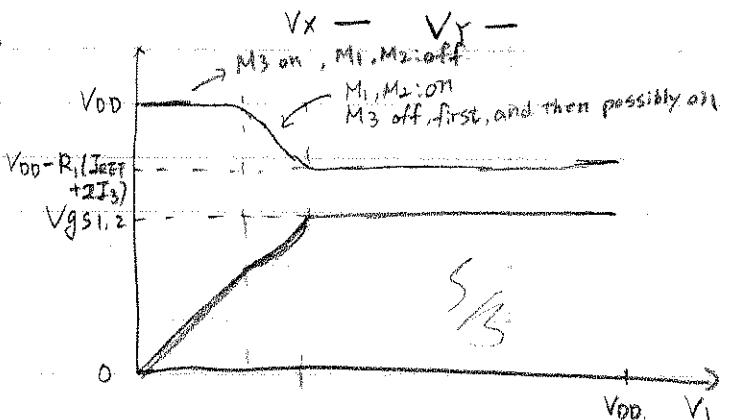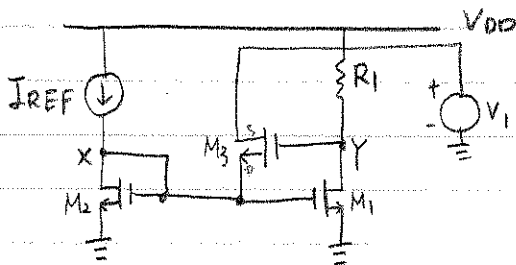
#5 <5.12(b)> V_X and V_Y as a function of V_I for $0 < V_I < V_{DD}$



- i) $V_I = 0$
 M_1 and M_2 turn off.
 $V_X = 0V \quad V_Y = V_{DD} \quad V_{DS3} = I_{REF} \times \frac{1}{g_{m3}}$


At low value of V_I , roles of drain and source of M_3 are switched.

#71 <5.20(b)>

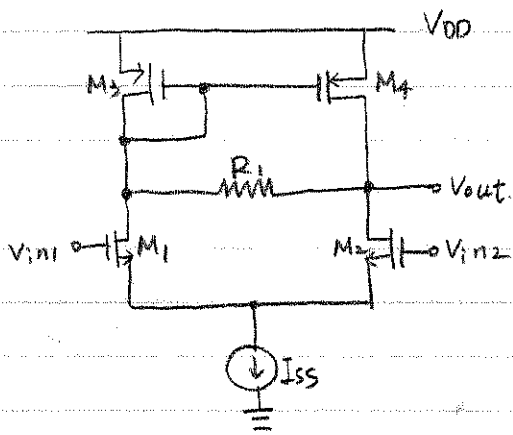

Using superposition,

1) $V_{in1} = +\frac{\Delta V}{2}$

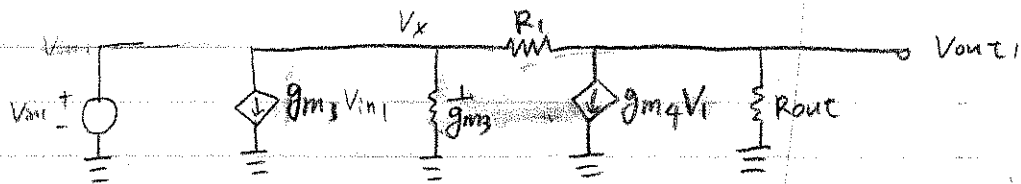


$$g_{m1} V_{in1} + g_{m3} V_x + \frac{V_x - V_{out1}}{R_i} = 0$$

$$g_{m2} V_x + \frac{V_{out1}}{R_{out}} + \frac{V_{out1} - V_x}{R_i} = 0$$

$$\frac{V_{out1}}{V_{in1}} = g_{m1} R_{out} \left[\frac{g_{m3} R - 1}{g_{m3} R + 2R_{out} + 1} \right]$$

2) $V_{in2} = -\frac{\Delta V}{2}$

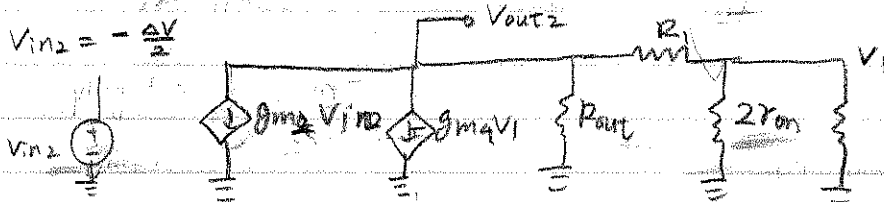

$$V_1 = V_{out2} \frac{g_{m3} \parallel 2R_{on}}{R + 2R_{on} \parallel \frac{1}{g_{m3}}} = V_{out2} \frac{2R_{on}}{2R_{on} + 2g_{m3} R_{on} R_i + R_i}$$

$$V_{out2} = \left(g_{m2} V_{in2} - g_{m4} V_{out2} - \frac{2R_{on}}{2R_{on} + 2g_{m3} R_{on} R_i + R_i} \right) \left((R_i + 2R_{on} \parallel \frac{1}{g_{m3}}) \parallel R_{out} \right)$$

$$\frac{V_{out2}}{V_{in2}} = -g_{m2} \frac{[(R_i + 2R_{on} \parallel \frac{1}{g_{m3}})]}{1 + \frac{2g_{m2} R_{on}}{R_i + 2R_{on} + 2g_{m3} R_{on} R_i}} \left[(R_i + 2R_{on} \parallel \frac{1}{g_{m3}}) \parallel R_{out} \right]$$

$$\therefore A_V = \frac{V_{out1} + V_{out2}}{V_{in1} - V_{in2}} = \frac{V_{out1} + V_{out2}}{\frac{\Delta V}{2} - (-\frac{\Delta V}{2})} = \frac{V_{out1} + V_{out2}}{\Delta V}$$

9/5