

58/60

1.

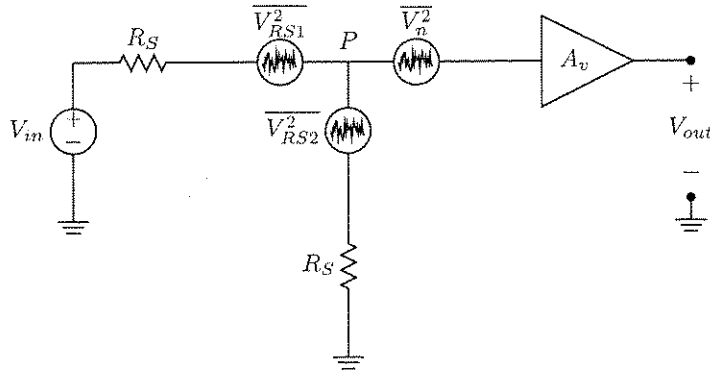


Figure 1: LNA driven by a source with impedance  $R_S$  and impedance matched with a resistor to ground

- (a) Since the LNA has a high input impedance, we can model the input-referred noise with just a voltage source  $\overline{V_n^2}$ , as shown in Fig. 1. From Eq. (2.81), we know that  $NF_1$  (the noise figure of the LNA itself with respect to  $R_S$ ) is:

$$NF_1 = 1 + \frac{\overline{V_n^2}}{4kTR_S}$$

From Eq. (2.84), we can find the noise figure of the overall circuit by finding  $V_{n,out}^2$ . First, note that  $\overline{V_{RS1}^2}$  and  $\overline{V_{RS2}^2}$  see the same voltage gain  $\alpha = 1/2$  between the input port and node  $P$ .

$$\begin{aligned} V_{n,out}^2 &= \alpha^2 A_v^2 \overline{V_{RS1}^2} + \alpha^2 A_v^2 \overline{V_{RS2}^2} + A_v^2 \overline{V_n^2} \\ &= \alpha^2 A_v^2 4kTR_S + \alpha^2 A_v^2 4kTR_S + A_v^2 \overline{V_n^2} \\ &= A_v^2 \left( \alpha^2 8kTR_S + \overline{V_n^2} \right) \\ NF &= \frac{V_{n,out}^2}{A^2} \frac{1}{4kTR_S} \quad (\text{Eq. 2.84}) \\ &= \frac{A_v^2 \left( \alpha^2 8kTR_S + \overline{V_n^2} \right)}{\alpha^2 A_v^2} \frac{1}{4kTR_S} \\ &= 2 + \frac{V_n^2}{kTR_S} \\ &= \boxed{4NF_1 - 2} \quad \checkmark \textcircled{9} \end{aligned}$$

- (b) Let  $NF_0 = 2$  be the noise figure of the resistor to ground at node  $P$  (in general, this is  $1 + R_S/R_P$  where  $R_P$  is the resistor value, but since  $R_S = R_P$ , this reduces to 2).

We can see that we'll need to reference the noise figure of the LNA to the output impedance of the previous stage (let's call this result  $NF'_1$ ). We can see that the impedance driving this stage is  $R_S/2$ , so we'll reference  $NF'_1$  to a source impedance of  $R_S/2$ .

Finally, we need to find the available power gain of  $R_P$ . From Eq. (2.104), we have:

$$A_P = \left( \frac{R_{in}}{R_S + R_{in}} \right)^2 A_v^2 \frac{R_S}{R_{out}}$$

We can see that  $R_{in} = R_S$ ,  $A_v = 1$ , and  $R_{out} = R_S/2$ . Thus, we get  $A_P = 1/2$ .

$$\begin{aligned}
 NF &= NF_0 + \frac{NF'_1 - 1}{A_P} \\
 NF_0 &= 2 \\
 NF'_1 &= 1 + \frac{\overline{V_n^2}}{2kTR_S} = 2NF_1 - 1 \\
 A_P &= 1/2 \\
 NF &= 2 + \frac{2NF_1 - 1 - 1}{1/2} \\
 &= \boxed{4NF_1 - 2} \quad \text{⑤}
 \end{aligned}$$

This matches the noise figure calculated in part (a).

2. The SPICE netlist is listed at the end of this problem.

⑤ (a) From the SPICE model, we have:

$$\begin{aligned}
 \mu_n &= 310.235 \text{ cm}^2/\text{V} \cdot \text{s} \\
 t_{ox} &= 4.1 \text{ nm} \\
 C_{ox} &= 0.8418 \text{ } \mu\text{F}/\text{cm}^2 \\
 \mu_n C_{ox} &= 261.2 \text{ } \mu\text{A}/\text{V}^2
 \end{aligned}$$

From the current mirror that biases  $M_1$ , we see that:

$$I_{D1} = I_{D3} = 5I_{D4} = 2.5 \text{ mA}$$

Since the SPICE model doesn't provide  $\phi_F$  or  $\gamma$ , we'll have to assume a reasonable value for  $\eta$  for this calculation, then adjust the width in SPICE until  $g_{m1} + g_{mb1} = (50 \Omega)^{-1}$ . Let's assume  $\eta = 0.1$ .

$$\begin{aligned}
 g_{m1} (1 + \eta) &= (50 \Omega)^{-1} = \sqrt{2 \frac{W_1}{L_1} \mu_n C_{ox} I_{D1}} (1 + \eta) \\
 \checkmark \quad W_1 &= \boxed{45.56 \text{ } \mu\text{m}}
 \end{aligned}$$

Using  $W_1 = 45.56 \text{ } \mu\text{m}$  in the SPICE simulation gives

$$\begin{aligned}
 g_{m1} &= 16.7837 \text{ mS} \\
 g_{mb1} &= 3.0493 \text{ mS}
 \end{aligned}$$

Thus, we have  $g_{m1} + g_{mb1} = (50.42 \Omega)^{-1}$ , which matches well with the calculations.

⑤ (b) We want the inductor to resonate with the capacitance at the output at 5.2 GHz. SPICE reports the total capacitance at the output due to transistors  $M_1$  and  $M_2$ , and we can calculate the

parasitic capacitance due to  $L_1$  based on the inductor model provided.

$$\begin{aligned}
 C_{D1,tot} &= 71.8427 \text{ fF} \\
 C_{G2,tot} &= 36.8818 \text{ fF} \\
 C_P &= L_1 \times 10^9 \times 10^{-14} = 10^{-5} L_1 \\
 f &= 5.2 \text{ GHz} = \frac{1}{2\pi\sqrt{L_1(C_{D1,tot} + C_{G2,tot} + C_P)}} \\
 &= \frac{1}{2\pi\sqrt{L_1(C_{D1} + C_{G2} + 10^{-5}L_1)}} \\
 \checkmark L_1 &= \boxed{5.665 \text{ nH}} \\
 C_P &= 56.65 \text{ fF} \\
 Q &= \frac{R_P}{\omega L_1} \\
 &= \frac{R_P}{2\pi f L_1} \\
 R_P &= 2\pi f L_1 Q \\
 &= 740.36 \Omega
 \end{aligned}$$

Using these values in the SPICE simulation and performing an AC analysis produces the gain vs. frequency plot shown in Fig. 2. The plot shows a peak right around  $f = 5.2$  GHz.

- (c)  $L_1$  will present a very different impedance at 5.2 GHz than it does at DC, meaning that looking only at  $(g_m + g_{mb})^{-1}$  as the input resistance neglects the inductor's impedance at 5.2 GHz.

8/10

Using SPICE, we find that  $W_1 = 71 \mu\text{m}$  gives  $R_{in} = 49.80 \Omega$  at 5.2 GHz.

However, since we changed  $W_1$ ,  $C_{D1,tot}$  will also change. This causes the resonance frequency to shift as well, meaning we need to recalculate  $L_1$  (causing  $R_{in}$  to change, and so on). Iterating over these calculations a few times produces:

$$\begin{aligned}
 W_1 &= \boxed{83.0 \mu\text{m}} \\
 L_1 &= 4.42 \text{ nH} \\
 C_P &= 44.2 \text{ fF} \\
 R_P &= 577.65 \Omega \\
 R_{in} &= 49.75 \Omega
 \end{aligned}$$

The new AC response is shown in Fig. 3.

- (d) Performing an FFT analysis in SPICE (using a 8192-point FFT and a Blackman window for weighting) gives the output spectrum shown in Fig. 4. The two primary tones are located at 5.2 GHz and 5.3 GHz, and the  $IM_3$  products are located at 5.1 GHz and 5.4 GHz. The amplitude of the input tones was chosen to be 10 mV to ensure we do not experience any gain compression.

5

From this plot, we can find  $IIP_3$  as follows:

$$\begin{aligned}
 IIP_3|_{\text{dBm}} &= \frac{\Delta P|_{\text{dB}}}{2} + P_{in}|_{\text{dBm}} \\
 P_{in} &= \frac{V_{in,rms}^2}{4R_S} = \frac{V_{in}^2}{8R_S} \\
 V_{in} &= 10 \text{ mV} \\
 P_{in} &= 0.25 \mu\text{W} = -36.0206 \text{ dBm} \\
 \Delta P &= 77.0807 \text{ dB} \\
 IIP_3 &= \boxed{2.51975 \text{ dBm}}
 \end{aligned}$$

We can read the gain off of the AC response in Fig. 3.

$$A_v = 5.4785 = \boxed{14.77 \text{ dB}}$$

- (c) First, we need to calculate  $L_2$  for resonance at 5.2 GHz.

⑥

$$C_{D2,tot} = 23.8292 \text{ fF}$$

$$f = 5.2 \text{ GHz} = \frac{1}{2\pi\sqrt{L_2(C_{D2,tot} + 60 \text{ fF} + 10^{-5}L_2)}}$$

$$L_2 = 6.3558 \text{ nH}$$

Plotting the AC response of the circuit in SPICE shows this value of  $L_2$  to be a little too large (i.e., the resonance occurs slightly below 5.2 GHz). Using  $L_2 = 6.3 \text{ nH}$  puts the resonance at 5.2 GHz. Fig. 5 shows the AC response of the circuit, from which we can obtain the gain.

$$A_v = 4.1442 = \boxed{12.35 \text{ dB}}$$

Fig. 6 shows the output spectrum for a two-tone test, which allows us to calculate  $IIP_3$ .

$$IIP_3|_{\text{dBm}} = \frac{\Delta P|_{\text{dB}}}{2} + P_{in}|_{\text{dBm}}$$

$$P_{in} = \frac{V_{in,rms}^2}{4R_S} = \frac{V_{in}^2}{8R_S}$$

$$V_{in} = 10 \text{ mV}$$

$$P_{in} = 0.25 \text{ } \mu\text{W} = -36.0206 \text{ dBm}$$

$$\Delta P = 81.5554 \text{ dB}$$

$$IIP_3 = \boxed{4.7571 \text{ dBm}}$$

- (f) When we cascade the two stages, the capacitance at the gate of  $M_2$  will change (it will increase due to the Miller effect acting on  $C_{GD2}$ ), meaning the resonance frequency of the first stage will change. We must adjust  $L_1$  to compensate for this increased capacitance in order to retain a resonance frequency of 5.2 GHz. Using  $L_1 = 3.3 \text{ nH}$  maintains the appropriate resonance frequency when the stages are cascaded. Fig. 7 shows the AC response of the overall LNA.

⑩

The overall voltage gain is  $\boxed{16.423}$ . This is substantially less than the product of the voltage gains measured in parts (d) and (e). However, this is expected, since cascading the stages will decrease the gain of the first stage due to loading (and due to the smaller value of  $L_1$ , which forces a smaller  $R_P$  in order to maintain the same  $Q$ ). The loaded gain of the first stage is 4.2973, which gives an overall gain of 17.81 when multiplied by the gain of the second stage, giving relatively good agreement with the measured overall gain.

The overall  $IIP_3$  can be found from the spectrum of the output (shown in Fig. 8) as in previous parts of the problem. Doing so gives  $IIP_3 = \boxed{-7.626 \text{ dBm}}$ . We can calculate an expected  $IIP_3$  based on the result from (d) and (e) as follows (let subscript  $A$  indicate the first stage and subscript  $B$  indicate the second stage):

$$IIP_{3,A} = 2.51975 \text{ dBm} = 0.845313 \text{ V}$$

$$IIP_{3,B} = 4.7571 \text{ dBm} = 1.09367 \text{ V}$$

$$A_{v,A} = 4.2973$$

$$\frac{1}{IIP_3^2} = \frac{1}{IIP_{3,A}^2} + \frac{A_{v,A}^2}{IIP_{3,B}^2}$$

$$IIP_3 = 0.244 \text{ V} = -8.28 \text{ dBm}$$

This agrees relatively well with the value measured directly from the LNA.

⑥ (g) When we cascade the two stages, the input resistance drops to  $R_{in} = 43.67 \Omega$ . This is due to the increased capacitance at the output of the first stage and the decreased value of  $L_1$  (which decreases  $R_p$ ). The impedance at the drain of  $M_1$  is lowered due to these effects, causing the input resistance to decrease.

⑤ (h) The second stage limits the  $IIP_3$  of the LNA. If we look at the two terms in the equation for the  $IIP_3$  of a cascade, we can see that in this case:

$$\frac{1}{IIP_{3,A}^2} = 1.39947$$

$$\frac{A_{v,A}^2}{IIP_{3,B}^2} = 15.439$$

Clearly, the second term dominates. Qualitatively, we can see that the  $IIP_3$  of each individual stage is similar, but the moderate gain of the first stage causes the  $IIP_3$  of the second stage to dominate.

Here is the SPICE netlist used in this problem (the first and second stage were simulated independently before being combined in this netlist):

```
* EE215C HW1 Problem 2

.inc '215a.sp'
.option post accurate nomod

.param W1=83e-6
.param L1=3.3e-9
.param CP='L1*1e-5'
.param Q=4
.param PI=3.14159265358979
.param FREQ=5.2e9
.param RP='2*PI*FREQ*L1*Q'
.param L2=6.3e-9
.param CP2='L2*1e-5'
.param RP2='2*PI*L2*FREQ*Q'

vdd vdd gnd 1.8

* Used for AC analysis
** vin vin gnd AC 1

* Used for FFT
vin1 vin1 gnd sin(0 10m 5.2G 0 0 0)
vin2 vin vin1 sin(0 10m 5.3G 0 0 0)

* Comment out r1 when finding R_in
r1 vin 1 50
c1 1 vd3 1uF

m3 vd3 vd4 gnd gnd CMOSN W=25u L=0.25u
+PS='2*25e-6+1.2e-6' PD='2*25e-6+1.2e-6' AS='25e-6*0.6e-6' AD='25e-6*0.6e-6'
m4 vd4 vd4 gnd gnd CMOSN W=5u L=0.25u
+PS='2*5e-6+1.2e-6' PD='2*5e-6+1.2e-6' AS='5e-6*0.6e-6' AD='5e-6*0.6e-6'
c2 vd4 gnd 0.2p
i1 vdd vd4 0.5m
```

```

m1  vout1 vdd  vd3  gnd  CMOSN W=W1 L=0.18u
+PS='2*W1+1.2e-6' PD='2*W1+1.2e-6' AS='W1*0.6e-6' AD='W1*0.6e-6'
l1  vdd  vout1 L1
rp  vdd  vout1 RP
cp1 vdd  gnd  CP
cp2 vout1 gnd  CP

m2  vout  vout1 vs2  gnd  CMOSN W=15u L=0.18u
+PS='2*15e-6+1.2e-6' PD='2*15e-6+1.2e-6' AS='15e-6*0.6e-6' AD='15e-6*0.6e-6'
i2  vs2  gnd  2m
c3  vs2  gnd  1p
l2  vdd  vout  L2
c4  vout  gnd  60f
cp21 vout  gnd  CP2
cp22 vdd  gnd  CP2
rp2 vdd  vout  RP2

* Used when finding resonance frequency, gain, and R_in
.ac lin 1000 1G 10G

* Used to measure gain
** .measure ac gain find vm(vout) at = 5.2e9

* Used to measure R_in
** .measure ac itest find ir(vin) at = 5.2e9
** .measure ac rin param = '-1/itest'

* Used to plot the spectrum of the output to find IIP3
* Use a 8192-point FFT with a Blackman window
.tran 0.1p 100n
.fft v(vout) fmin=4.75G fmax=5.75G np=8192 format=unorm window=black

.end

```

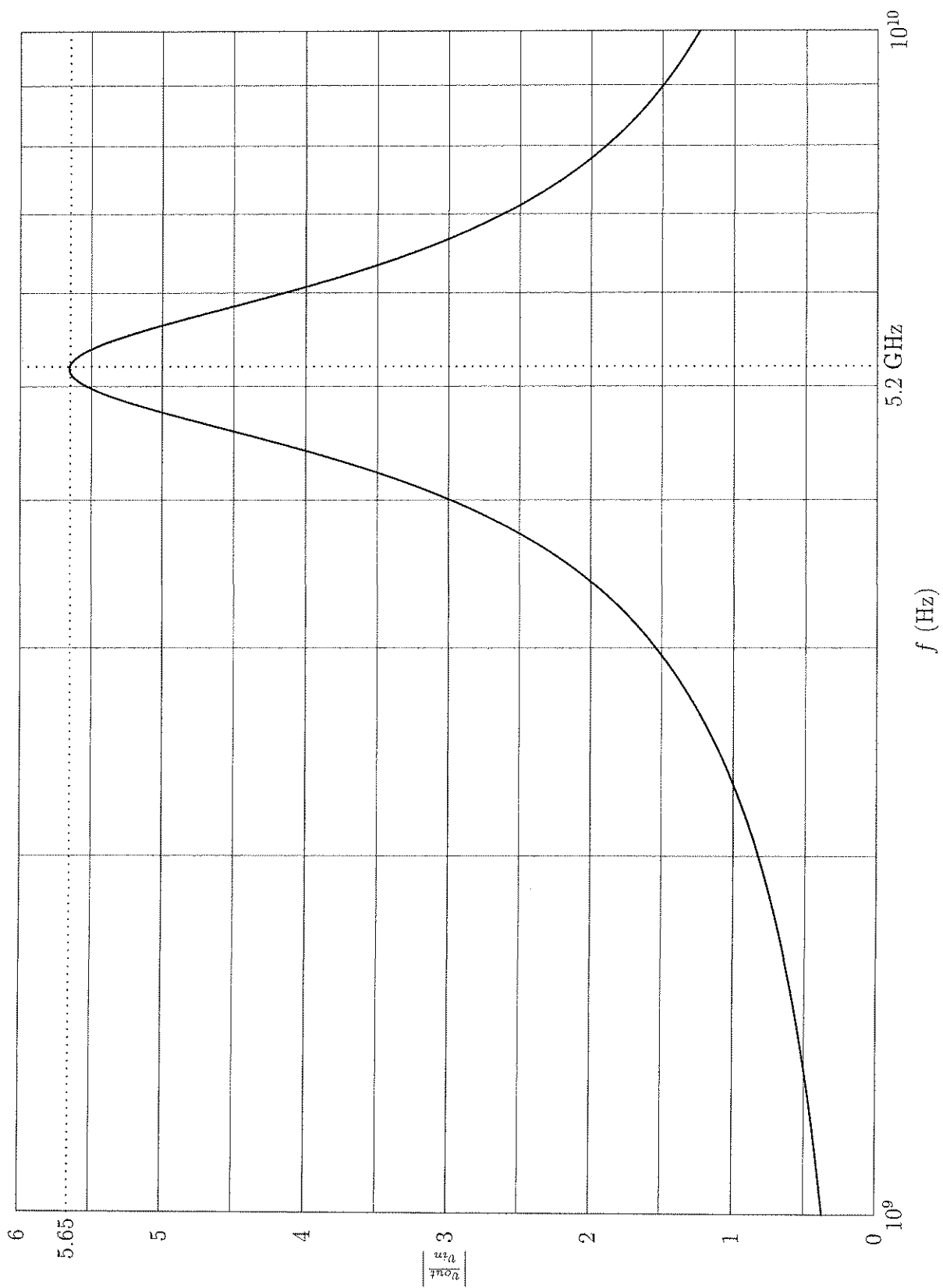


Figure 2: AC response of the LNA showing resonance at 5.2 GHz

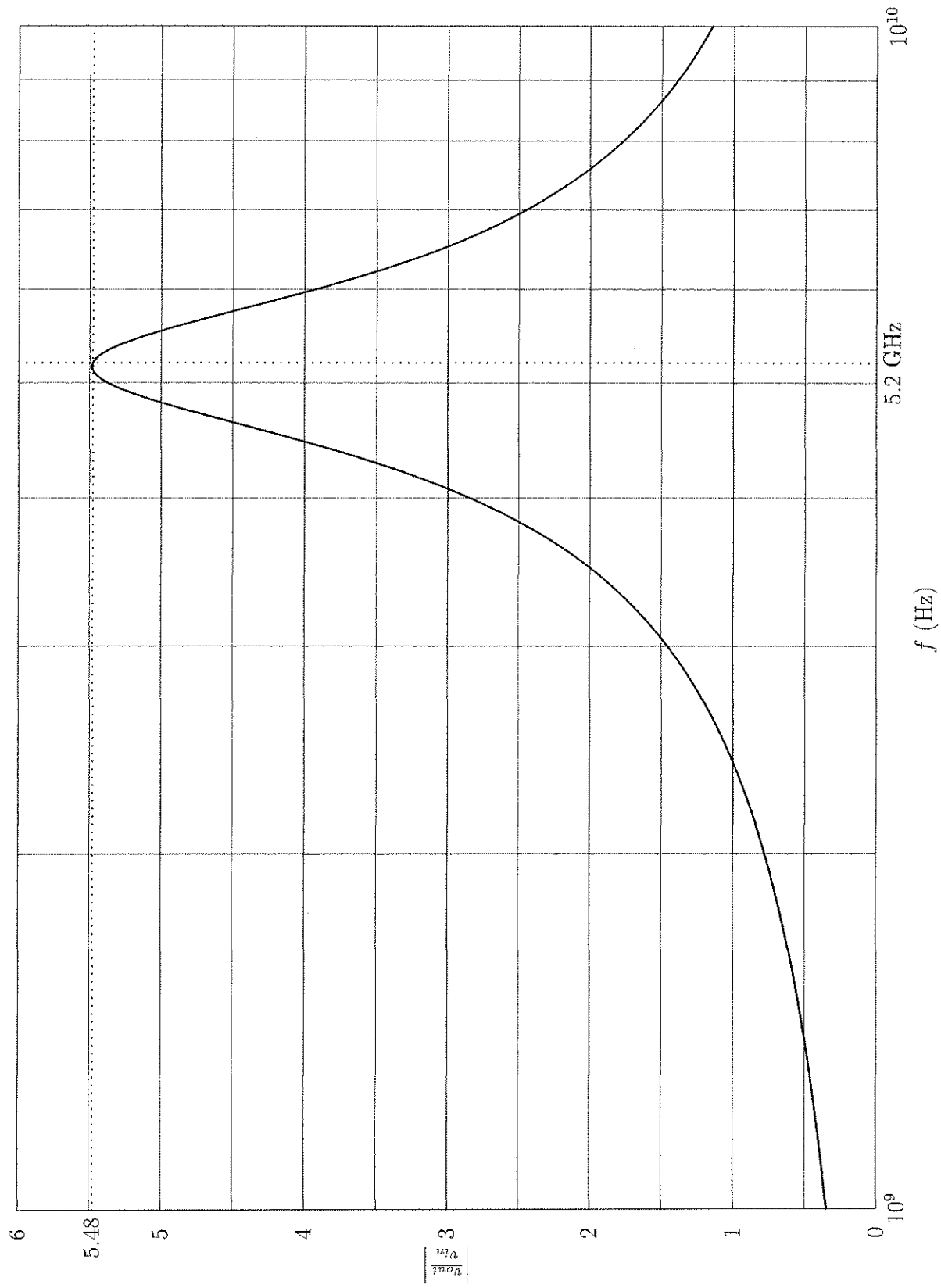


Figure 3: AC response of the LNA showing resonance at 5.2 GHz with an impedance match at the input



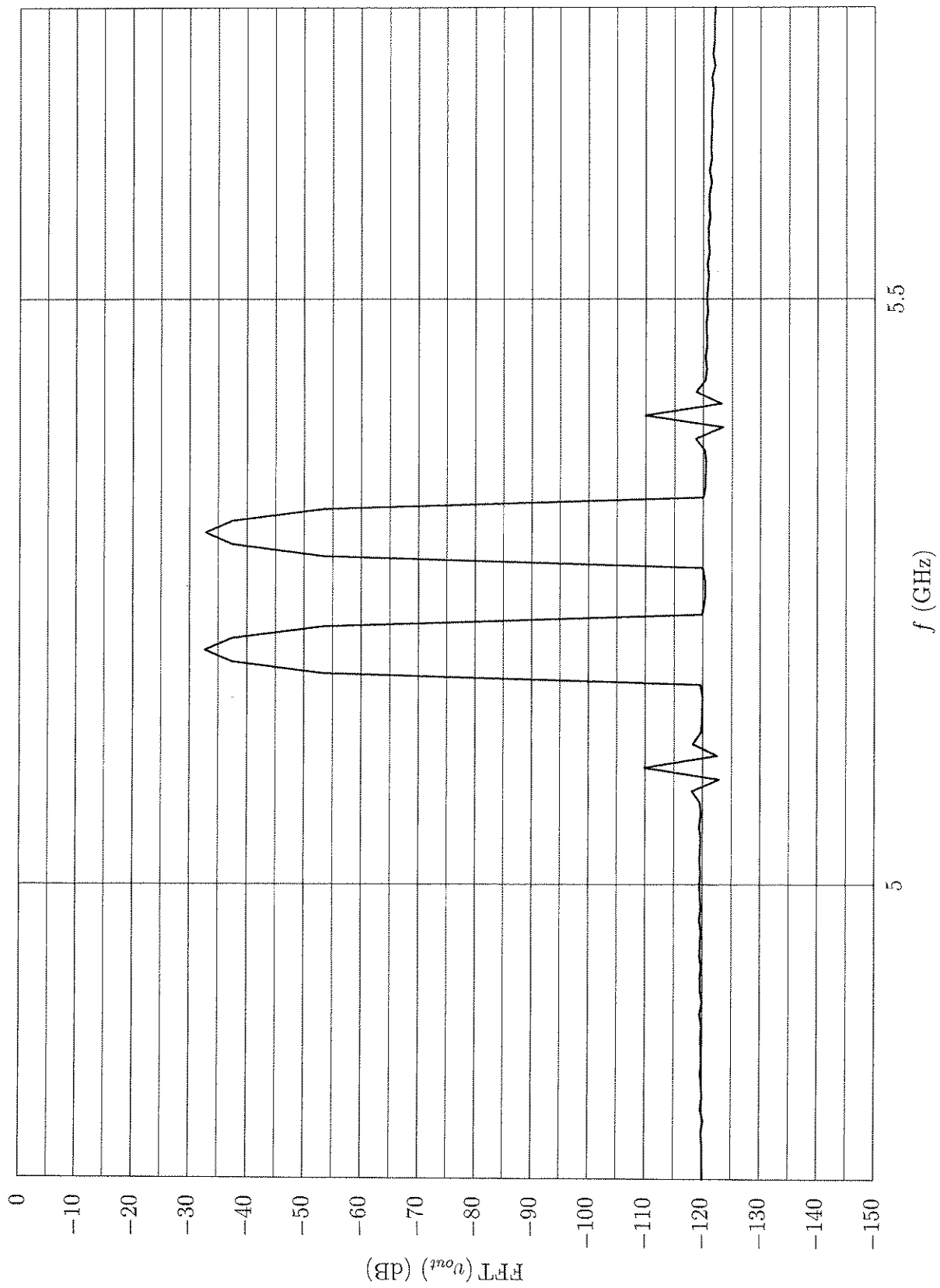


Figure 4: Output spectrum of the LNA with a two-tone input

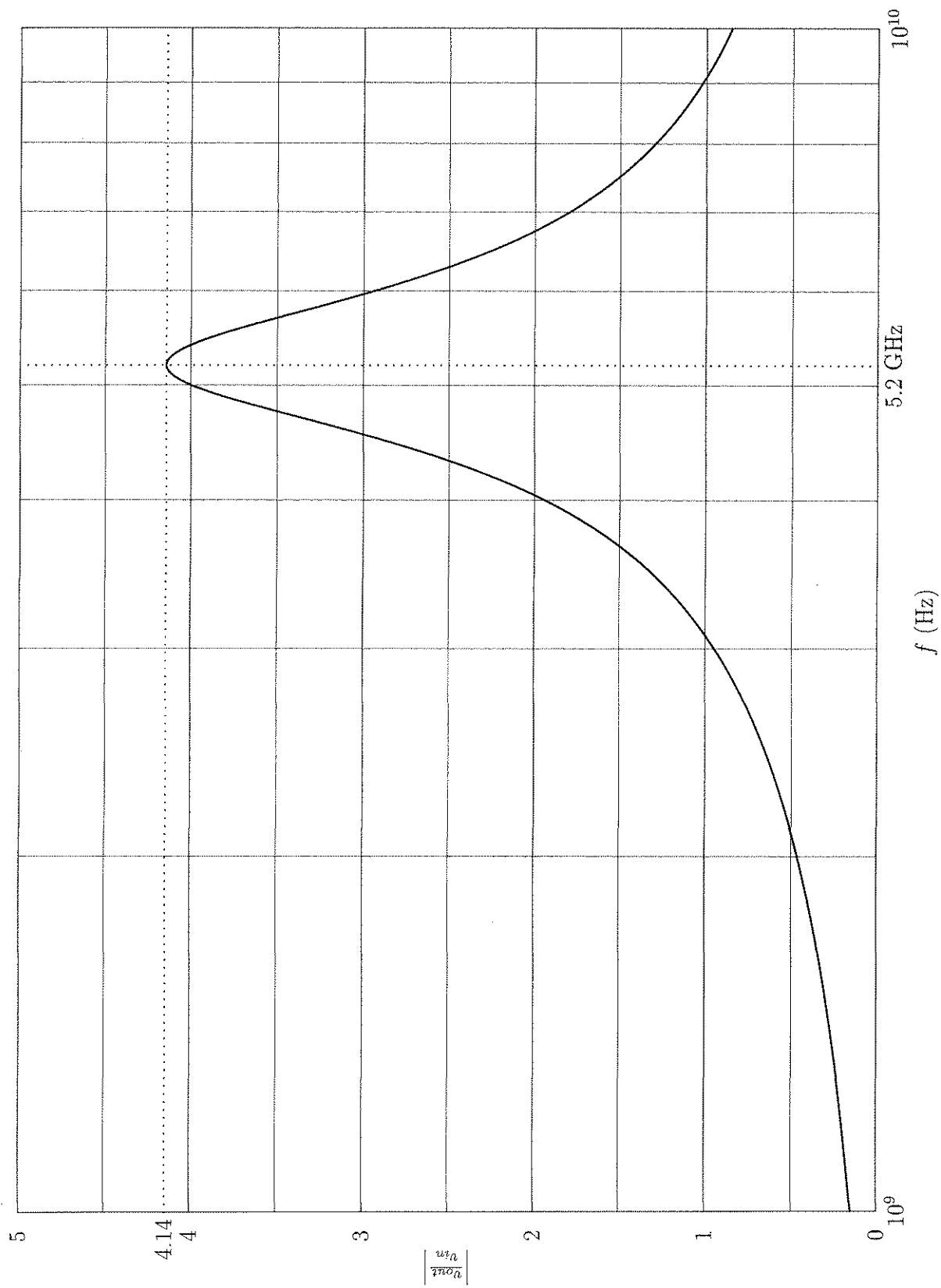


Figure 5: AC response of the second stage of the LNA showing resonance at 5.2 GHz

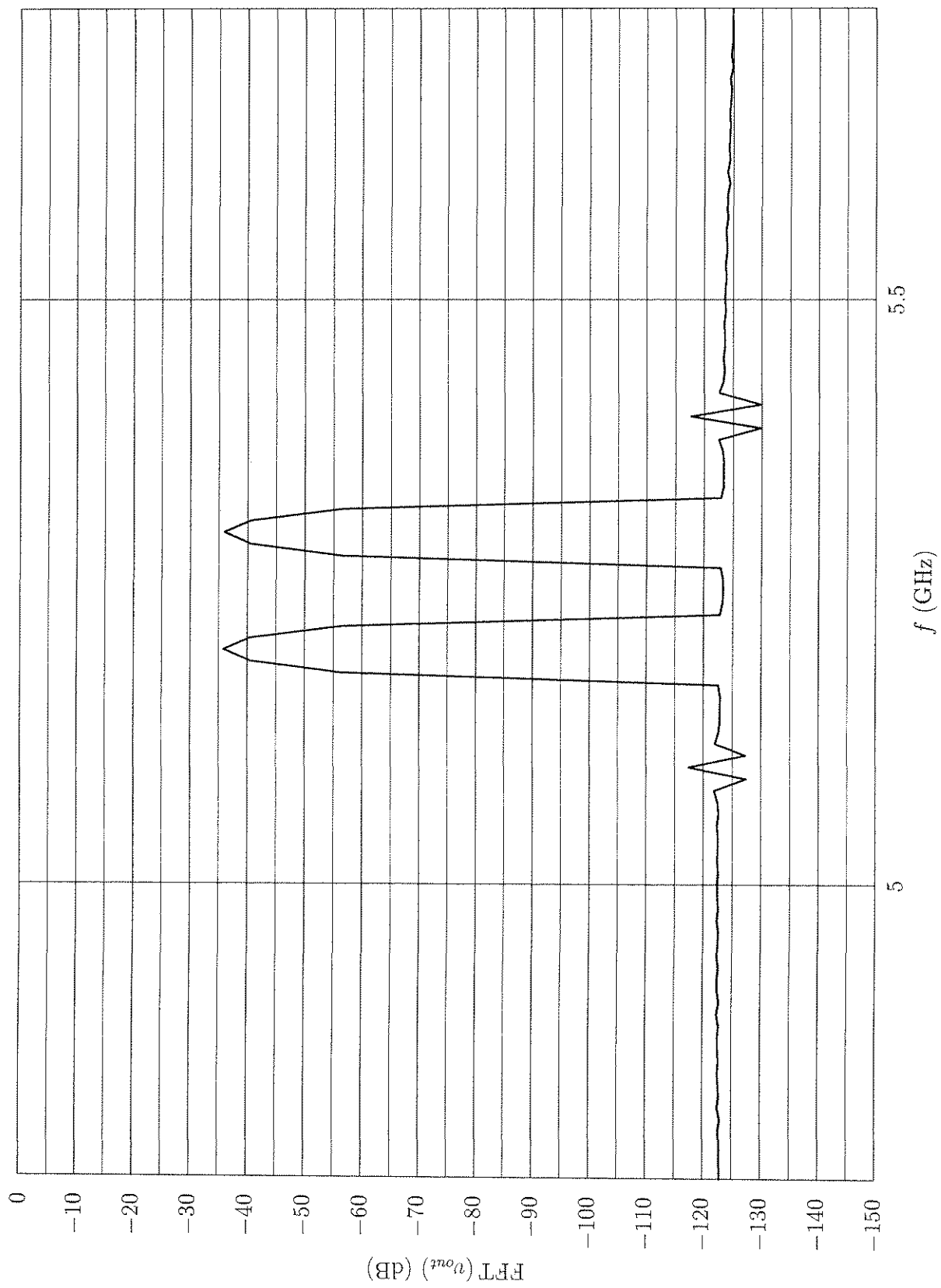


Figure 6: Output spectrum of the second stage of the LNA with a two-tone input

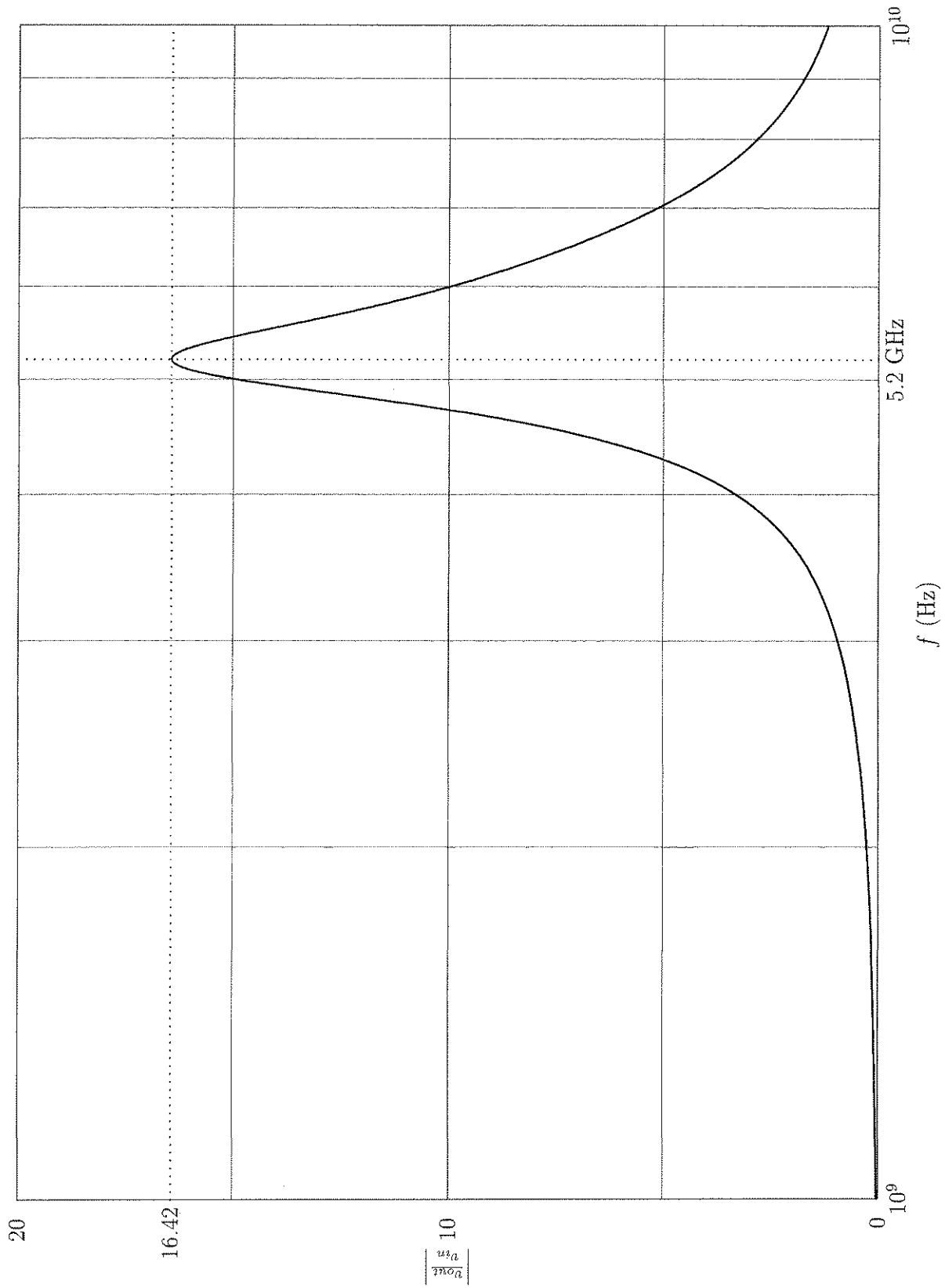


Figure 7: AC response of the overall LNA

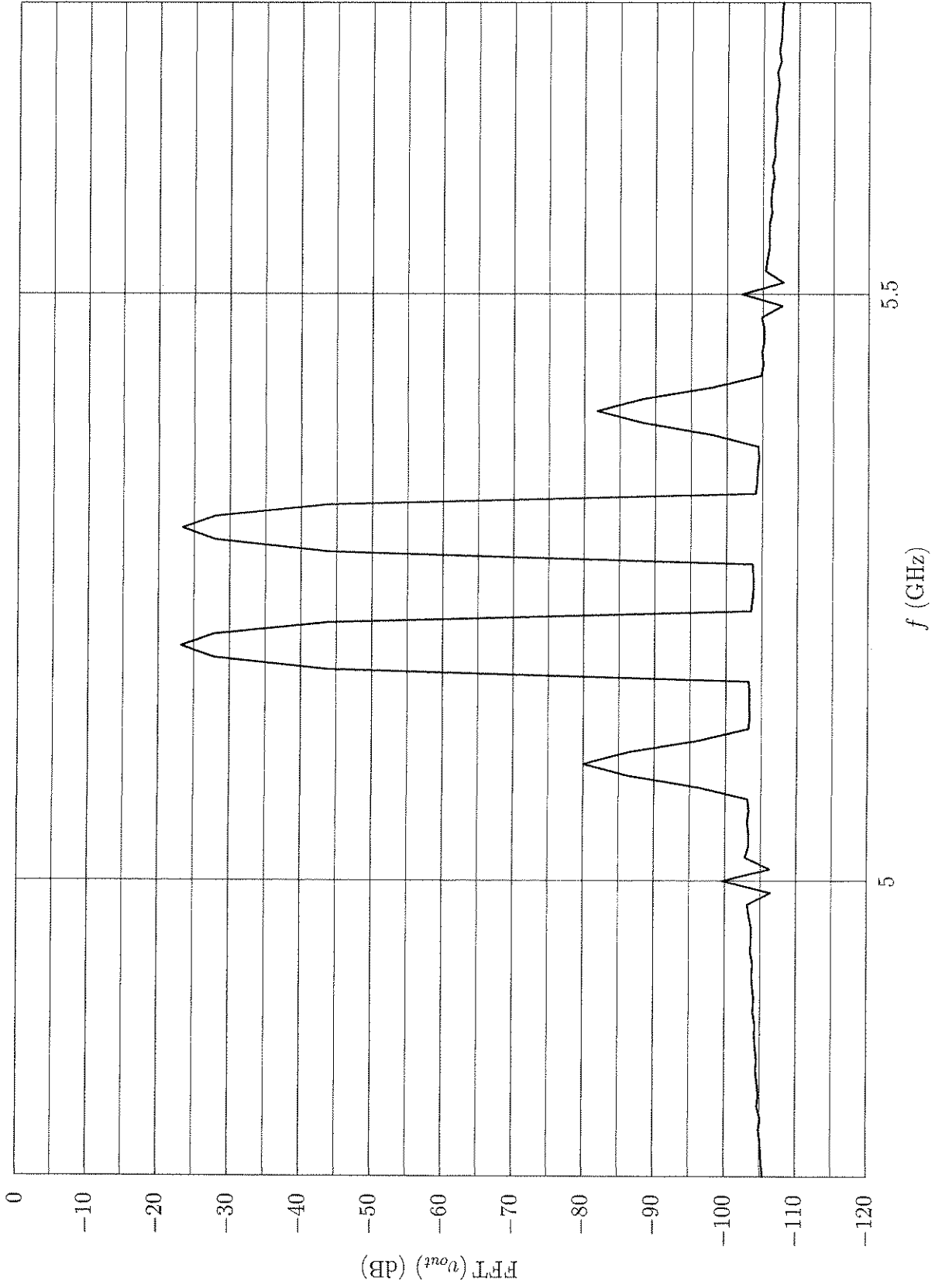


Figure 8: Output spectrum of the overall LNA with a two-tone input

