

circuit is fully differential, so node X_1 can be treated as virtual ground. The half circuit is shown right.

$$\frac{V_{out}}{V_{in}} = g_{m1} \cdot (r_{o1} \parallel r_{o3} \parallel R_1)$$



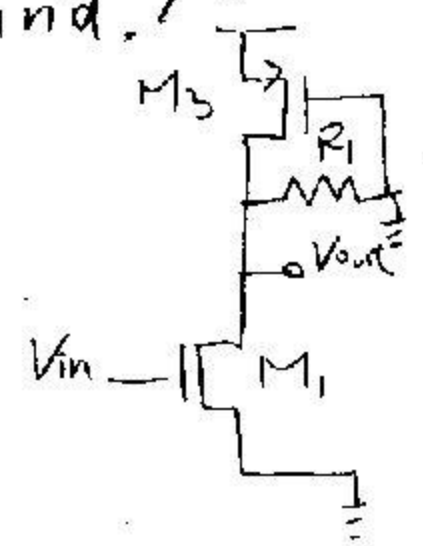


Fig 4.39 (c)

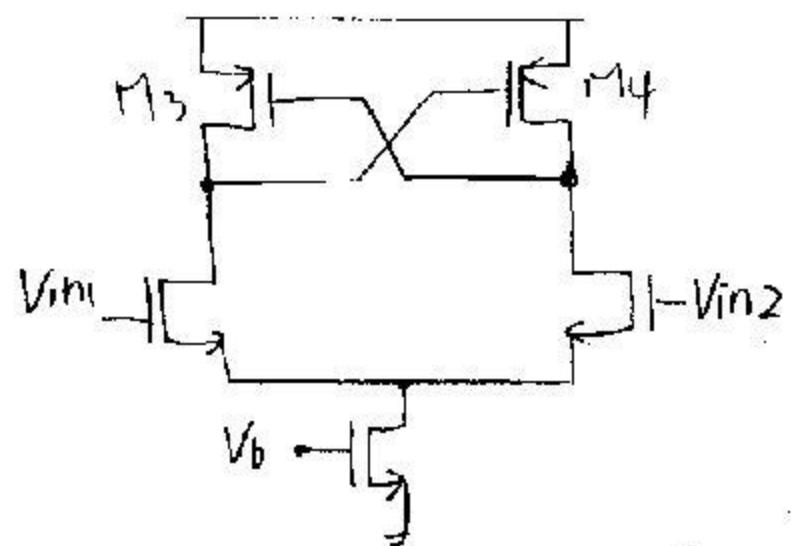

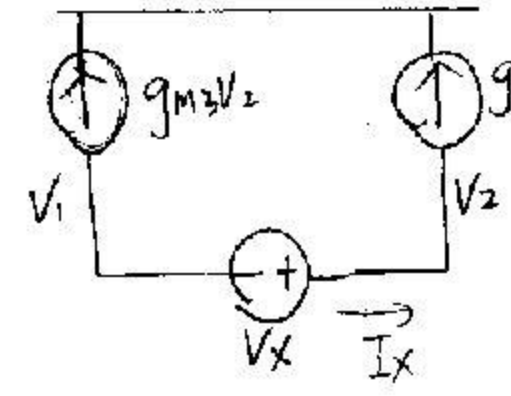M_3, M_4 is a cross-coupled load, and can be analyzed first with λ neglected first.




$$I_x = g_{m4} V_1$$

$$-I_x = g_{m3} V_2$$

assume $g_{m3} = g_{m4} = g_{m3,4}$

$$\frac{V_x}{I_x} = \frac{V_2 - V_1}{I_x} = \frac{-\frac{I_x}{g_{m3}} - \frac{I_x}{g_{m4}}}{I_x} = -\frac{2}{g_{m3,4}}$$

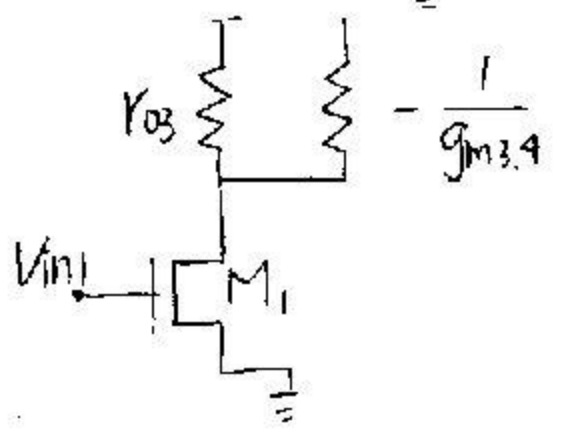Then we can separate the cross-coupled load into half circuit. The overall half circuit is shown left.




$$A_v = \frac{V_{out}}{V_{in}} = g_{m1} \times \left[r_{o1} \parallel r_{o3} \parallel \left(-\frac{1}{g_{m3,4}} \right) \right]$$

$$= -g_{m1} \times \frac{1}{r_{o1}^{-1} + r_{o3}^{-1} - g_{m3,4}}$$

Here the cross-coupled structure induce a negative resistance, $-\frac{1}{g_{m3,4}}$ which must be smaller than $\frac{1}{r_{o1}} + \frac{1}{r_{o3}}$ in order not to induce a positive feedback and instability.

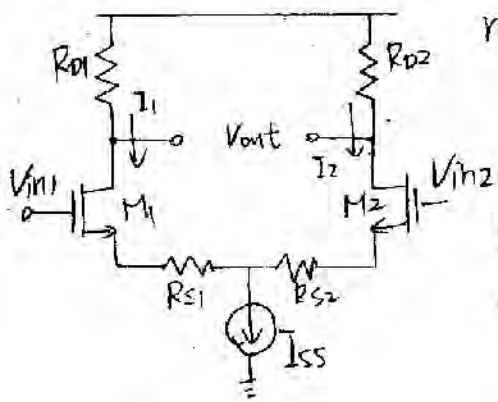4.21

If no symmetry is assumed, half circuit is not valid, therefore we can use superposition to calculate the impact of input on each output.




First calculate V_{in1} and let $V_{in2} = 0$, the circuit can be expressed as figure (a)

$$R_{sx} = R_{s1} + R_{s2} + \frac{1}{g_{m2} + g_{mb2}}$$

Therefore R_{D1} , M_1 , R_{sx} form a CS with source degeneration.

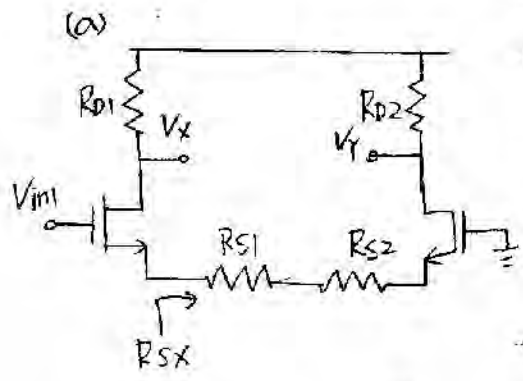
$$\frac{V_x}{V_{in1}} = \frac{g_{m1} \cdot R_{D1}}{1 + (g_{m1} + g_{mb1}) R_{sx}}$$



To calculate the contribution of V_{in1} to V_y , the circuit can be re-drawn through Thevenin equivalent circuit as figure (b), where

$$V_{TH} = V_{in1}, R_{TH} = \frac{1}{g_{m1} + g_{mb1}}$$

The circuit is the same as CG amplifier

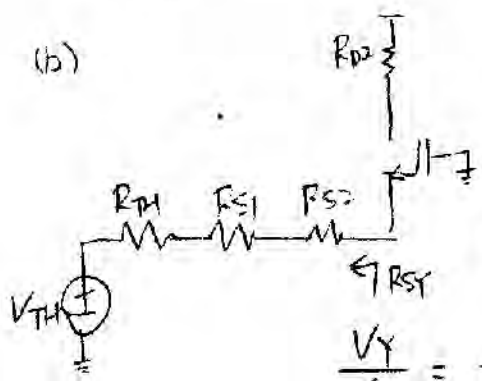

$$\frac{V_y}{V_{in1}} = \frac{R_{D2}}{R_{SY} + \frac{1}{g_{m2} + g_{mb2}}} = \frac{(g_{m2} + g_{mb2}) R_{D2}}{1 + (g_{m2} + g_{mb2}) R_{SY}} \quad R_{SY} = \frac{1}{g_{m1} + g_{mb1}} + R_{S1} + R_{S2}$$

$$\therefore (V_x - V_y) \text{ due to } V_{in1} = \left[\frac{g_{m1} R_{D1}}{1 + (g_{m1} + g_{mb1}) R_{sx}} - \frac{(g_{m2} + g_{mb2}) R_{D2}}{1 + (g_{m2} + g_{mb2}) R_{SY}} \right] \cdot V_{in1} \quad (1)$$


$$\text{Similarly, } (V_x - V_y) \text{ due to } V_{in2} = \left[- \frac{g_{m2} R_{D2}}{1 + (g_{m2} + g_{mb2}) R_{SY}} + \frac{(g_{m1} + g_{mb1}) R_{D1}}{1 + (g_{m1} + g_{mb1}) R_{sx}} \right] \cdot V_{in2} \quad (2)$$

$$V_{out} = V_x - V_y = (1) + (2)$$

(0)

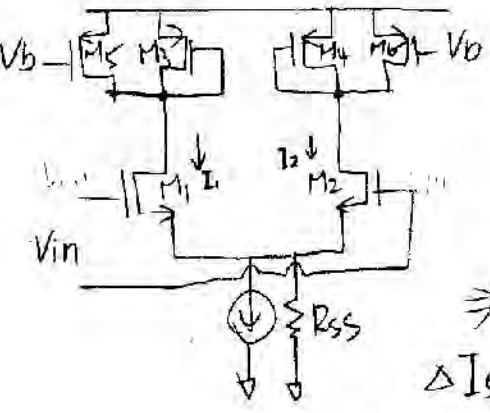4.26

assume $\lambda = 0 \Rightarrow R_{D3} = \frac{1}{g_{m3}}$



The mismatch of threshold voltage between M5, M6 will cause a ΔI between I_5 and I_6 .

However, $I_5 + I_3 = \frac{1}{2} I_{SS} = I_4 + I_6$

$\Rightarrow \Delta I_5 + \Delta I_3 = 0 \Rightarrow \Delta I_5 = -\Delta I_3$

$$\Delta I_5 = \frac{\partial I_5}{\partial V_{TH}} \cdot \Delta V_{TH} = -\mu_p C_{ox} \left(\frac{W}{L}\right)_5 (V_{GS} - V_{TH}) \cdot \Delta V_{TH}$$

$$= -2 I_{D5} \frac{\Delta V_{TH}}{V_{DD} - V_b - |V_{TH,P}|} \Rightarrow \Delta I_3 = 2 I_{D5} \frac{\Delta V_{TH}}{V_{DD} - V_b - |V_{TH,P}|}$$

$$\Delta g_{m3} = \frac{\partial g_{m3}}{\partial I_{D3}} \cdot \Delta I_3$$

$$= \sqrt{\frac{\mu_p C_{ox} (W/L)_3}{2 I_{D3}}} \times \Delta I_3 \Rightarrow \frac{\Delta g_{m3}}{g_{m3}} = \frac{\Delta I_3}{2 I_3} = \frac{I_5}{I_3} \times \frac{\Delta V_{TH}}{V_{DD} - V_b - |V_{TH,P}|} = 4 \frac{\Delta V_{TH}}{V_{DD} - V_b - |V_{TH,P}|}$$
 (1)

$$A_{CM \rightarrow DM} = -\frac{g_{m1}}{1 + g_{m1} \cdot 2R_{SS}} \times \Delta R_D, \quad A_{DM \rightarrow DM} = -g_{m1} R_D$$

$$\Rightarrow CMRR = \frac{A_{DM \rightarrow DM}}{A_{CM \rightarrow DM}} = \frac{1 + g_{m1} \cdot 2R_{SS}}{\frac{\Delta R_D}{R_D}} \quad (2)$$


$$R_D = \frac{1}{g_{m3}}, \quad \Delta R_D = \frac{\partial R_D}{\partial g_{m3}} \cdot \Delta g_{m3} = -\frac{1}{g_{m3}^2} \Delta g_{m3} \Rightarrow \frac{\Delta R_D}{R_D} = -\frac{1}{g_{m3}} \Delta g_{m3}$$
 (3)

Substitute $\frac{\Delta R_D}{R_D}$ in (2) with (1) and (3), and neglect the minus sign,

$$CMRR = \frac{1 + g_{m1} \cdot 2R_{SS}}{4 \frac{\Delta V_{TH}}{V_{DD} - V_b - |V_{TH,P}|}}$$

10

5.10 (a)

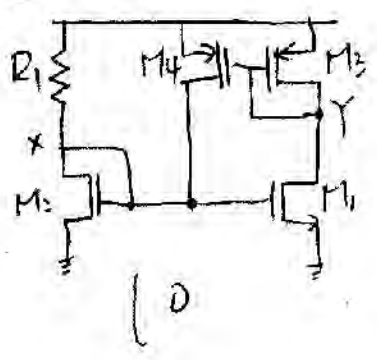


When $V_{DD} < V_{TH1,2}$, all transistors are off, and $V_x = V_{DD}$, $V_y = \text{floating}$

When $V_{DD} = V_{TH1,2}$, M_2 just turns on and hence M_1 . Assume $V_{TH3,4} = V_{TH1,2}$ then M_3 also turns on and hence M_4 . M_1, M_4 are in deep triode regions. In the meanwhile, $V_x = V_{DD} = V_{TH1,2}$, $V_y = V_{DD} - V_{TH3} = 0$


When $V_{DD} > V_{TH1,2}$, $V_x = V_{gs2}$, $V_y = V_{DD} - V_{gs3}$
 $V_x - V_y = V_{gs2} - V_{DD} + V_{gs3} \quad \text{--- (1)}$

(1) $> V_{TH}$ so both $|V_{gs}|$ of M_1, M_4 is larger than V_{TH} , $\Rightarrow M_1, M_4$ is kept in triode region.

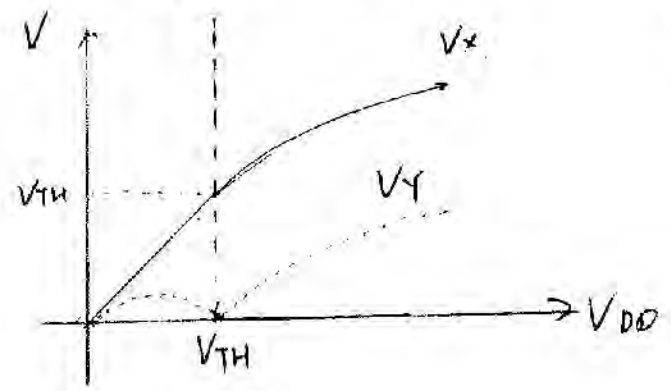
When V_{DD} increases further, M_4 never enters saturation, because if it is the case, I_D will inject M_2 and mirror more current back to itself, raising V_x and lowering V_y until M_4 conduct less current than M_2 . Therefore, M_4 is always in triode region, $V_x - V_y > V_{TH}$, and so is M_1 . The V_x, V_y vs V_{DD} plot is as follows.



5.12 (b)

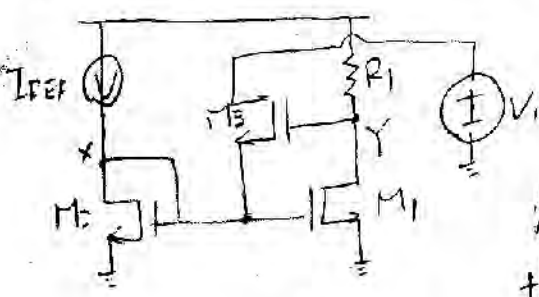


Co

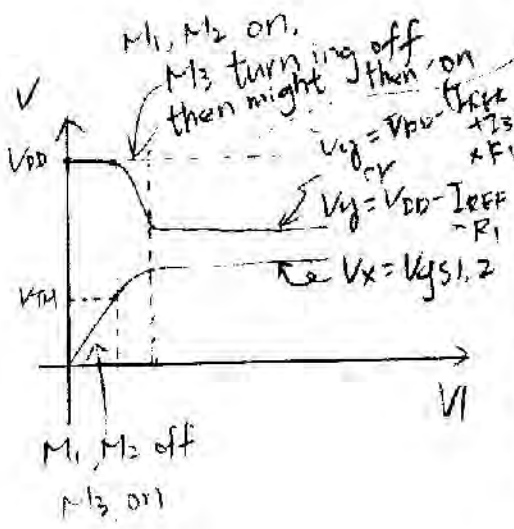

When $V_i = 0$, S/D of M_3 swap, some current might flow out through M_3 to V_i , therefore, $I_{M1} = I_{M2} < I_{REF}$. However, it is possible that M_3 sinks all the I_{REF} and make $I_{M2} = I_{M1} = 0$. Assume it is the case, then $V_Y = V_{DD}$, $V_X = V_i + V_{DS3}$. When $V_i \uparrow$, V_X also increases, but M_2, M_1 remain off until V_X reaches V_{TH} . In the meanwhile V_{GS3} decreases, so V_{DS3} increases to conduct the same current. Therefore V_X increases faster than V_i . When V_X reaches V_{TH} , M_1, M_2 starts to turn on. $V_Y = V_{DD} - I_{M1} R_1$, so V_Y starts to drop. When V_i keeps increasing, $V_{GS} = V_Y - V_i$ shrinks sharply and may finally get M_3 turned-off.

After M_3 turns off, increasing V_i will not affect I_{M1}, I_{M2} , so V_X, V_Y keep constant. However, it is also possible that $V_i > V_X$ before making M_3 off, then enters a stable state with conducting some current. Then $I_{M1} = I_{M2} = I_{REF} + I_3$,
 $V_Y = V_{DD} - R_1 (I_{REF} + I_3)$

5.19

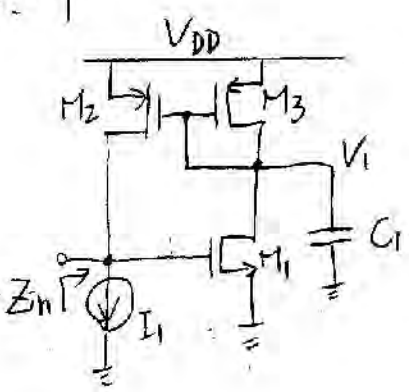


The small-signal model is drawn below assuming $\lambda=0$

$$I_{in} = g_{m2} V_1, \quad V_1 = -g_{m1} V_{in} \times \frac{1}{g_{m3} \parallel \frac{1}{sC_1}}$$

$$= -g_{m1} V_{in} \times \frac{1}{g_{m3} + sC_1}$$
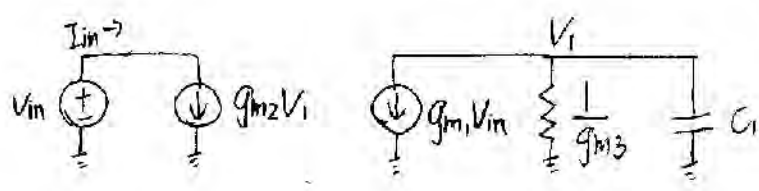
$$\Rightarrow I_{in} = g_{m2} \times (-g_{m1} V_{in}) \times \frac{1}{g_{m3} + sC_1}$$




$$\Rightarrow Z_{in} = \frac{V_{in}}{I_{in}} = \frac{-(g_{m3} + sC_1)}{g_{m1} g_{m2}}$$

$$= -\frac{g_{m3}}{g_{m1} g_{m2}} - \frac{sC_1}{g_{m1} g_{m2}}$$

negative $R = -\frac{g_{m3}}{g_{m1} g_{m2}}$, negative $= -\frac{sC_1}{g_{m1} g_{m2}}$

5.20(b)

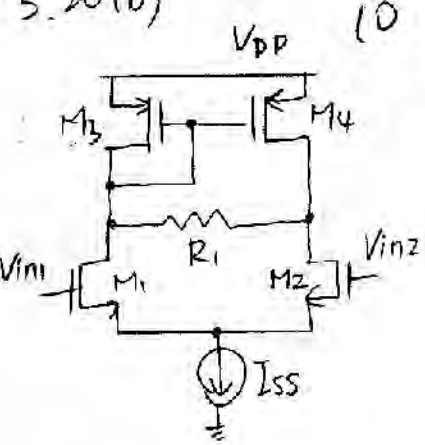

First we can treat M_1, M_2, I_{ss} as a one-port network and replace it with Thevenin equivalent circuit.

$$V_{eq1} = g_{m1,2} r_{o1,2} V_{in}, \quad R_{eq1} = 2r_{o1,2}$$




Combine R_1 with V_{eq1} and R_{eq1} , a second Thevenin can be derived, too.

equivalent circuit

$$V_{eq2} = \frac{R_1}{R_{eq1} + R_1} \times V_{eq1} = \frac{R_1}{R_{eq1} + R_1} \times g_{m1,2} r_{o1,2} V_{in}$$

$$R_{eq2} = R_{eq1} \parallel R_1 = 2r_{o1,2} \parallel R_1$$

The overall circuit is shown below

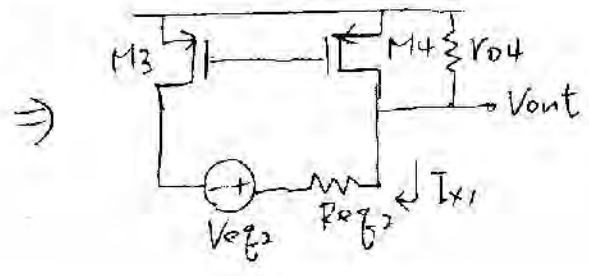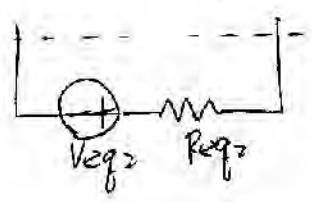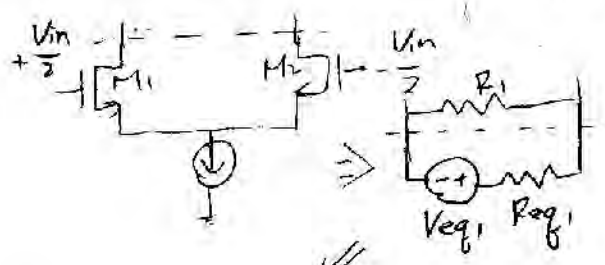

$$I_x = \frac{V_o - V_{eq2}}{R_{eq2} + \frac{1}{g_{m3}} \parallel r_{o3}} \quad \text{Since } I_x \text{ is mirrored into } M_4, \text{ we have}$$

$$2 \frac{V_{out} - V_{eq2}}{R_{eq2} + \frac{1}{g_{m3}} \parallel r_{o3}} \times \frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}} = \frac{-V_{out}}{r_{o4}} \quad \text{--- "}$$

$$\text{Assume } r_{o3} \gg \frac{1}{g_{m3}} \Rightarrow \frac{1}{g_{m3}} \parallel r_{o3} \approx \frac{1}{g_{m3}}$$

$$\text{Assume } R_{eq2} \gg \frac{1}{g_{m3}}$$

$$1) \Rightarrow 2 \frac{V_{out} - V_{eq2}}{R_{eq2}} = \frac{-V_{out}}{r_{o4}}$$

$$\Rightarrow V_{out} (2r_{o4} + R_{eq2}) = 2r_{o4} V_{eq2}$$

$$\Rightarrow V_{out} = \frac{2r_{o4} V_{eq2}}{2r_{o4} + R_{eq2}}$$

$$= \frac{2r_{o4}}{2r_{o4} + 2r_{o1,2} \parallel R_1} \times \frac{R_1}{2r_{o1,2} + R_1} \times g_{m1,2} r_{o1,2} V_{in}$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{2r_{o4} R_1 g_{m1,2} r_{o1,2}}{(2r_{o4} + 2r_{o1,2} \parallel R_1)(2r_{o1,2} + R_1)}$$