

EE 215A
Fall 2011

50/50
+ 70/70
120/120.

Analog Integrated Circuit Design

Homework #2.

Date: 2011.10.12.

UID: 904037458

Name: Yoonho Song

(10)

2.6 In saturated device,

$$r_o = \frac{H \lambda V_{DS}}{\lambda I_D}$$

(a) Intrinsic gain $|A_v| = g_m r_o = \frac{2I_D}{(V_{DS} - V_{TH})} \cdot \frac{1}{\lambda I_D} = \frac{2}{V_{DS} - V_{TH}} \cdot \frac{1}{\lambda}$


(5)

where λ is function of L

Under Drain current (I_D) is constant,

~~When λ is constant \rightarrow h is constant~~

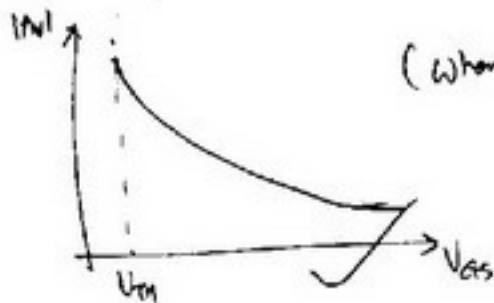(When λ is constant \rightarrow h is constant)



(b)


Intrinsic gain $|A_v| = g_m r_o = \mu_n C_{ox} \frac{W}{L} (V_{DS} - V_{TH}) \cdot \frac{1}{\lambda I_D}$

(5)

$$= \mu_n \left(\propto \frac{W}{L} (V_{DS} - V_{TH}) \right) \cdot \frac{1}{\lambda \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DS} - V_{TH})^2}}$$

$W \& L = \text{const}$
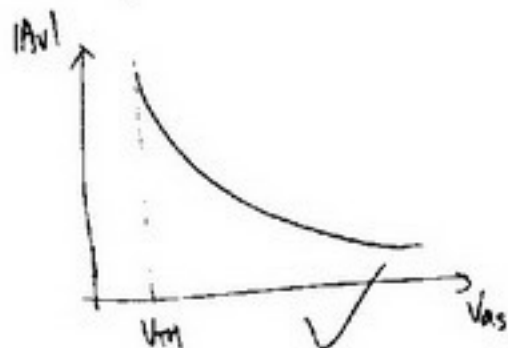
$$= \frac{2}{\lambda (V_{DS} - V_{TH})} \quad (\lambda \text{ is function of } L)$$




3.7 (a)

Intrinsic gain of saturated devices vs W/L

(a) $V_{GS} = \text{const.}$

(3) $|A_v| = g_m r_o = \frac{2}{(V_{GS} - V_{TH}) \cdot \lambda}$


~~_____~~
 λ is function of L

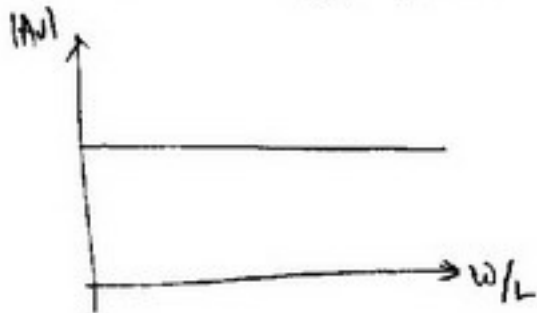

when λ is constant.

(b) $I_D = \text{const}$

(3) $|A_v| = g_m r_o = \sqrt{2 \mu_n C_{ox} \frac{W}{L} \cdot I_D} \cdot \frac{1}{\lambda I_D}$
 $= \frac{\sqrt{2 \mu_n C_{ox} \frac{W}{L}}}{\lambda \sqrt{I_D}} = \frac{\sqrt{2 \mu_n C_{ox}}}{\lambda \sqrt{I_D}} \cdot \sqrt{W/L}$, λ is function of L

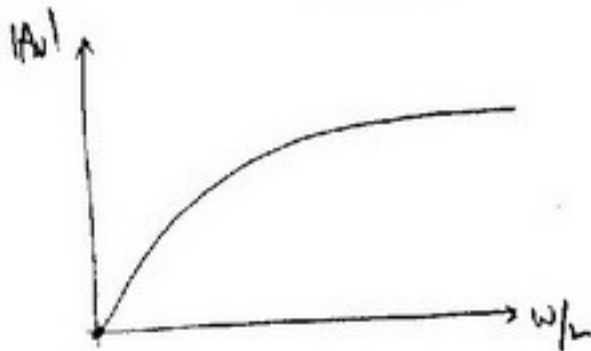

when λ is constant

29 Sum. no. g_{m0} in saturated device (NMOS)


① $g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$

(10) $V_{TH} = V_{TH0} + \gamma (\sqrt{|2\Phi_F + V_{GS}|} - \sqrt{|2\Phi_F|})$

Let's assume $V_S = 0$.

$V_B = 0 \rightarrow V_{GB} = 0 : V_{TH} = V_{TH0}$

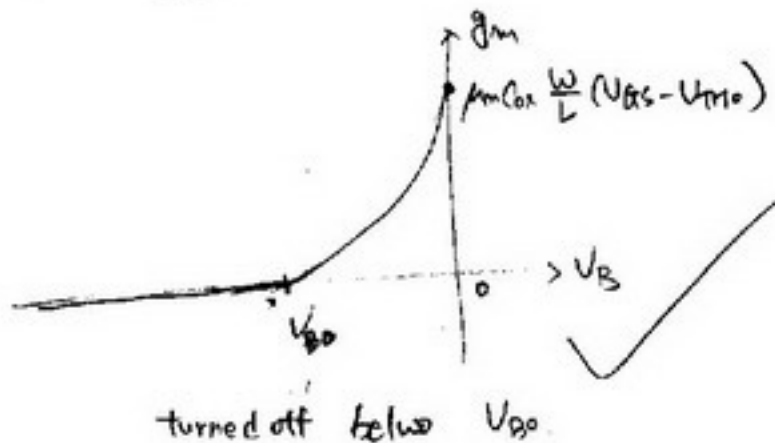$V_B = -\infty \rightarrow V_{GB} = \infty : V_{TH} = \infty$



$V_{BO} : V_{GS} = V_{TH}$
 $= V_{TH0} + \gamma (\sqrt{|2\Phi_F - V_{BO}|} - \sqrt{|2\Phi_F|})$


$\Rightarrow \frac{(V_{GS} - V_{TH0})}{\gamma} + \sqrt{|2\Phi_F|} = \sqrt{|2\Phi_F - V_{BO}|}$

$\therefore V_{BO} = 2\Phi_F - \left(\frac{(V_{GS} - V_{TH0})}{\gamma} + \sqrt{|2\Phi_F|} \right)^2$

② r_D


$r_D = \frac{1}{\lambda I_D} = \frac{1}{\lambda \cdot \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2} = \frac{2 \mu_n C_{ox} \frac{W}{L}}{\lambda \cdot g_m^2}$

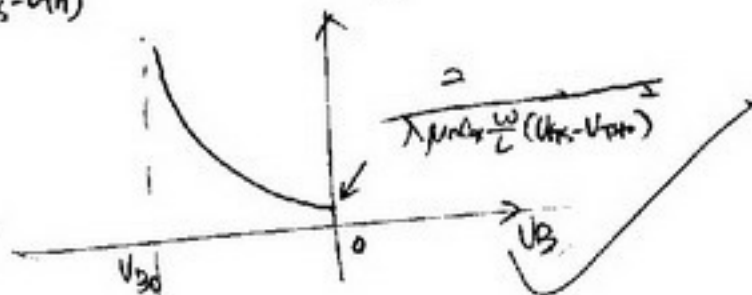$V_S = 0 : \dots$
 $r_D = \frac{2}{\lambda \cdot \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2}$




3.9 - cont'd

③ g_{m0}

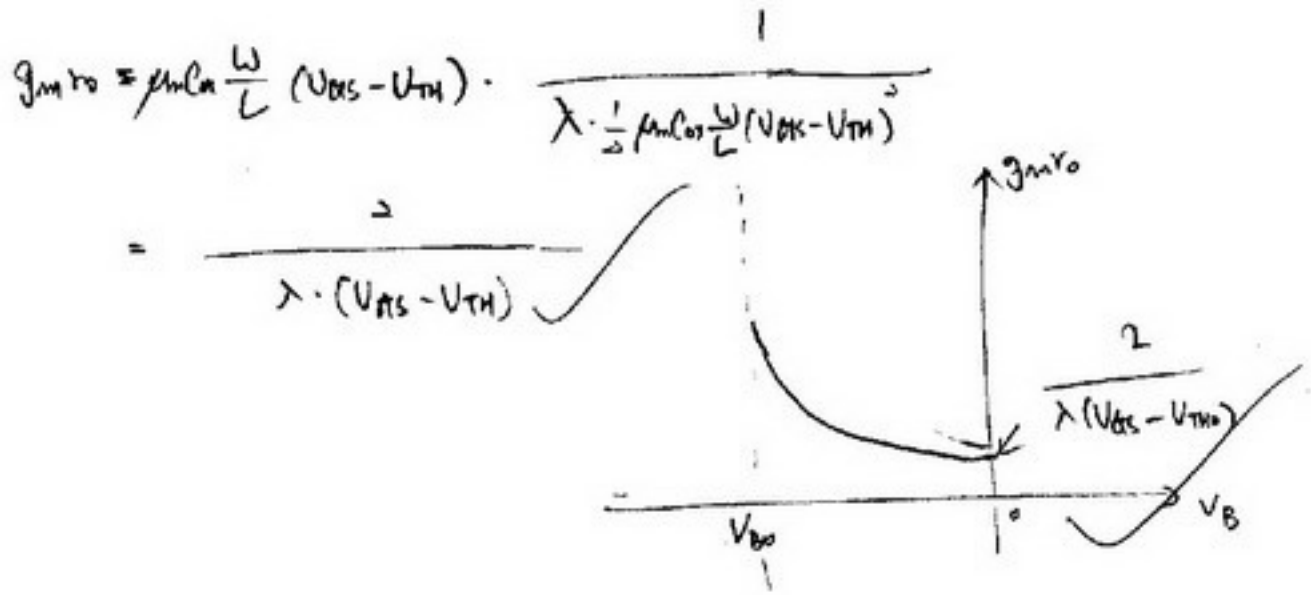

3.16 (a) V_{out} vs. V_{in} , $V_{in}: 0 \rightarrow V_{DD}$

(10)

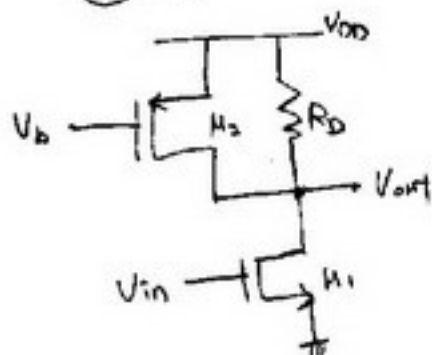

- i) $V_{in} < V_{TH1}$: M_1 off, $V_{out} = V_{DD}$
- ii) $V_{TH1} \leq V_{in} < V_1$: M_1 saturation, M_2 triode
- iii) $V_1 \leq V_{in} < V_2$: M_1 saturation, M_2 saturation
- iv) $V_2 \leq V_{in} \leq V_{DD}$: M_1 triode, M_2 saturation

• $V_{in} = V_1$,

M_2 enters in saturation region.

$$|V_{out} - V_{DD}| = |V_b - V_{DD}| - |V_{TH2}|$$

$$\rightarrow V_{DD} - V_{out} = V_{DD} - V_b - |V_{TH2}| \quad \therefore V_{out} = V_b + |V_{TH2}|$$

$$\rightarrow I_D = \frac{V_{DD} - V_{out}}{R_D} + \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_b - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_b - V_{TH1})^2$$

$$\therefore V_1 = V_{TH1} + \left\{ \left[\frac{V_{DD} + V_b + |V_{TH2}|}{R_D} + \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_b - |V_{TH2}|)^2 \right] \frac{2}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1} \right\}^{1/2}$$


• $V_{in} = V_2$

M_1 is in the edge of saturation region


$$V_{out} = V_{in} - V_{TH1} = V_2 - V_{TH1}$$

$$I_D = \frac{V_{DD} - (V_2 - V_{TH1})}{R_D} + \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_b - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_2 - V_{TH1})^2$$

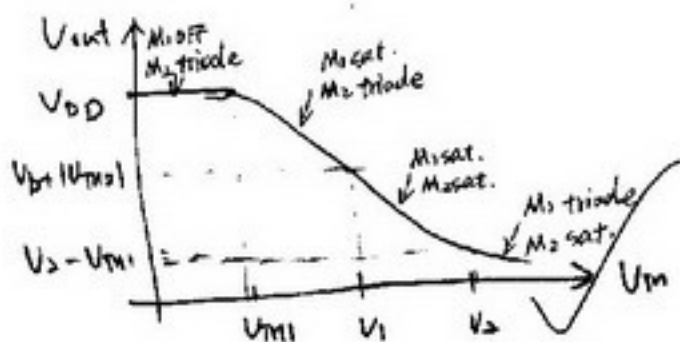$\therefore V_2$ value can be solved from the above equation



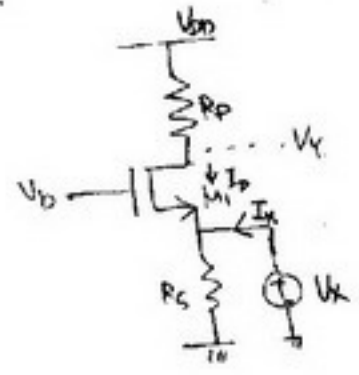3.18 (c) I_x vs V_x $V_x = 0 \rightarrow V_{DD}$



$$V_x = V_{DD} - I_D R_D = V_{DD} - \left(\frac{V_x}{R_S} - I_x \right) R_D$$

$$I_D = \frac{V_x}{R_S} - I_x \quad , \quad I_x = \frac{V_x}{R_S} - I_D$$

- i) $0 < V_x < V_1$: M_1 is in triode
- ii) $V_1 \leq V_x < V_2$: M_1 is in saturation and $I_x < 0$
- iii) $V_2 \leq V_x < V_{DD}$: M_1 is turned off and $I_x = \frac{V_x}{R_S}$


@ V_1 point.

$$V_x = V_b - V_{TH} \quad , \quad I_D = \frac{V_{DD} - (V_b - V_{TH})}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_1 - V_{TH})^2$$

$$V_1 = V_b - V_{TH} - \sqrt{\frac{2(V_{DD} - V_b + V_{TH})}{R_D \mu_n C_{ox} \frac{W}{L}}} \quad \text{If } V_1 < 0, M_1 \text{ won't be in triode.}$$

@ V_2 point.
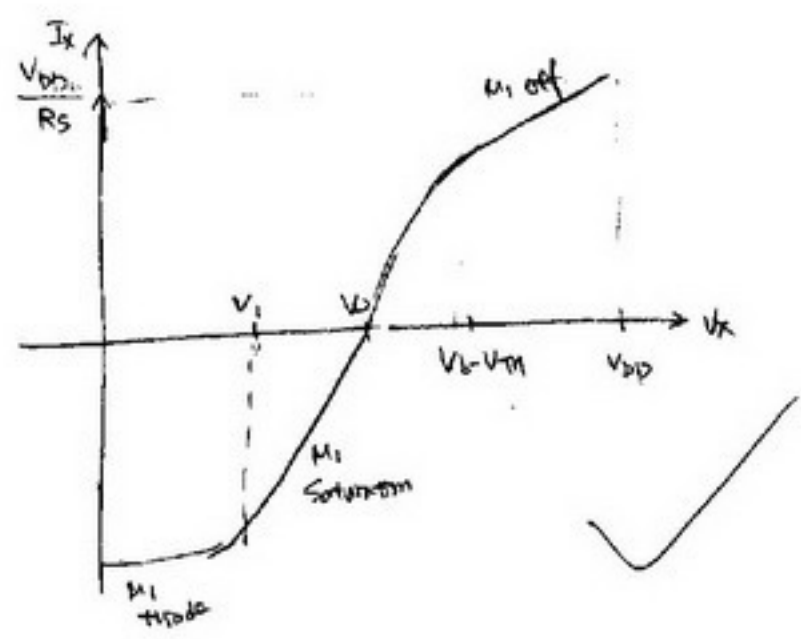
$$I_D = \frac{V_2}{R_S} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_2 - V_{TH})^2$$



3.19 (d)

10


I_x vs. V_x

$V_x: 0 \rightarrow V_{DD}$

M_1, M_2 are in saturation in all V_x

i) $0 \leq V_x < V_{THN}$, $I_N = 0$ ($\because M_1$ is off)

$$I_x = -I_P = -\frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_x - |U_{THP}|)^2$$

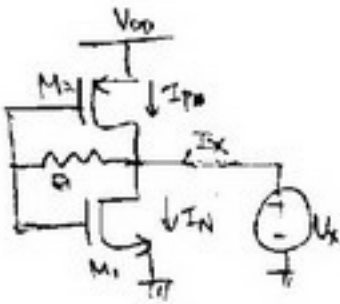

ii) $V_{THN} \leq V_x \leq V_{DD} - |U_{THP}|$

$$I_x = I_N - I_P$$

$$= \frac{1}{2} \mu_N C_{ox} \left(\frac{W}{L}\right)_1 (V_x - U_{THN})^2 - \frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_x - |U_{THP}|)^2$$

iii) $V_{DD} - |U_{THP}| < V_x \leq V_{DD}$

M_2 off: $I_P = 0$

$$I_x = I_N = \frac{1}{2} \mu_N C_{ox} \left(\frac{W}{L}\right)_1 (V_x - U_{THN})^2$$


@ $V_x = V_0$, $I_x = 0$ when $I_N = I_P$

$$\frac{1}{2} \mu_N C_{ox} \left(\frac{W}{L}\right)_1 (V_0 - U_{THN})^2 = \frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_0 - |U_{THP}|)^2$$

$$K_1 (V_0 - U_{THN})^2 = K_2 (V_{DD} - V_0 - |U_{THP}|)^2$$


$$V_0 (\sqrt{K_1} + \sqrt{K_2}) = U_{THN} \sqrt{K_1} + (V_{DD} - |U_{THP}|) \sqrt{K_2}$$

$$\therefore V_0 = \frac{\sqrt{K_1} \cdot U_{THN} + \sqrt{K_2} \cdot (V_{DD} - |U_{THP}|)}{\sqrt{K_1} + \sqrt{K_2}}$$

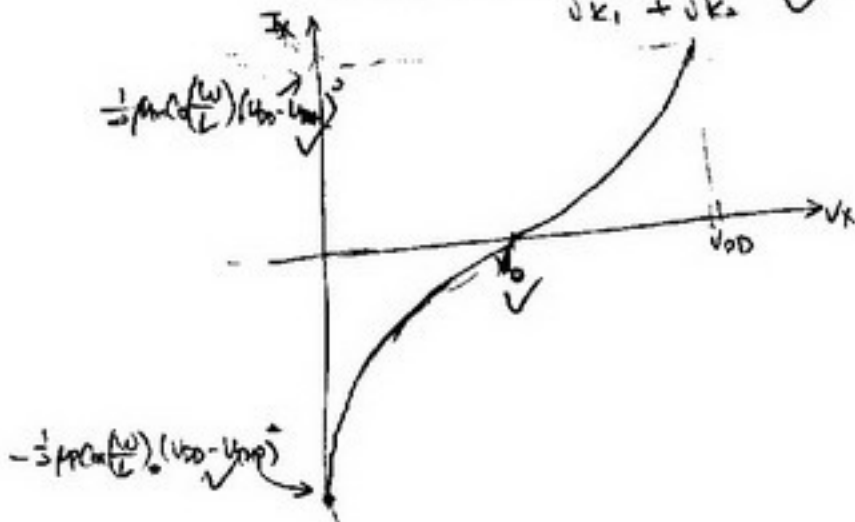


3.20 (b) all MOSFETs are in saturation. $\lambda \neq 0, \gamma = 0$

(10) Small signal voltage gain?

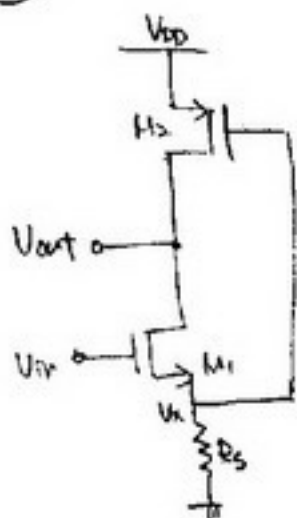

Small sig. equivalent ckt.

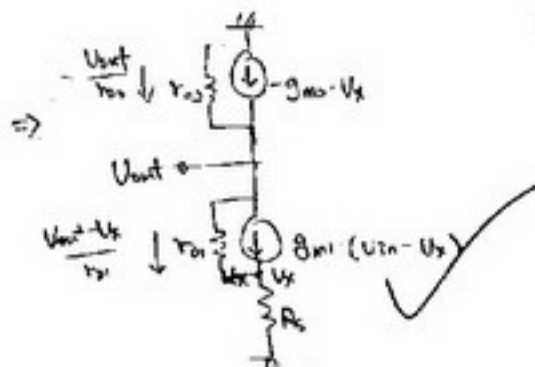

$$-g_{m2} \cdot V_x - \frac{V_{out}}{r_{o2}} = g_{m1} \cdot (V_{in} - V_x) + \frac{V_{out} - V_x}{r_{o1}} = \frac{V_x}{R_S} \quad (1)$$

$$V_x \left(\frac{1}{R_S} + g_{m2} \right) = -\frac{V_{out}}{r_{o2}} \quad (2) \quad \therefore V_x = -\frac{V_{out}}{r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)}$$

$$g_{m1} \cdot \left(V_{in} + \frac{V_{out}}{r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)} \right) + \frac{V_{out} + \frac{V_{out}}{r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)}}{r_{o1}} = -\frac{1}{R_S} \cdot \frac{V_{out}}{r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)}$$

$$V_{out} \left(\frac{g_{m1}}{r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)} \right) + V_{out} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o1} \cdot r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)} \right) + V_{out} \left(\frac{1}{R_S \cdot r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)} \right)$$


$$= -g_{m1} \cdot V_{in}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{-g_{m1}}{\frac{g_{m1}}{r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)} + \frac{1}{r_{o1}} + \frac{1}{r_{o1} \cdot r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)} + \frac{1}{R_S \cdot r_{o2} \left(\frac{1}{R_S} + g_{m2} \right)}}$$


$$= \frac{-g_{m1} \cdot r_{o2} \left(g_{m2} + \frac{1}{R_S} \right)}{g_{m1} + \frac{r_{o2}}{r_{o1}} \left(g_{m2} + \frac{1}{R_S} \right) + \frac{1}{r_{o1}} + \frac{1}{R_S}}$$

(10)

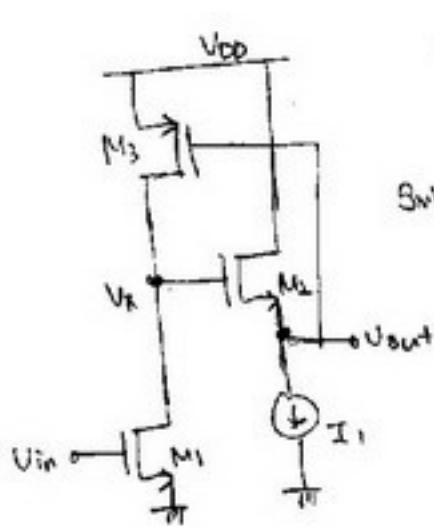3.21 (h) Assuming all MOSFETs are in saturation $\lambda \neq 0, \gamma = 0$
Find small signal gain.



Small sig. equivalent ckt

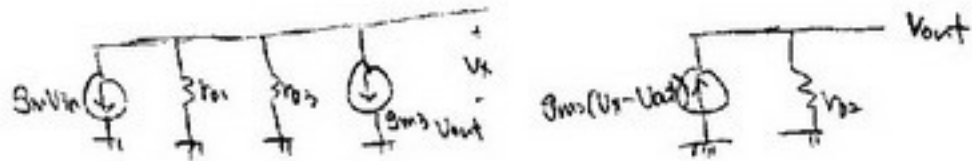

$$\begin{cases} V_x = -(g_{m1} V_{in} + g_{m3} V_{out}) \cdot (r_{O1} \parallel r_{O3}) \\ V_{out} = g_{m2} (V_x - V_{out}) \cdot r_{O2} \end{cases}$$

$$V_{out} = g_{m2} (-g_{m1} V_{in} + g_{m3} V_{out}) (r_{O1} \parallel r_{O3}) r_{O2} - g_{m2} \cdot V_{out} \cdot r_{O2}$$

$$V_{out} (1 + g_{m2} \cdot g_{m3} \cdot r_{O2} (r_{O1} \parallel r_{O3}) + g_{m2} \cdot r_{O2}) = -g_{m1} \cdot g_{m2} \cdot (r_{O1} \parallel r_{O3}) r_{O2} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1} \cdot g_{m2} \cdot (r_{O1} \parallel r_{O3}) r_{O2}}{1 + g_{m2} \cdot r_{O2} + g_{m2} \cdot g_{m3} (r_{O1} \parallel r_{O3}) r_{O2}}$$


$$= \frac{-g_{m1} \cdot g_{m2} \cdot \frac{r_{O1} \cdot r_{O2} \cdot r_{O3}}{r_{O1} + r_{O3}}}{1 + g_{m2} r_{O2} + g_{m2} \cdot g_{m3} \cdot \frac{r_{O1} \cdot r_{O1} \cdot r_{O2}}{r_{O1} + r_{O3}}}$$

$$= \frac{-g_{m1} \cdot g_{m2} \cdot r_{O1} \cdot r_{O2} \cdot r_{O3}}{r_{O1} + r_{O3} + g_{m2} \cdot r_{O2} (r_{O1} + r_{O3}) + g_{m2} \cdot g_{m3} \cdot r_{O1} \cdot r_{O2} \cdot r_{O3}}$$

(10)

3.22(b)

V_x, V_y vs time. $V_{C1}(0) = V_{DD}$

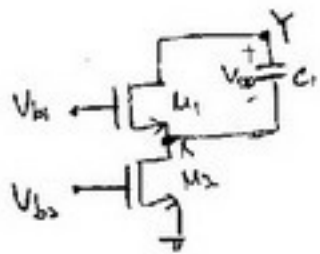

assume $V_x(0) = V_{DD}$, $V_y(0) = 0$

$$I_{D2}(0) = 0$$

$$I_{D1}(0) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{DD} - V_{TH})^2$$

When $V_x \uparrow \Rightarrow V_y \downarrow \Rightarrow I_{D2} \uparrow \rightarrow V_x \downarrow$: V_x returns to zero

: V_y goes from V_{DD} to zero

M_1 is saturated until $V_y = V_{DD} - V_{TH}$ ✓

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{DD} - V_{TH})^2$$

$$C_1 \Delta V = I_{D1} \Delta t \rightarrow C_1 \cdot (V_{DD} - (V_{DD} - V_{TH})) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{DD} - V_{TH})^2 \cdot \Delta t$$

$$\therefore \Delta t = \frac{C_1 \cdot (V_{DD} - V_{DD} + V_{TH})}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{DD} - V_{TH})^2} = t_1$$

after t_1 , M_1 enters to triode region

$$I_D = C \frac{dV_C}{dt} \rightarrow -C_1 \frac{dV_y}{dt} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[(V_{DD} - V_{TH}) V_y - V_y^2 \right]$$

$$\frac{dV_y}{(V_{DD} - V_{TH}) V_y - V_y^2} = - \frac{\mu_n C_{ox} \frac{W}{L}}{2 C_1} dt$$

$$\left[\frac{1}{V_y} + \frac{1}{(V_{DD} - V_{TH}) - V_y} \right] \cdot \frac{dV_y}{(V_{DD} - V_{TH})} = - \frac{\mu_n C_{ox} \frac{W}{L}}{\sqrt{2} C_1} dt$$

$$\int \Rightarrow \ln(V_y) - \ln[(V_{DD} - V_{TH}) - V_y] = - \frac{\mu_n C_{ox} \frac{W}{L}}{C_1} (V_{DD} - V_{TH}) t + K$$

at $t = t_1$, $V_y = V_{DD} - V_{TH}$


$$\ln(V_{DD} - V_{TH}) - \ln[(V_{DD} - V_{TH}) - (V_{DD} - V_{TH})] = - \frac{\mu_n C_{ox} \frac{W}{L}}{C_1} (V_{DD} - V_{TH}) t_1 + K$$

3.22 (b) cont'd

$$0 = -\frac{\mu(V_{DD} - V_b + V_{TH})}{(V_b - V_{TH})} + K$$

$$\therefore K = \frac{\mu(V_{DD} - V_b + V_{TH})}{V_b - V_{TH}}$$
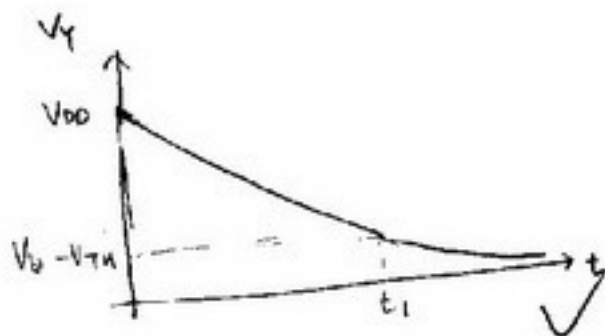
$$\therefore \ln \left[\frac{V_Y}{\mu(V_b - V_{TH}) - V_Y} \right] = -\frac{\mu C_{ox} \frac{W}{L}}{C_1} (V_b - V_{TH}) t + \frac{\mu(V_{DD} - V_b + V_{TH})}{V_b - V_{TH}}$$



2. $W/L = 20/0.18$ $V_{DD} = 1.8V$

(a) $V_{b1} = V_{DD} - |V_{DS1}| - |V_{GS2}|$

(5) $V_{b2} = V_{DS4} + V_{GS3}$

M1: $I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{GS1} - V_{THP1})^2$

$V_{DS1} = |V_{GS1}| - |V_{THP1}|$ at the edge of saturation

$\Rightarrow |V_{DS1}| = |V_{GS1}| - |V_{THP1}| = \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L}}}$

M2: $I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS2}| - |V_{THP1}|)^2$

$\Rightarrow |V_{GS2}| = |V_{THP1}| + \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L}}}$

$\therefore V_{b1} = V_{DD} - |V_{DS1}| - |V_{GS2}|$ ✓

$= V_{DD} - \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L}}} - |V_{THP1}| - \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L}}} = V_{DD} - |V_{THP1}| - 2 \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L}}}$

$= 0.793V$ ✓

M3: $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS3} - V_{THN})^2$

$\Rightarrow V_{GS3} = V_{THN} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}$

M4: $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS4} - V_{THN})^2$

$V_{GS4} - V_{THN} = V_{DS4}$ at the edge of saturation

$\Rightarrow V_{DS4} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}$

$\therefore V_{b2} = V_{DS4} + V_{GS3} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{THN} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = V_{THN} + 2 \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}$

$= 0.803V$

- (b) PMOS side
 $|V_{DS1}| \geq |V_{DS2}| - |V_{THP}|$

(B)
 $V_{out} \geq -V_{b1} - |V_{THP}|$

$$\therefore V_{out} \leq V_{b1} + |V_{THP}| = V_{DD} - |V_{THP}| - 2\sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + |V_{THP}| = V_{DD} - 2\sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 1.284V$$


• NMOS side

$$V_{out} \geq V_{b2} - V_{THN} = V_{THN} + 2\sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = V_{THN} \Rightarrow \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.312V$$

$$\therefore \text{Swing} = V_{DD} - 2\sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} - 2\sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.952V$$

(c) $\frac{V_{out}}{A} \approx -g_{m1} (r_{up} || r_{dn})$

(10)

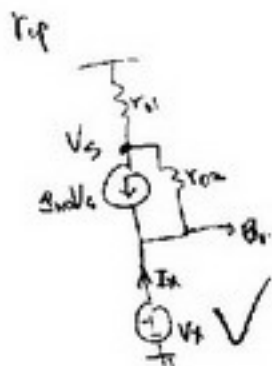

$$I_x = \frac{V_x}{r_{o1}} = \frac{V_x - V_s}{r_{o2}} - g_{m2} \cdot V_s$$


$$V_s = r_{o1} \cdot I_x$$

$$\therefore I_x = \frac{V_x - I_x \cdot r_{o1}}{r_{o2}} - g_{m2} \cdot I_x \cdot r_{o1}$$

$$I_x \left(1 + \frac{r_{o1}}{r_{o2}} + g_{m2} \cdot r_{o1}\right) = \frac{V_x}{r_{o2}}$$

$$\therefore \frac{V_x}{I_x} = r_{up} = r_{o1} + r_{o2} + g_{m2} \cdot r_{o1} \cdot r_{o2}$$

r_{dn}

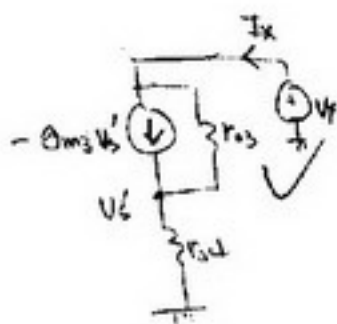

$$I_x = \frac{V_x}{r_{o3}} = \frac{V_x - V_{s'}}{r_{o4}} - g_{m3} \cdot V_{s'}$$

$$V_{s'} = I_x \cdot r_{o4}$$

$$I_x = \frac{V_x - I_x \cdot r_{o4}}{r_{o4}} - g_{m3} \cdot I_x \cdot r_{o4}$$


$$I_x \left(1 + \frac{r_{o4}}{r_{o2}} + g_{m3} \cdot r_{o4}\right) = \frac{V_x}{r_{o2}}$$

$$\therefore \frac{V_x}{I_x} = r_{dn} = r_{o2} + r_{o4} + g_{m3} \cdot r_{o2} \cdot r_{o4}$$

$$\frac{V_{out}}{A} \approx -g_{m1} \cdot \left[(r_{o1} + r_{o2} + g_{m3} \cdot r_{o1} \cdot r_{o2}) \parallel (r_{o3} + r_{o4} + g_{m3} \cdot r_{o3} \cdot r_{o4}) \right] = -g_{m1} \cdot R_o$$

$\frac{V_{out}}{V_{in}}$: closed loop

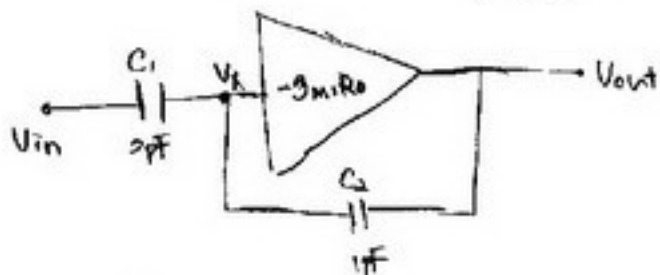(resistor can be viewed as open circuit in midband)



$$V_{out} = -g_{m1} \cdot R_o \cdot V_x$$

$$(V_{in} - V_x) \cdot C_1 = (V_x - V_{out}) \cdot C_2$$

$$V_x (sC_2 + sC_1) = V_{in} \cdot sC_1 + V_{out} \cdot sC_2 \quad \therefore V_x = \frac{C_1 \cdot V_{in} + C_2 \cdot V_{out}}{C_1 + C_2}$$

$$\Rightarrow V_{out} = -g_{m1} \cdot R_o \cdot \frac{C_1 \cdot V_{in} + C_2 \cdot V_{out}}{C_1 + C_2}$$

$$V_{out} \left(1 + \frac{g_{m1} \cdot R_o \cdot C_2}{C_1 + C_2} \right) = \frac{-g_{m1} \cdot R_o \cdot C_1}{C_1 + C_2} V_{in}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{-g_{m1} \cdot R_o \cdot C_1}{C_1 + g_{m1} \cdot R_o \cdot C_2} \approx \frac{-g_{m1} \cdot R_o \cdot C_1}{g_{m1} \cdot R_o \cdot C_2} = -\frac{C_1}{C_2} = -2$$

$$C_1 = 2\text{pF}, C_2 = 1\text{pF}$$

$$r_{o1} + r_{o2} + g_{m3} \cdot r_{o1} \cdot r_{o2} \approx g_{m3} \cdot r_{o1} \cdot r_{o2} = 157.6\text{k}$$

$$r_{o3} + r_{o4} + g_{m3} \cdot r_{o3} \cdot r_{o4} \approx g_{m3} \cdot r_{o3} \cdot r_{o4} = 188.8\text{k}$$

$$R_o = \frac{1}{\frac{1}{157.6\text{k}} + \frac{1}{188.8\text{k}}} = 86.9\text{k}\Omega$$

Coefficient Values.

$$I_D = 600 \mu A$$

Simul.

$$V_{THN0} = 0.743V, V_{THP0} = -0.418V \quad \gamma = 0 \quad \left| \quad V_{THN} = 0.471V, V_{THP} = -0.491$$

$$\mu_n = 310.24 \text{ cm}^2/\text{V}\cdot\text{sec}, \quad \mu_p = 128.28 \text{ cm}^2/\text{V}\cdot\text{sec}$$

$$t_{ox} = 4.1 \times 10^{-9} \text{ m}$$

$$C_{ox} = \frac{\epsilon_{SiO_2}}{t_{ox}} = \frac{3.9 \times 8.854 \times 10^{-12}}{4.1 \times 10^{-9}} = 8.422 \times 10^{-3} \text{ F/m}^2 = 0.8422 \mu \text{ A}\cdot\text{s}/\text{V}\cdot\text{cm}^2$$

$$\frac{W}{L} = \frac{30 \mu\text{m}}{0.18 \mu\text{m}}$$

$$V_{DD} = 1.8V$$

$$2 \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L}}} = 2 \sqrt{\frac{2 \times 600}{128.28 \times 8.422 \times \frac{30}{0.18}}} = 0.2582$$

$$g_{m1} = \sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D} = \sqrt{2 \times 128.28 \times 0.8422 \times \frac{30}{0.18} \times 600} = 5.684 \text{ mA/V}$$

$$g_{m3} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \times 310.24 \times 0.8422 \times \frac{30}{0.18} \times 600} = 7.229 \text{ mA/V}$$

@ 1.8V

$$\text{Let } r_{o1} = r_{o2} = 5.8 \text{ k}\Omega$$

$$r_{o3} = r_{o4} = 5.11 \text{ k}\Omega$$

$$g_{m1} \approx g_{m2}$$


$$g_{m3} \approx g_{m4}$$

at saturation region


$$r_{o1} + r_{o2} + g_{m1} \cdot r_{o1} \cdot r_{o2} \approx g_{m3} \cdot r_{o1} \cdot r_{o2} = 157.6 \text{ k}\Omega$$

$$r_{o3} + r_{o4} + g_{m3} \cdot r_{o3} \cdot r_{o4} \approx g_{m2} \cdot r_{o3} \cdot r_{o4} = 188.8 \text{ k}\Omega \quad \checkmark$$

10

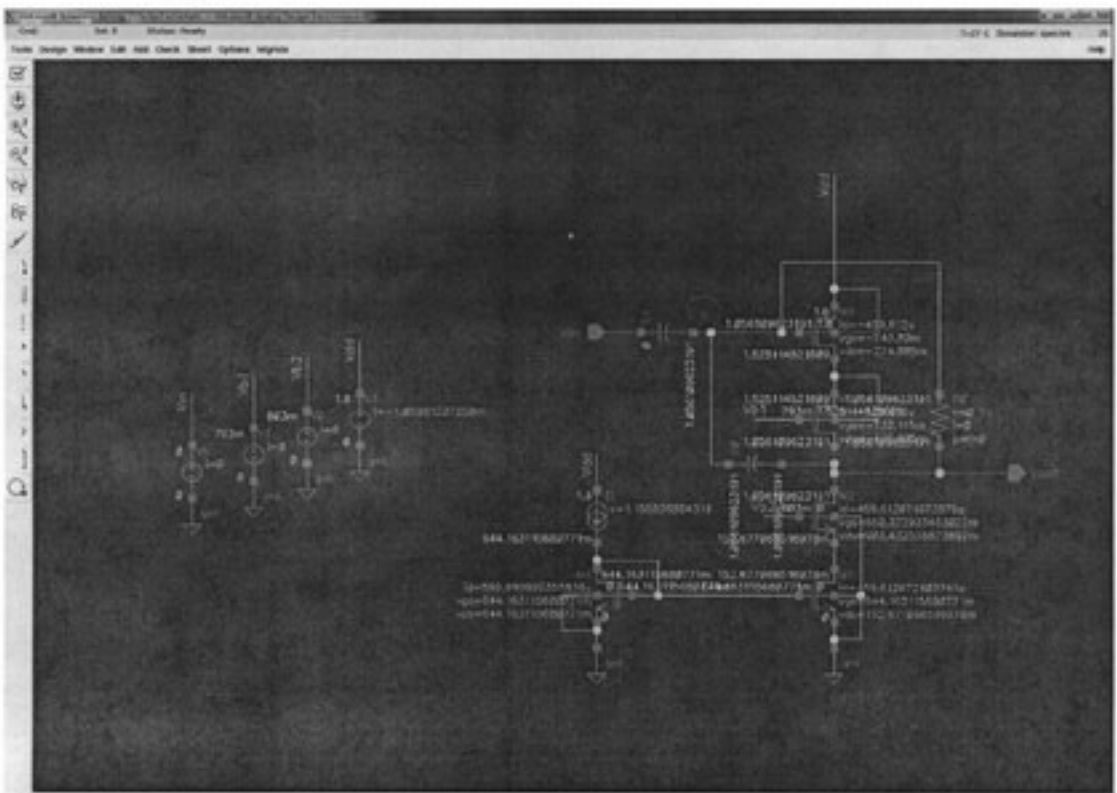

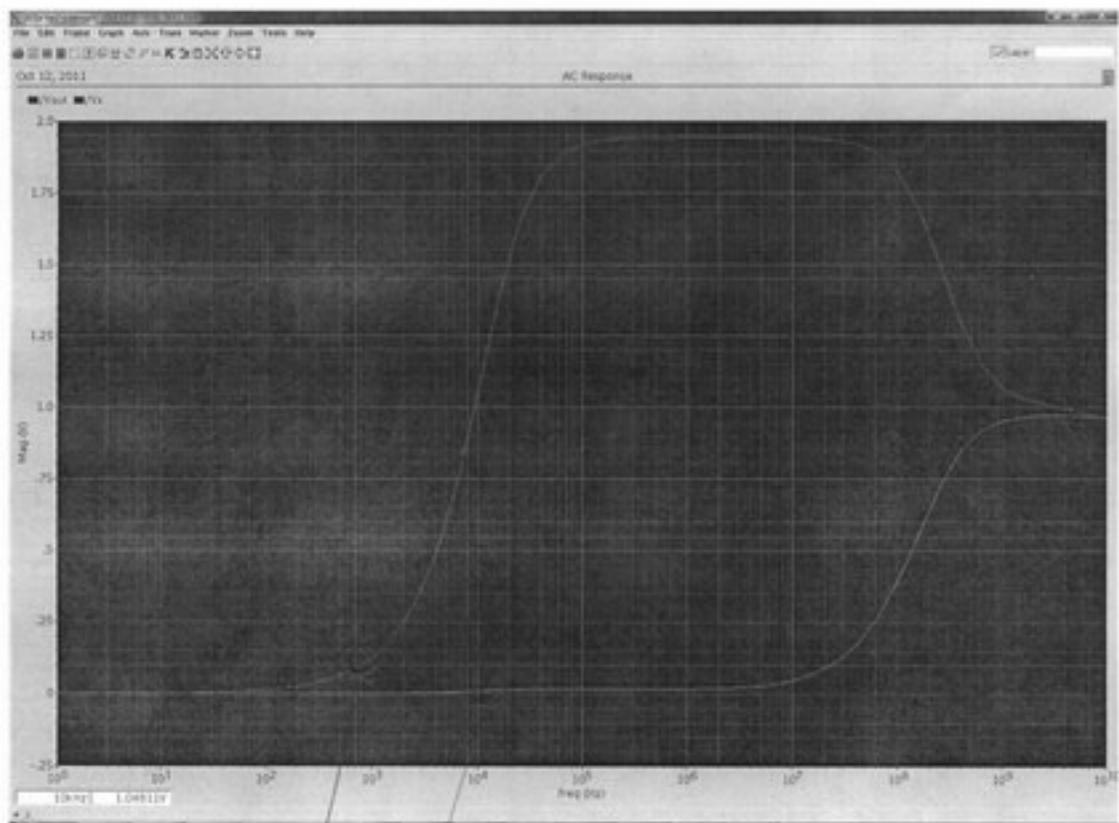$I_D = 46 \mu\text{m}$ due to channel length modulation on M4




Vout


VA : AC Ground

Closed loop gain is below 2.

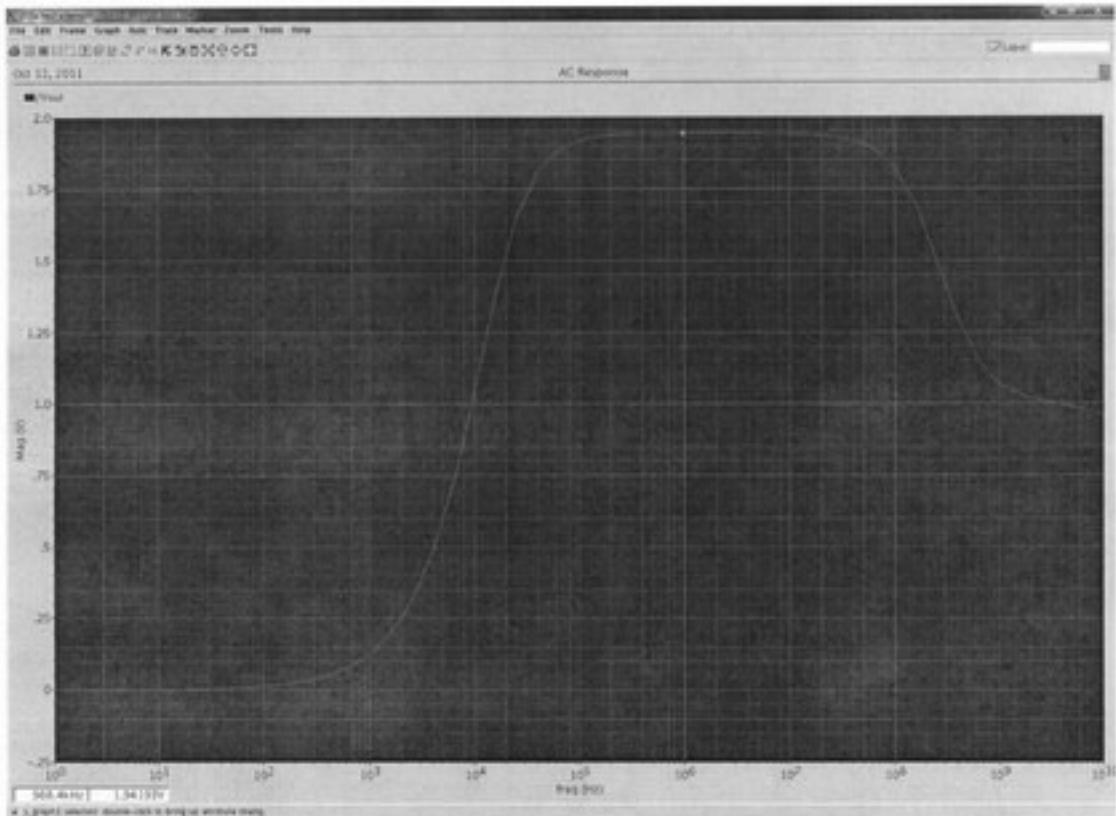
Also, amplifier is loaded by transistor caps which manifest themselves in high frequency.




closed loop gain

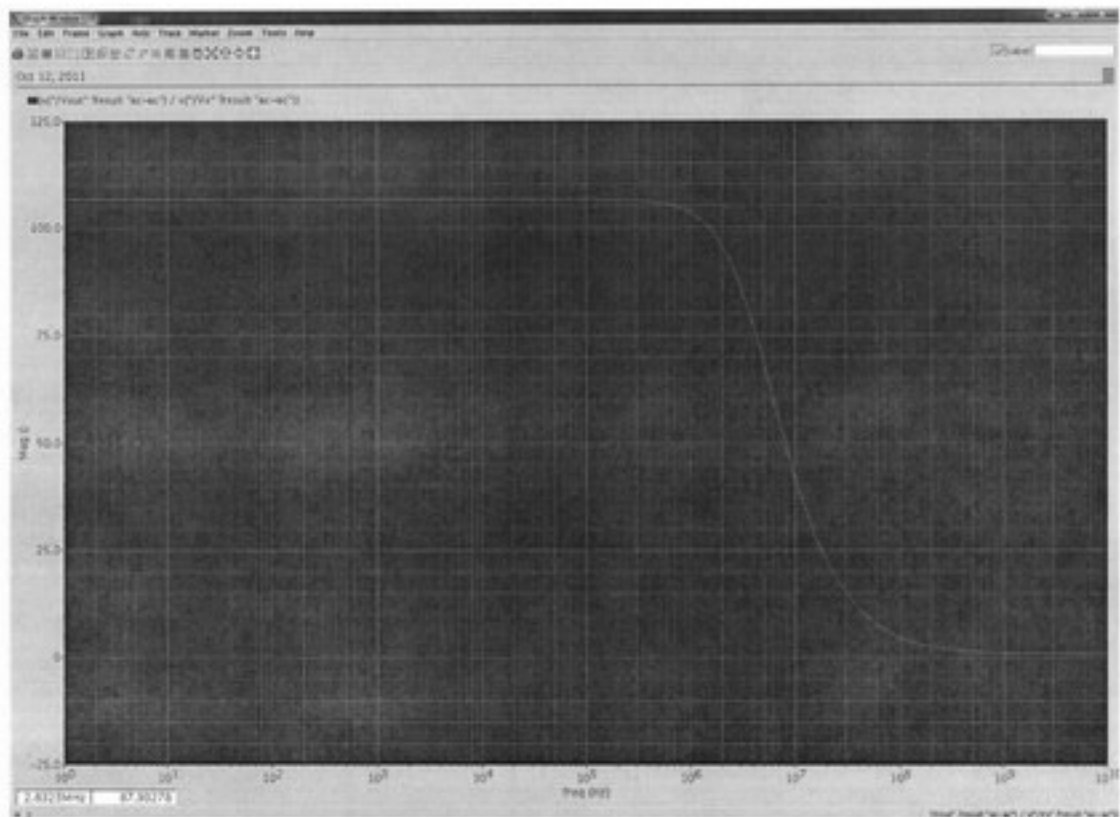

Open loop gain = $\frac{V_{out}}{V_A}$

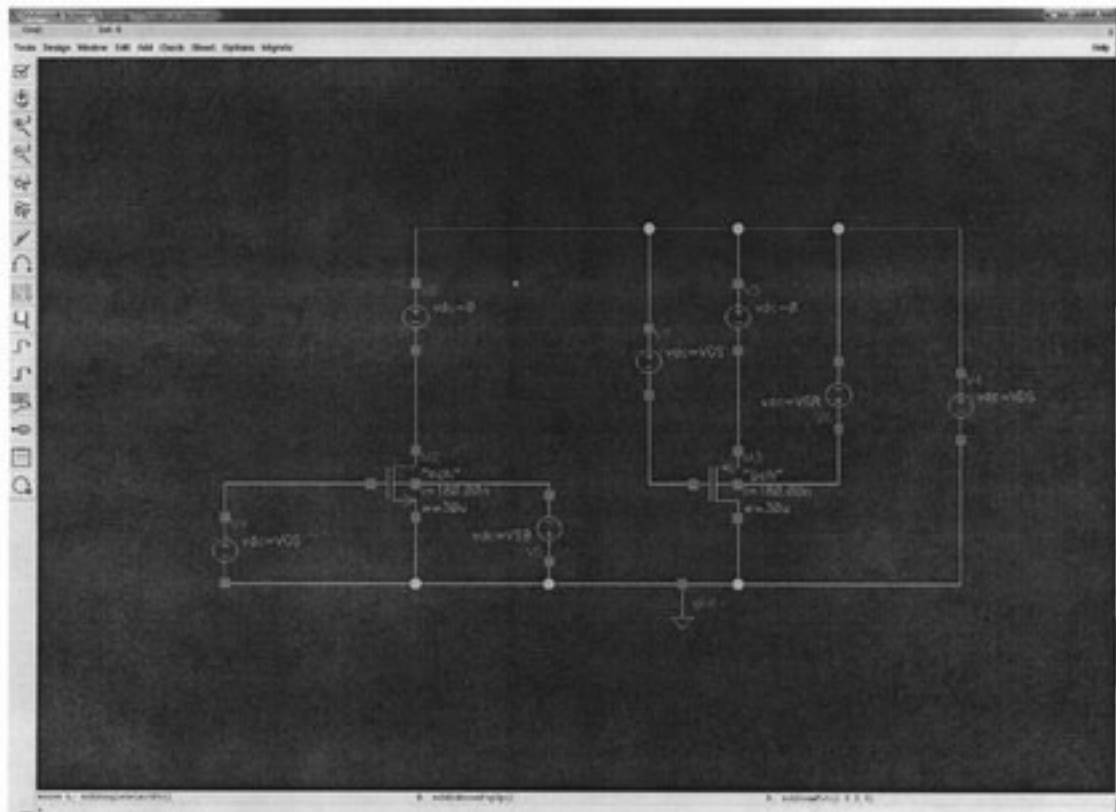

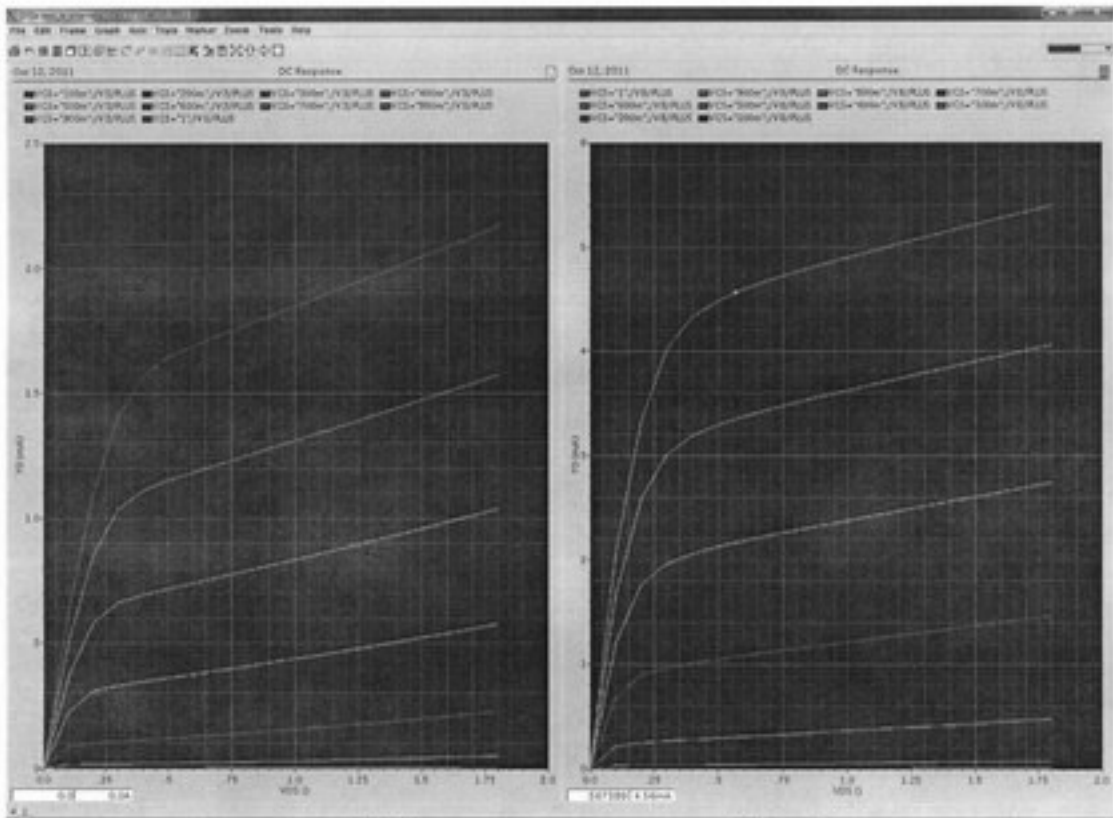Schematic to find I-V characteristics of NMOS & PMOS



NMOS

PMOS

I-V Characteristic Curve of NMOS & PMOS.