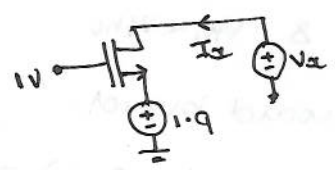



2.5c

QW:  $I_{D1}$  gm as a function of  $V_{DS} \in (0, \infty)$

$\beta = \mu_n C_{ox} W/L$   
in all questions.



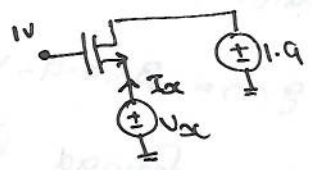
(i) Starting at  $V_{DS} = 0$  & showing source at lowest voltage




Device starts in saturation as  $V_{DS} > V_{GS} - V_{th}$

$I_{D1} = -\frac{\beta}{2} (1 - V_{DS} - V_{th})^2 = -I_{D0}$ ;  $g_m = \frac{\partial I_{D0}}{\partial V_{GS}} = \beta(1 - V_{DS} - V_{th})$

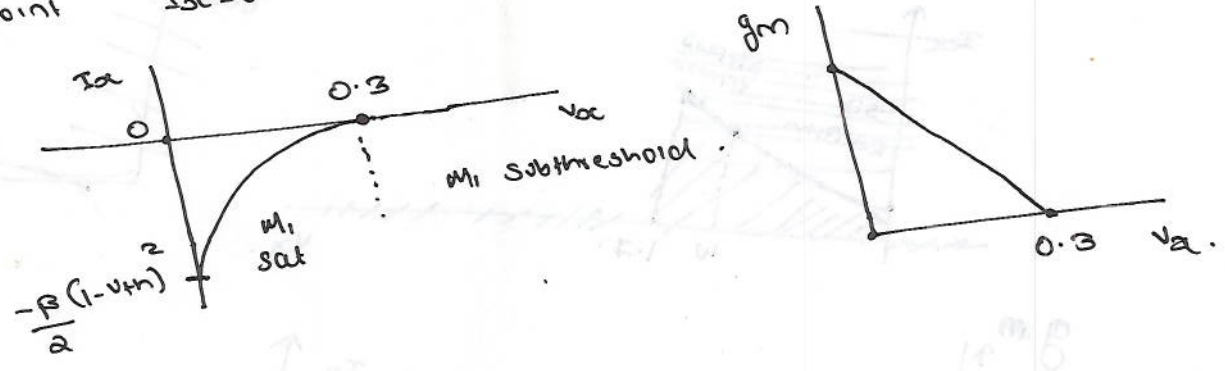Device goes off at  $V_{DS} = 1 - V_{th} = 0.3V$  at which point  $I_{D1} = 0$



Q.5E

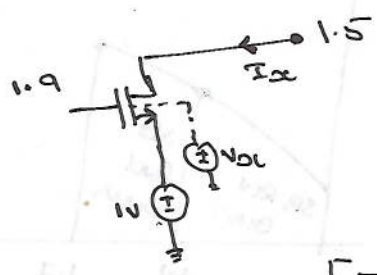

$V_{th} = V_{th0} + \sqrt{\alpha \phi_F + V_{SB}} - \sqrt{\alpha \phi_F}$

$V_{SB} = (1 - V_{DS})$

$V_{th} = V_{th0} + \sqrt{\alpha \phi_F + 1 - V_{DS}} - \sqrt{\alpha \phi_F}$  — (1)

(i)  $0 \leq V_{DS} \leq 1 \Rightarrow V_{th} > V_{th0}$  & device  $M_1$  in saturation & BB clock in reverse biased

$\Rightarrow V_{th, max} (V_{DS} = 0, \gamma = 0.45, \phi_F = 0.9) = 0.893V$

$$I_x = \frac{\beta}{2} (0.9 - v_{th})^2$$

$$g_m = \beta (0.9 - v_{th})$$

(ii)  $1 \leq v_x \leq 1.7 \Rightarrow v_{SB}$  is negative &  $v_{th} < v_{th0}$

$\Rightarrow$  SB diode is forward biased.

$$\Rightarrow v_{th_{min}} \left. \begin{array}{l} \} v_{SB} = -0.7, \gamma = 0.45, \alpha \beta_F = 0.9 \end{array} \right) = 0.47V$$

$\Rightarrow M_1$  is in saturation.





$$I_x = \frac{\beta}{2} (0.9 - v_{th})^2$$

$$g_m = \beta (0.9 - v_{th})$$


(iii)  $v_x \geq 1.7 \Rightarrow$  SB diode heavily forward biased

$\Rightarrow$  Eqn (1) no longer valid

$\Rightarrow$  device will latch up

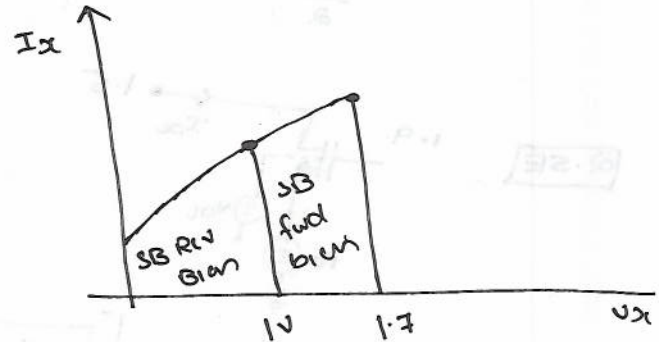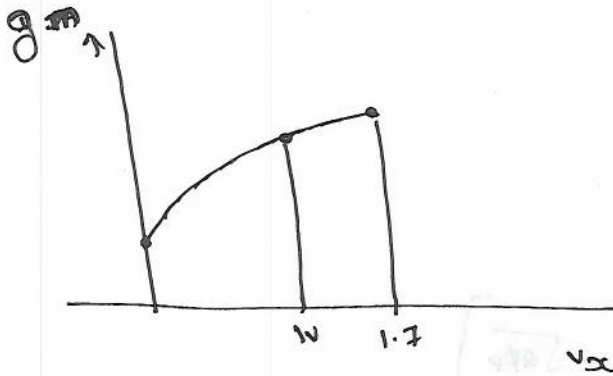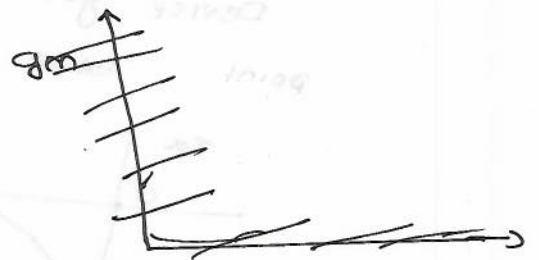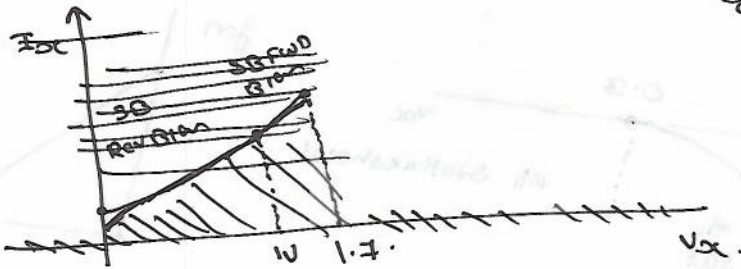

2.6b

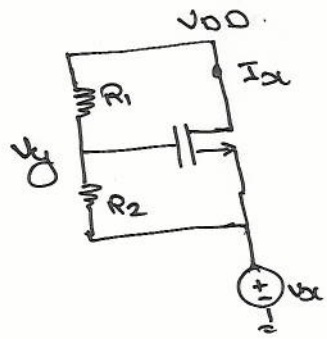

$$V_y = \frac{V_{DD}R_2 + V_x R_1}{R_1 + R_2}$$

$$V_{gs} = \frac{[V_{DD} - V_x]R_2}{R_1 + R_2}$$

where  $M_1$  is off.

i) starting  $V_x = V_{DD}$  for convenience  
 an  $V_y = V_{DD}$ .  $V_{gs} = 0$ .

device will turn on when  $V_{gs} = V_{th}$

$$\Rightarrow \frac{(V_{DD} - V_x)R_2}{R_1 + R_2} = V_{th}$$



$V_x = V_{DD} - V_{th} \frac{(R_1 + R_2)}{R_2} = V_{x1}$  till which  $I_x = 0$ .

ii) since  $V_g < V_d$


so for device always in saturation.

$$I_x = \frac{\beta}{2} \left( \frac{(V_{DD} - V_x)R_2}{R_1 + R_2} - V_{th} \right)^2$$
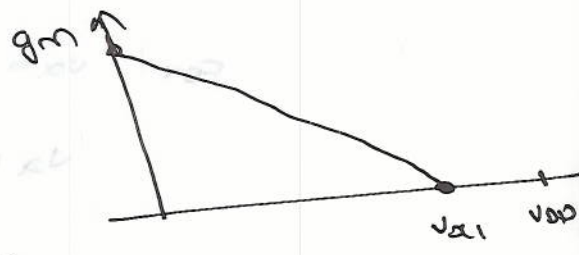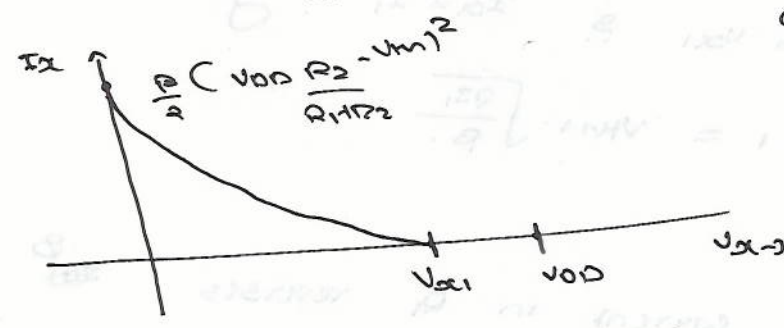
$$g_m = \frac{\beta}{2} \left( \frac{(V_{DD} - V_x)R_2}{R_1 + R_2} - V_{th} \right)$$



2.6 e

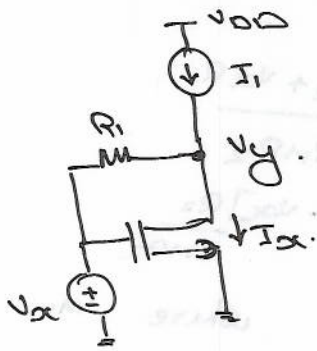

(i) Starting at  $v_a = 0$  for convenience.  
 Device  $M_1$  in off at this point &  $v_y = 0 + I_1 R_1$   
 As  $v_a$  increase  $v_y$  and increases on  $v_a + I_1 R_1$   
 $I_a = 0$  &  $v_y = v_a + I_1 R_1$  until  $v_a = v_{th}$ .

(ii)  $v_a > v_{th}$  & device turn on in saturation on  $v_a > v_g - v_{th}$   
 $\{v_y > v_a \text{ at } v_a = v_{th}\}$

$$I_a = \frac{\beta}{2} (v_a - v_{th})^2 ; g_m = \beta (v_a - v_{th})$$

hence  $v_y = v_a + (I_1 - I_a) R_1$

For  $v_a = v_{a1}$   $\therefore I_a = I_1$   $v_y = v_a$

$$v_{a1} = v_{th} + \sqrt{\frac{2I_1}{\beta}}$$

(iii)  $v_a > v_{a1}$  current in  $R_1$  reverses  
 Device still in saturation until  
 $v_d = v_g - v_{th}$   
 $v_{a2} = v_{a1}$   $\therefore v_d = v_g - v_{th}$

$$\Rightarrow v_{a2} + (I_1 - I_a) R_1 = v_{a1} - v_{th}$$

$$\Rightarrow (I_a - I_1) R_1 = v_{th}$$



$$\Rightarrow \left( \frac{\beta}{2} (v_{a2} - v_{th})^2 - I_1 \right) R_1 = v_{th}$$

$$I_{D1} = \frac{\beta}{2}(v_{GS1} - v_{th})^2 \quad \text{in this region; } g_m = \beta(v_{GS1} - v_{th})$$

(iv)  $v_{GS} > v_{GS2}$  device is in demand region.


$$I_{D1} = \beta \left[ (v_{GS} - v_{th})(v_{GS} - v_{GS2}) - \frac{(v_{GS} - v_{GS2})^2}{2} \right] \quad \text{where } v_{GS} = v_{GS2} + (I_{D1} - I_{D2})R_1$$

$$g_m = \beta(v_{GS} - v_{GS2})$$

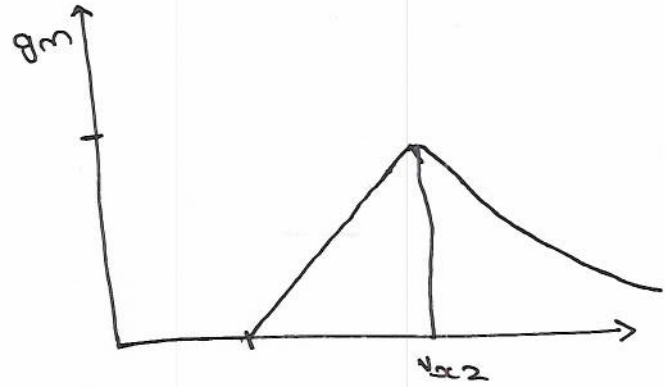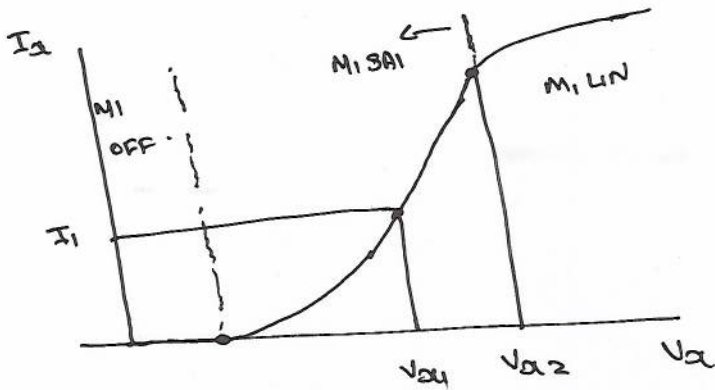




2.7b Qn Vout on f(vin) on vin ∈ (0, ∞)

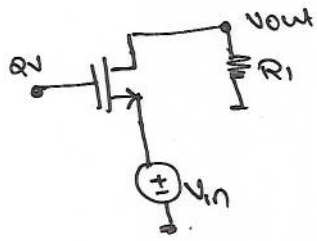

$V_{in} > V_{out}$

Redrawing

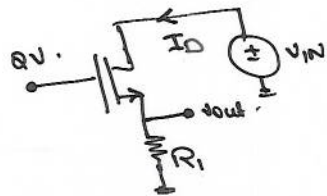

(i) starting from  $V_{in} = 0 \Rightarrow I_D = 0 \Rightarrow V_{out} = 0$ .  
Device starts in linear region

$$I_D = \beta \left( \frac{Q - V_{out}}{-V_{th}} (V_{in} - V_{out}) - \frac{(V_{in} - V_{out})^2}{2} \right)$$

$$V_{out} = I_D R_i$$



this is valid until  $V_{in} = V_{in1} = Q - V_{th}$  when  
 $V_{th} = V_{th0} + \left[ \sqrt{2\beta R_i + V_{out}} - \sqrt{2\beta R_i} \right]$

(ii) when  $V_{in} > V_{in1}$  device is in saturation.

$$I_D = \frac{\beta}{2} (Q - V_{out} - V_{th})^2 \quad \& \quad V_{out} = I_D R_i = V_{out1}$$


$$= \frac{\beta}{2} (Q - \cancel{I_D R_i} - V_{th})^2$$

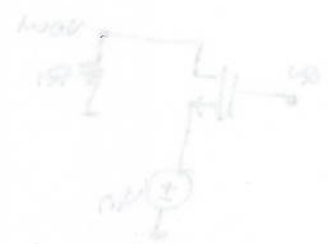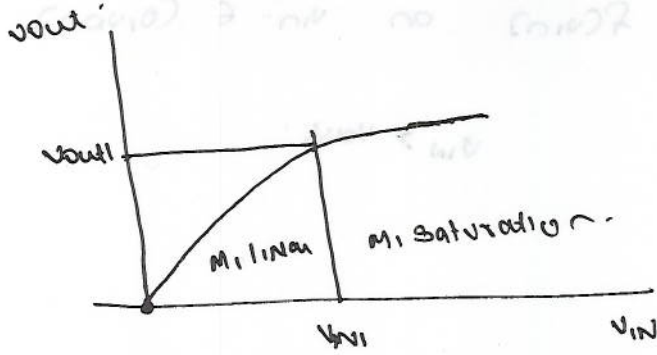For high  $V_{in}$   $V_{out}$  increases slightly due to channel length modulation but otherwise stays constant.



2.7c

Same as 2.7b with  $v_{G1} = 3V$ .

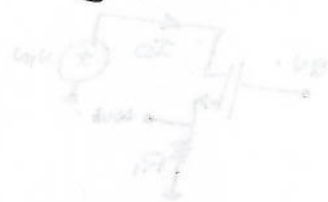

① Starting from  $v_{in} = 0$  to  $v_{in} = 1.5V$  the device operates in linear region

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_{th})^2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (3 - v_{DS})^2$$


② When  $v_{in} > 1.5V$  device is in saturation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_{th})^2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (3 - 1.5)^2$$


For  $v_{in} > 1.5V$  the drain current is constant and the output voltage increases.




Q.8c

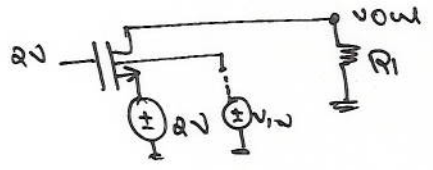

$V_{out} < 2V$

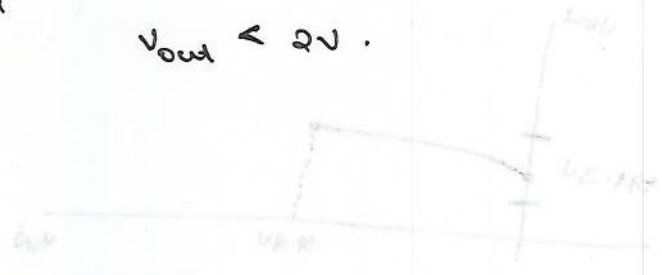

Redrawing

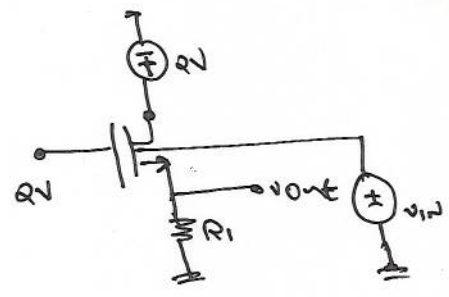

① Starting with  $V_{in} = 0$  ~~device~~ is in saturation  
 $V_{th} = V_{th0} + \sqrt{\frac{2\phi_F + (V_{out} - V_{in})}{\phi_F}}$



$V_{out} = I_D R_i$

$I_D = \frac{\beta}{2} (2 - V_{out} - V_{th})^2$  (ignoring channel length modulation)

As  $V_{in}$  increases  $V_{th}$  reduces increasing  $I_D$   
 & hence  $V_{out}$  slowly increases due to negative feedback via  $V_{GS}$  &  $R_i$   
 increase in  $V_{out}$  is much slower compared to  $V_{in}$ .

② As  $V_{in}$  increases it will catch up with  $V_{out}$  at some point. ( $V_{out}$  stays in the vicinity of  $2 - 0.7 = 1.3V$ ) and beyond which SB diode will forward bias taking  $V_{th}$  below  $V_{th0}$ .

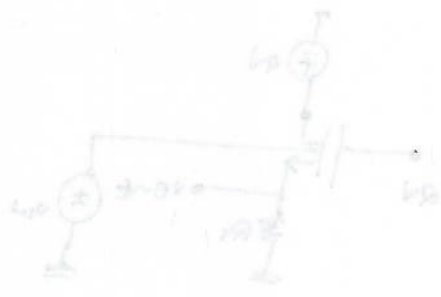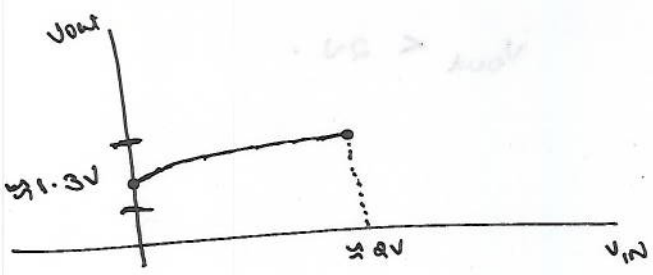③ For large values of  $V_{in}$  SB junction will be heavily forward biased & equation 2 won't be valid



① showing that  $I_C = I_E$  when  $V_{CE} > V_{CE(sat)}$

$$I_C = I_E - I_{B(sat)} = I_E - \frac{I_{C(sat)}}{\beta}$$


$$I_C = I_E - I_{B(sat)}$$

$$I_C = \frac{\beta}{\beta + 1} (I_E - I_{B(sat)})$$

(identical)  
 (transistor)  
 (circuit)

As an increase in  $I_E$  will cause a corresponding increase in  $I_C$  and  $I_B$ .  
 The collector current  $I_C$  is approximately equal to the emitter current  $I_E$ .  
 The base current  $I_B$  is very small compared to  $I_E$  and  $I_C$ .  
 The relationship between  $I_C$  and  $I_E$  is given by  $I_C = I_E - I_B$ .  
 For large  $\beta$ ,  $I_C \approx I_E$ .  
 The collector current  $I_C$  is limited by the collector resistor and the supply voltage.

Q.9b

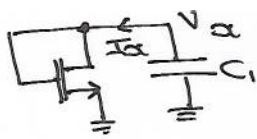

$t = 0$   $V_a = 3V$  Device is in saturation

$$t > 0 \quad I_d = \frac{\beta}{2} (V_a - V_{th})^2 = -C_1 \frac{dV_a}{dt}$$

$$\frac{dV_a}{(V_a - V_{th})^2} = \frac{-\beta dt}{2C_1}$$

Integrating  $\Rightarrow$

$$\frac{(V_a - V_{th})^{-1}}{-1} = \frac{-\beta t}{2C_1} + K$$

$$\frac{1}{V_a - V_{th}} = \frac{\beta t}{2C_1} - K$$


$t = 0$   $V_a = 3 \Rightarrow$


$$\frac{1}{3 - V_{th}} = -K$$

$$\Rightarrow \frac{1}{V_a - V_{th}} = \frac{\beta t}{2C_1} + \frac{1}{3 - V_{th}}$$

$$V_a = V_{th} + \frac{1}{\frac{\beta t}{2C_1} + \frac{1}{3 - V_{th}}}$$
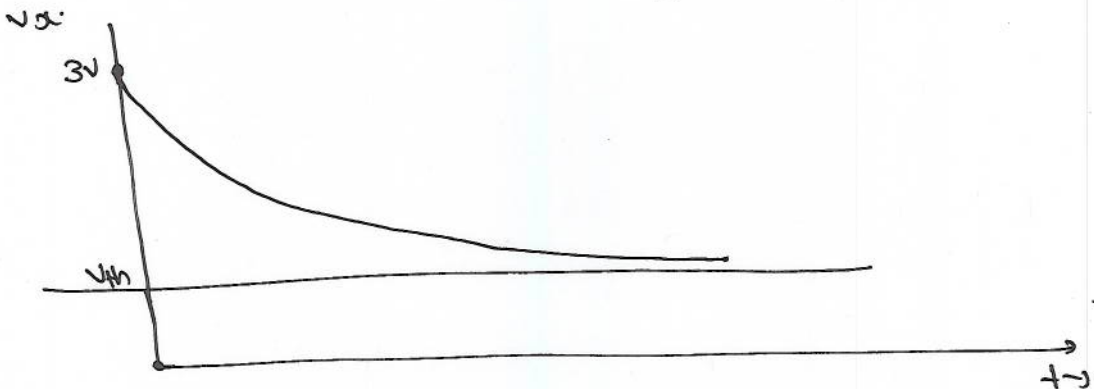
$$I_d = \frac{\beta}{2} \left( \frac{1}{\frac{\beta t}{2C_1} + \frac{1}{3 - V_{th}}} \right)^2$$



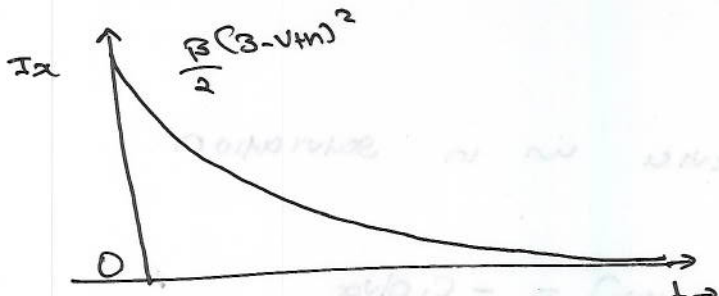

$$I_x = \frac{1}{2} B (3 - v_{th})^2 e^{-\frac{t}{\tau}}$$

$$\frac{dI_x}{dt} = -\frac{I_x}{\tau}$$

$$I_x + \frac{1}{\tau} I_x = \dots$$

$$I_x = \dots$$

$$t = 0 \Rightarrow \dots$$

$$I_x = \dots$$


$$\frac{1}{\tau} + \frac{1}{\tau} = \dots$$

$$\frac{1}{\tau} = \dots$$

$$\frac{1}{\tau} = \dots$$





2.9c

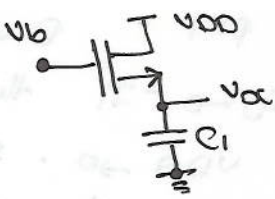


$V_b < V_{DD} = 3V$

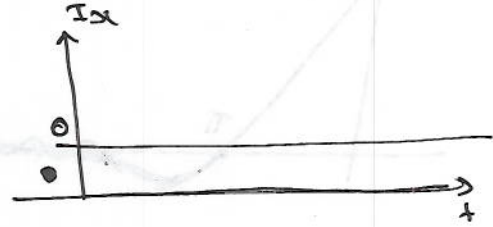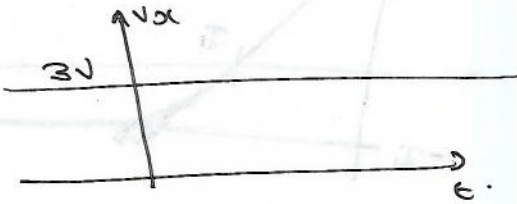$t = 0^-$   $V_a = 3V$   $\Rightarrow$  device  $M_1$  is off so  $V_a$  stays at  $3V$ .  $I_a = 0$



2.10a

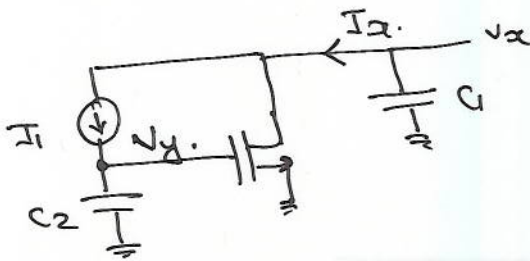

$t = 0^-$   $V_y = 3V$   $V_a = 1V$   
 $t > 0$

device is in linear region


$V_y = 3 + \frac{I_1 t}{C_1}$

$I_1 + \beta \left[ (V_y - V_{th}) V_a - \frac{V_a^2}{2} \right] + C_1 \frac{dV_a}{dt} = 0$

$\Rightarrow V_a$  discharges towards zero &  $V_a(t = \tau_1) = 0$ .

$t > \tau_1$   $V_a < 0 \Rightarrow$  source drain swap. Device still in linear region




$V_y = 3 + I_1 t$

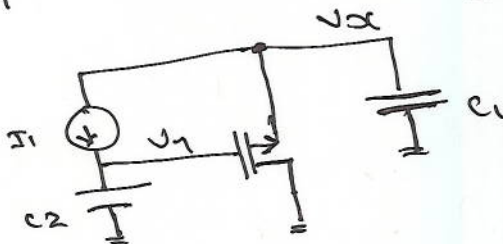

$I_1 - \beta \left[ (V_y - V_a - V_{th})(-V_a) - \frac{V_a^2}{2} \right] + C_1 \frac{dV_a}{dt} = 0$

clearly  $V_a$  will reduce &  $I_D$  will tend to  $I_1$  at steady state.

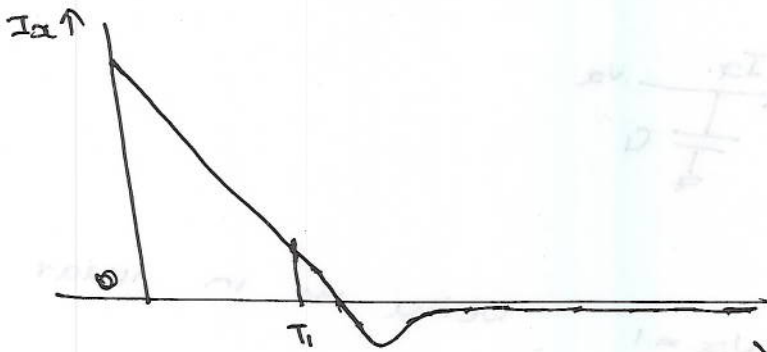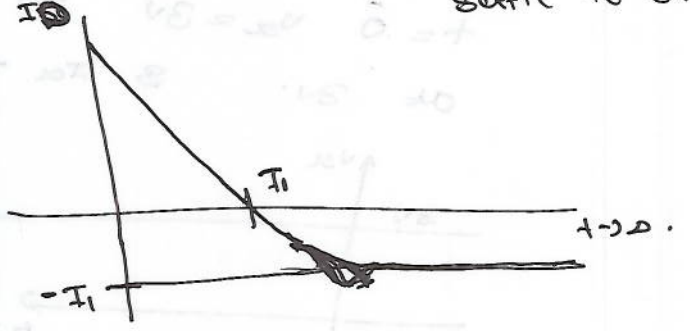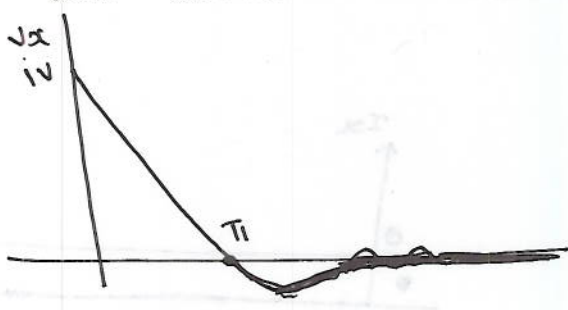Solving this we can get a plot. But intuitively at  $t = \infty$   $v_{gs} = \infty$   $I_D \rightarrow -I_1$  this will be achieved by a small  $v_{DS} \rightarrow 0$ . So  $v_{DS}$  will overshoot to a negative value & then will slowly settle to zero.



$$v_{gs} = \dots$$


$$0 = \frac{v_{gs}}{R_D} + \left[ \frac{v_{gs}}{C_L} - \dots \right] + I_1$$



$$I_1 = \dots$$


Clearly  $v_{gs}$  will reach  $\infty$  &  $I_D$  will reach  $-\infty$  at  $t = \infty$

2.11a)

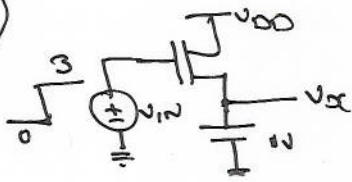

$t < 0$  M<sub>1</sub> is off  $v_{gs} < 0$ .

$t > 0$

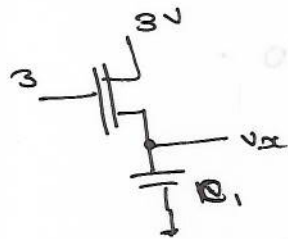

ignoring body effect & channel length modulation.

$$\frac{\beta}{2} (3 - v_{th} - v_o)^2 = C_1 \frac{dv_o}{dt}$$

$$\frac{dv_o}{(3 - v_{th} - v_o)^2} = + \frac{\beta dt}{2C_1}$$

$$\frac{1}{1 + (3 - v_{th} - v_o)} = + \frac{\beta t}{2C_1} + K$$


$t=0 \quad v_o = 1$

$$K = \frac{1}{2 - v_{th}}$$


$$3 - v_{th} - v_o = \frac{1}{\frac{\beta t}{2C_1} + K}$$

$$v_o = 3 - v_{th} - \frac{1}{\frac{\beta t}{2C_1} + K}$$
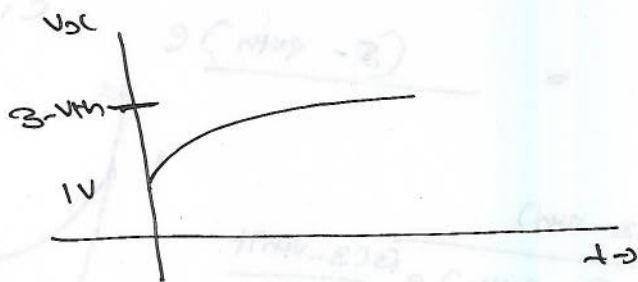
$$= 3 - v_{th} - \frac{1}{\frac{\beta t}{2C_1} + \frac{1}{2 - v_{th}}}$$



Q.11b

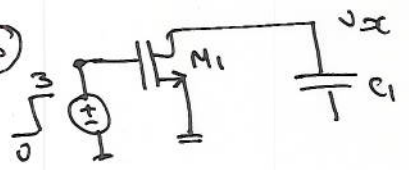

$t=0^-$   $v_{gs} = 0$   $M_1$  in off.  
 $t>0$   $v_{gs} = 3V$   $M_1$  in on in linear region

$$\beta \left[ (3 - v_{th}) v_x - \frac{v_x^2}{2} \right] + C_1 \frac{dv_x}{dt} = 0$$

$$\frac{dv_x}{v_x \left[ (3 - v_{th}) - \frac{v_x}{2} \right]} = - \frac{\beta dt}{2C_1}$$

$$\frac{dv_x}{2(3 - v_{th})} \left[ \frac{1}{v_x} + \frac{1}{2(3 - v_{th}) - v_x} \right] = - \frac{\beta dt}{2C_1}$$

Integrating  $\int \frac{v_x}{2(3 - v_{th}) - v_x} = - \frac{\beta(3 - v_{th})t}{C_1} + \text{unk}$


$$\frac{v_x}{2(3 - v_{th}) - v_x} = k e^{- \frac{\beta(3 - v_{th})t}{C_1}}$$

$t=0$   $v_x = 1 \Rightarrow k = \frac{1}{5 - 2v_{th}}$

$$\frac{v_x}{2(3 - v_{th}) - v_x} = \frac{1}{5 - 2v_{th}} e^{- \frac{\beta(3 - v_{th})t}{C_1}}$$

$$\frac{2(3 - v_{th}) - 1}{v_x} = \frac{(5 - 2v_{th}) e^{- \frac{\beta(3 - v_{th})t}{C_1}}}{1}$$
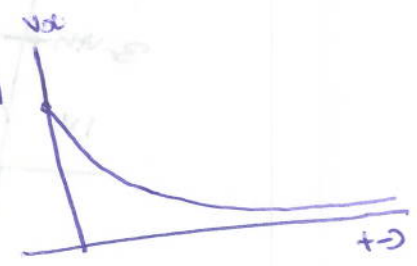
$$v_x = \frac{2(3 - v_{th})}{1 + (5 - 2v_{th}) e^{- \frac{\beta(3 - v_{th})t}{C_1}}}$$





(2.26) a)  $t=0^-$   $v_x = v_{DD}$ ,  $I_D = I_1$ ,  $v_y = v_{y0} = v_{DD} - v_{th} - \sqrt{\frac{2I_1}{\beta}}$

$t=0^+$  voltage across capacitor can't change instantly - so the step at  $v_{in}$  propagates to  $v_x \approx v_y$

$v_y(0^+) = v_{y0} + v_0$  &  $v_x(0^+) = v_{DD} + v_0$

$t > 0$  Since  $I_{CP} = 0$   $v_x - v_y = \text{constant} = v_{DD} - v_{y0}$



This means  $v_{gs}$  of device is constant and same as  $t=0^-$ . However since  $v_0 > v_{th}$  device enters linear region &  $I_D < I_1$  given by.

$$I_D = \beta \left[ (v_{DD} - v_{y0} - v_{th})(v_{DD} - v_y) - \frac{(v_{DD} - v_y)^2}{2} \right]$$

This will lead to discharge of node  $v_y$ .

an  $C_2 \frac{d}{dt} (v_0 - v_y) = I_1 - I_D$

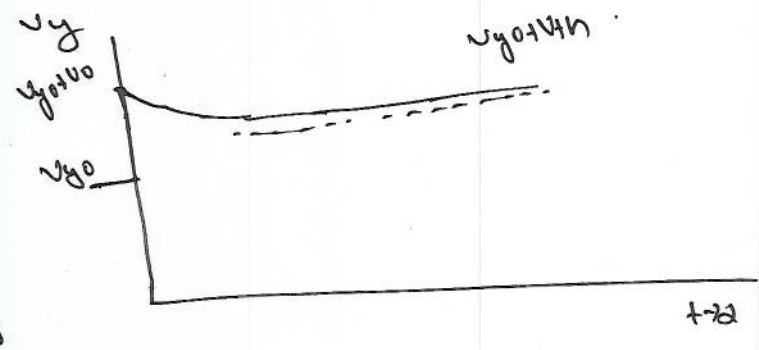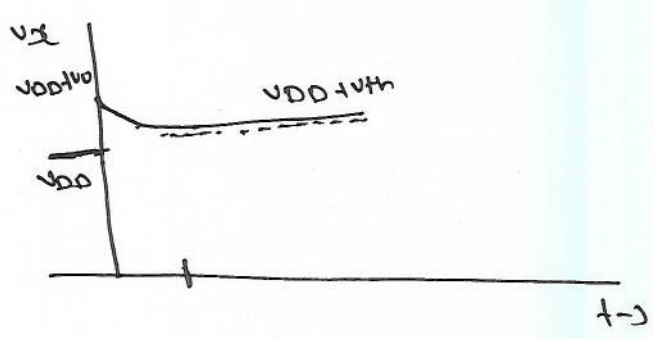As  $v_y$  falls  $v_x$  tracks the change & this will continue until  $v_x$  reaches  $v_{DD} + v_{th}$  at which point  $M_1$  enters saturation making  $I_D = I_1$ . The voltage at  $v_y$  will hence tend to  $v_{y0} + v_{th}$  in steady state.



Q.26b

$t=0^- \quad v_x = v_{00} \quad v_y = v_{y0} = v_{00} - \frac{v_{00}}{\beta} \sqrt{\frac{2I_0}{\beta}}$



$t=0^+ \quad v_x = v_{00} - v_0 \quad v_y = v_{y0} - v_0$

$t > 0 \quad \sin \alpha \quad I_{C1} = 0 \quad v_x - v_y = v_{00} - v_{y0}$

Since device is in saturation,  $I_0 = I_1 \Rightarrow I_{C2} = 0$  so no change in voltages after initiation step.

