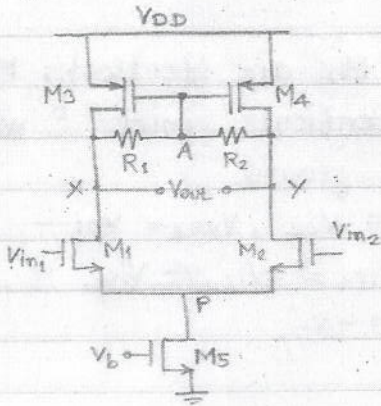


Total Q8.


Problem 4.18

Fig. 4.38(d)



If M_1 & M_2 are identical and so are M_3 & M_4 and if $R_1 = R_2$ the circuit is symmetric and half-circuit concept can be used. Since circuit is symmetric, point A will be at AC ground. P is also at AC ground.

Using the half-circuit concept,

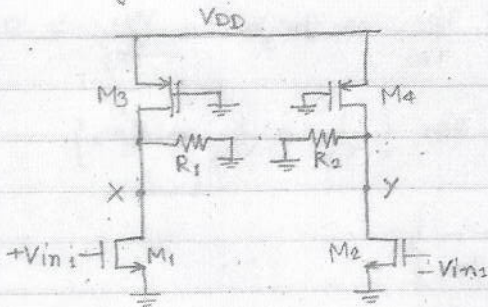

$$\frac{V_x}{V_{in1}} = -g_{m1} (r_{o3} \parallel r_{o1} \parallel R_1)$$

$$\frac{V_y}{-V_{in1}} = -g_{m2} (r_{o4} \parallel r_{o2} \parallel R_2)$$

$$V_x - V_y = -g_{m1} (r_{o3} \parallel r_{o1} \parallel R_1) V_{in1} - g_{m2} (r_{o4} \parallel r_{o2} \parallel R_2) V_{in1}$$

$$\therefore \frac{V_x - V_y}{2 V_{in1}} = -g_m (r_{o3} \parallel r_{o1} \parallel R_1)$$


$$\therefore \frac{V_{out}}{V_{in}} = A_v = -g_m (r_{o3} \parallel r_{o1} \parallel R_1) \quad \text{small signal differential voltage gain.}$$

1 mark for half ckt

2 mark for solution \Rightarrow give one mark for correct approach.

total = 3.

Fig. 4.39(c)

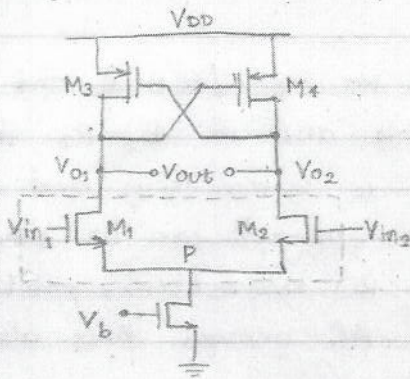


If M_1, M_2 are identical; M_3, M_4 are identical, point P will be an ac ground.

$$V_{GS3} = V_{02}, V_{GS4} = V_{01}$$

$$\text{If } V_{in1} = -V_{in2} = V_{in1}$$

$$V_{01} = -V_{02}$$

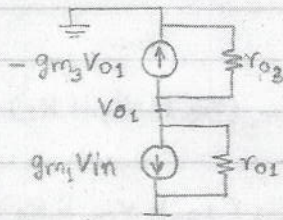The small signal equivalent circuit can be drawn as follows:



$$g_m V_{in} + \frac{V_{01}}{r_{o1}} - g_{m3} V_{01} + \frac{V_{01}}{r_{o3}} = 0$$

$$-g_{m1} V_{in} = V_{01} \left\{ \frac{1}{r_{o1}} + \frac{1}{r_{o3}} - g_{m3} \right\}$$

$$\therefore \frac{V_{01}}{V_{in1}} = -g_{m1} \left\{ \frac{1}{\frac{1}{r_{o1}} + \frac{1}{r_{o3}} - g_{m3}} \right\}$$

Also, similarly,

$$\frac{V_{02}}{-V_{in1}} = -g_{m2} \left\{ \frac{1}{\frac{1}{r_{o2}} + \frac{1}{r_{o4}} - g_{m4}} \right\}$$


$$\Rightarrow \frac{V_{01} - V_{02}}{2 V_{in1}} = -g_{m1} \left\{ \frac{1}{r_{o1}^{-1} + r_{o3}^{-1} - g_{m3}} \right\}$$

$$\Rightarrow \frac{V_o}{V_{in}} = A_v = - \frac{g_{m1}}{\frac{1}{r_{o1}} + \frac{1}{r_{o3}} - g_{m3}} \quad \dots \text{small signal differential gain}$$

- 1 mark half cr
- 2 mark for solution

total 2


Problem 4.21

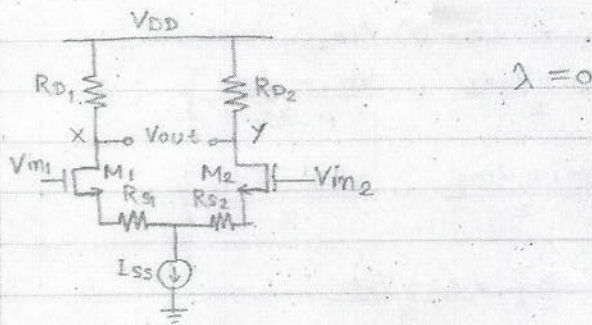

We use superposition theorem

From eqⁿ (3.55) if $v_o = \infty$,

$$\left. \frac{V_x}{V_{in1}} \right|_{V_{in2}=0} = \frac{-g_{m1} R_{D1}}{1 + (g_{m1} + g_{mb1})(R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}})}$$

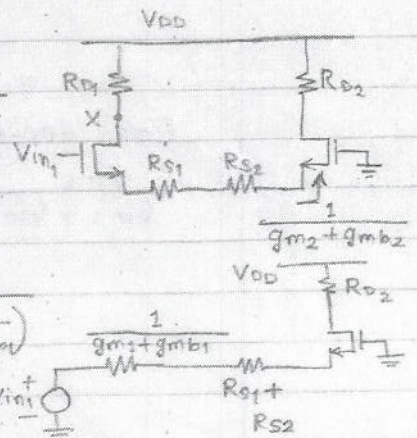

From eqⁿ if $v_o = \infty$,

$$\left. \frac{V_y}{V_{in2}} \right|_{V_{in1}=0} = \frac{(g_{m2} + g_{mb2}) \cdot R_{D2}}{1 + (g_{m2} + g_{mb2})(R_{S1} + R_{S2} + \frac{1}{g_{m1} + g_{mb1}})}$$

Similarly,

$$\left. \frac{V_y}{V_{in2}} \right|_{V_{in1}=0} = \frac{-g_{m2} R_{D2}}{1 + (g_{m2} + g_{mb2})(R_{S1} + R_{S2} + \frac{1}{g_{m1} + g_{mb1}})}$$

$$\& \left. \frac{V_x}{V_{in2}} \right|_{V_{in1}=0} = \frac{(g_{m1} + g_{mb1}) \cdot R_{D1}}{1 + (g_{m1} + g_{mb1})(R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}})}$$

$$V_x = \underbrace{\frac{-g_{m1} R_{D1}}{1 + (g_{m1} + g_{mb1})(R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}})}}_A V_{in1} + \underbrace{\frac{(g_{m2} + g_{mb2}) \cdot R_{D2}}{1 + (g_{m2} + g_{mb2})(R_{S1} + R_{S2} + \frac{1}{g_{m1} + g_{mb1}})}}_B V_{in2}$$

$$\therefore V_x = A V_{in1} + B V_{in2}$$

$$V_y = \underbrace{\frac{-g_{m2} R_{D2}}{1 + (g_{m2} + g_{mb2})(R_{S1} + R_{S2} + \frac{1}{g_{m1} + g_{mb1}})}}_D V_{in2} + \underbrace{\frac{(g_{m1} + g_{mb1}) \cdot R_{D1}}{1 + (g_{m1} + g_{mb1})(R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}})}}_C V_{in1}$$

$$\therefore V_y = C V_{in1} + D V_{in2}$$

Total 4 marks
 → give partial
 credits
 → 2 marks
 if approach
 is correct.

$$\therefore V_x - V_y = (A-C) V_{in1} + (B-D) V_{in2}$$

$$\therefore V_x - V_y = (A-C) \left\{ \frac{V_{in1} + V_{in2}}{2} + \frac{V_{in1} - V_{in2}}{2} \right\}$$

$$+ (B-D) \left\{ \frac{V_{in1} + V_{in2}}{2} - \frac{V_{in1} - V_{in2}}{2} \right\}$$

$$\therefore V_x - V_y = \{A-C+B-D\} \frac{V_{in1} + V_{in2}}{2}$$

$$+ \{A-C-B+D\} \frac{V_{in1} - V_{in2}}{2}$$

$$\therefore V_{out} = A_{cm} V_{cm} + A_{dm} V_{dm}$$


Considering only the differential mode gain,

$$\frac{V_{out}}{V_{in1} - V_{in2}} = (A-C-B+D)$$

$$= \frac{- (g_{m1}) (R_{D1} + R_{D2}) - g_{mb2} R_{D2}}{1 + (g_{m1} + g_{mb1}) (R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}})}$$

$$+ \frac{- (g_{m2}) (R_{D1} + R_{D2}) - g_{mb1} R_{D1}}{1 + (g_{m2} + g_{mb2}) (R_{S1} + R_{S2} + \frac{1}{g_{m1} + g_{mb1}})}$$

Problem 4.26

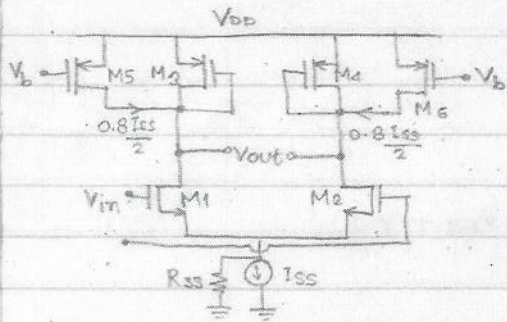

$$A_{VDM} = -g_{m1} R_D$$

$$A_{CM-DM} = \frac{-g_{m1} \Delta R_D}{(g_{m1} + g_{m2}) R_{SS} + 1} = \frac{-g_{m1} \Delta R_D}{1 + 2g_{m1} R_{SS}}$$

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \left| \frac{1 + 2g_{m1} R_{SS}}{\Delta R_D / R_D} \right| \quad (1)$$

$$R_D = r_{o5} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \parallel r_{o1} \approx \frac{1}{g_{m3}}$$

$$\frac{\Delta R_D}{R_D} = \frac{1}{R_D} \cdot \frac{\partial R_D}{\partial g_{m3}} \Delta g_{m3} = \frac{1}{R_D} \cdot \left(-\frac{1}{g_{m3}^2}\right) \Delta g_{m3}$$

$$\Rightarrow \frac{\Delta R_D}{R_D} = -\frac{\Delta g_{m3}}{g_{m3}} \quad \dots (ii)$$

$$g_{m3} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_3 I_{D3}}$$

$$\therefore \frac{\partial g_{m3}}{\partial I_{D3}} = \frac{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}{2\sqrt{I_{D3}}}$$

$$\therefore \frac{\Delta g_{m3}}{g_{m3}} = \frac{\partial g_{m3}}{\partial I_{D3}} \frac{\Delta I_{D3}}{g_{m3}} = \Delta I_{D3} \cdot \frac{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}{2\sqrt{I_{D3}}} \cdot \frac{1}{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_3 I_{D3}}}$$

$$\Rightarrow \frac{\Delta g_{m3}}{g_{m3}} = \frac{\Delta I_{D3}}{2I_{D3}} \quad \dots (iii)$$

$$I_{D5} + I_{D3} = \frac{I_{SS}}{2} \Rightarrow \Delta I_{D5} = -\Delta I_{D3}$$

$$\therefore I_{D5} = 0.8 \frac{I_{SS}}{2} \Rightarrow I_{D5} = 4 I_{D3}$$

$$\frac{\Delta I_{D5}}{I_{D5}} = -\frac{\Delta I_{D3}}{I_{D3}} \cdot \frac{I_{D3}}{I_{D5}} = -\frac{1}{4} \frac{\Delta I_{D3}}{I_{D3}} \quad \dots (iv)$$

$$I_{D5} = \mu_p C_{ox} \frac{W}{2L} (V_b - V_{DD} - V_{TH})^2$$

$$\Delta I_{D5} = \frac{\partial I_{D5}}{\partial V_{TH}} \Delta V = -\frac{\mu_p C_{ox} W}{2L} 2(V_b - V_{DD} - V_{TH}) \Delta V$$

$$\therefore \frac{\Delta I_{D5}}{I_{D5}} = -\frac{2 \Delta V}{V_b - V_{TH} - V_{DD}} \quad \dots (v)$$


total 4 marks
2 marks if approach is correct

(i), (ii), (iii), (iv), (v) \Rightarrow

$$CMRR = \left| \frac{1 + 2g_{m1}R_{SS}}{\left(-\frac{1}{2}\right)(-4)(-2) \frac{\Delta V}{V_b - V_{DD} - V_{TH}}} \right|$$

$$\therefore CMRR = \frac{(1 + 2g_{m1}R_{SS})(V_b - V_{DD} - V_{TH})}{4\Delta V}$$

Problem 5.10(a)

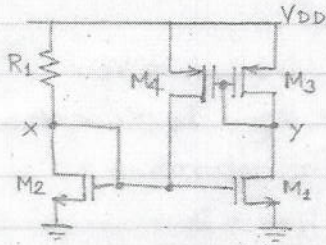

Initially, when $V_{DD} = 0$ assume M_3 & M_4 are OFF.

For $V_{DD} < V_{TH,1,2}$, $V_x = V_{DD}$ and M_1 & M_2 are OFF and Y is a floating output since it is isolated from V_{DD} and GND.

When $V_x \geq V_{TH,1,2}$, M_2 & M_1 turn ON.

M_2 & M_3 are always in saturation. At that moment, M_1 turns ON and pulls Y to GND, thus, turning ON M_3 & M_4 .

As $V_{DD} \uparrow$, $V_x = V_{GS2}$ & $V_y = V_{DD} - V_{GS3}$

$V_x > V_y$, M_1 & M_4 remain in triode always.

As $V_{DD} \uparrow$, $V_y \uparrow$ but not as

fast as V_{DD} because M_1 still tries to pull it to ground.

So, effectively $|V_x - V_{DD}| \uparrow$ i.e. $|V_{GS3}| \uparrow$, so, $I_{D3} \uparrow$

M_1 is in triode $I_{D1} = I_{D3} \propto [(V_{GS1} - V_{TH})V_{DS1} - V_{DS1}^2]$ small. $\therefore I_{D1} \propto [2(V_x - V_{TH})(V_y - V_y^2)]$. So, if $V_y \uparrow$, $V_x \uparrow$ to increase I_{D1} .

When $V_x > V_{TH,2}$ its not possible for M_4 & M_1 to be in saturation. since in that case. we would need

$$I_3 = I_2 = I_1 = I_4 + I_{R1} \text{ to be equal to } I_4.$$



so one of m_1 or m_4 has to be in triode $\Rightarrow V_x > V_y + V_{TH} \Rightarrow$ the other is in triode as well.

1 mark for each plot.


2 mark for the explanation

if explanation is wrong dont give marks for plot.

total 4.

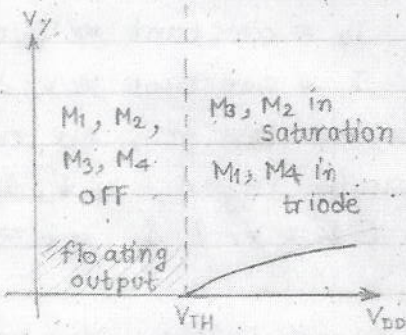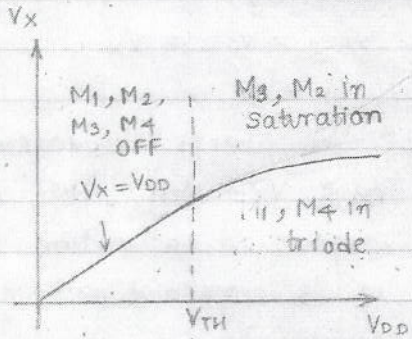

Problem 5.12(b)

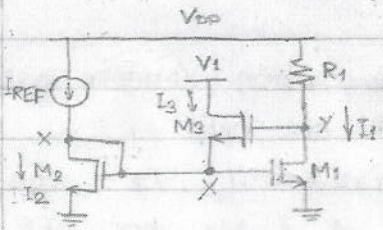

Initially let $V_1 = V_{DD}$

$$V_y = V_{DD} - I_1 \cdot R_1 < V_{DD}$$

M_3 in saturation.

$$I_2 = I_{REF} + I_3 =$$

Assuming $\lambda = 0$,

$$V_{GS2} = V_{GS1} = V_x$$

$$\therefore I_1 = I_2$$

If V_1 starts decreasing

$V_1 \geq V_y - V_{TH3}$, M_3 will remain in saturation

$$\Rightarrow I_3 \text{ constant} \Rightarrow I_1 = I_2$$


constant.

$$I_2 = \text{constant} \Rightarrow V_x \text{ const.}$$


$$I_1 = \text{constant} \Rightarrow V_y \text{ const.}$$

Beyond this pt., M_3 enters triode region, $I_3 \downarrow$, $I_2 \downarrow$, $I_1 \downarrow$
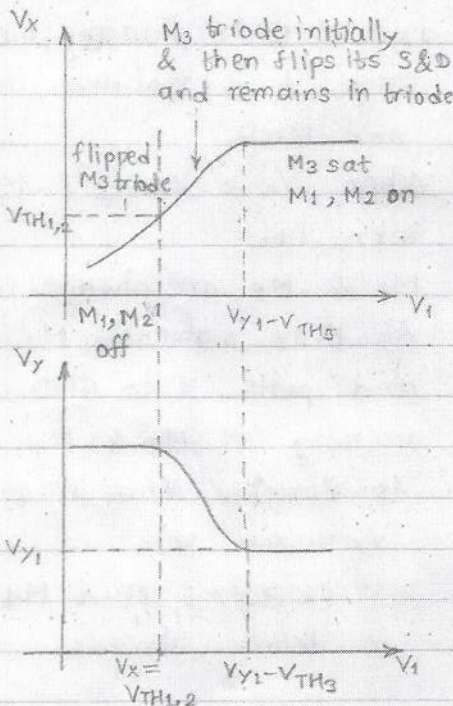
$$I_1 \downarrow \Rightarrow V_y \uparrow \text{ \& } I_2 \downarrow \Rightarrow V_x \downarrow$$



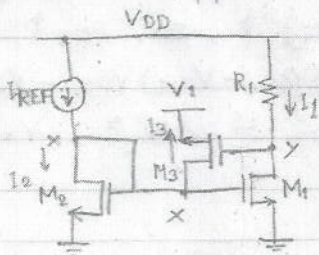At a point where $V_1 < V_x$ & $V_y - V_1 > V_{TH}$, M_3 turns ON in opposite direction. Now $I_3 \uparrow$, $I_2 \downarrow$, $I_1 \downarrow$. V_y continues to rise & V_x continues to drop.



When $V_x < V_{TH1,2}$, M_1 & M_2 are OFF.

$$I_3 = I_{REF}, \quad I_1 = I_2 = 0, \quad V_y = V_{DD}.$$

Now as $V_1 \downarrow$, $I_3 = I_{REF}$, $\therefore V_y = \text{const.}$


$V_{GS3} \uparrow$. In triode region, if V_{GS} is small

$I_3 \propto (V_{GS} - V_{TH}) V_{DS}$. So, if $V_{GS} \uparrow$, $V_{DS3} \downarrow$ to maintain I_3 constant. $\therefore V_{DS3} \downarrow$ i.e.


$$(V_x - V_1) \downarrow \Rightarrow V_x \downarrow$$

1 mark for each region
1/2 for plots
1/2 for explanation
total 3.

Problem 5.19

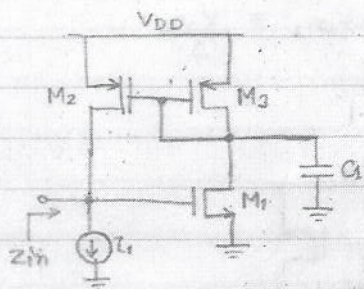

Small-signal equivalent model

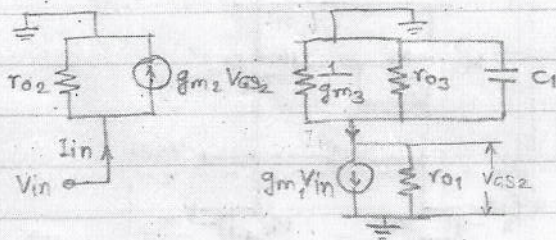

$$V_{gs2} = -g_{m1} V_{in} \left(\frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{o1} \parallel \frac{1}{sC_1} \right)$$

If $\lambda = 0$,

$$V_{gs2} = \frac{-g_{m1} V_{in}}{g_{m3} + sC_1}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{g_{m2} V_{gs2}} = \frac{V_{in}}{-g_{m1} g_{m2} V_{in}} \cdot \frac{g_{m3} + sC_1}{g_{m3} + sC_1}$$

$$\therefore Z_{in} = -\left(\frac{g_{m3} + sC_1}{g_{m1} g_{m2}} \right)$$

The negative input capacitive component is given by

$$C = \left(\frac{-sC_1}{g_{m1} g_{m2}} \right)$$



1 mark for small signal

2 mark for solution \Rightarrow if approach is correct.


total 3.

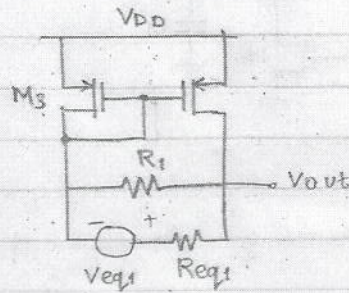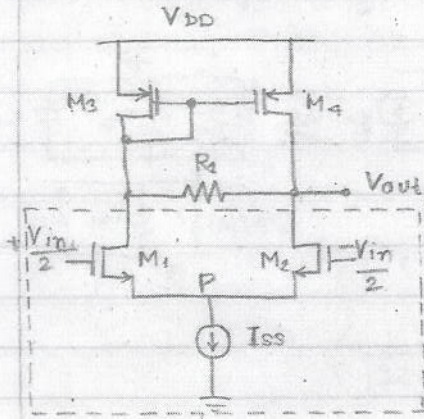Problem 5.20(b)

Let $V_{in1} = -V_{in2} = \frac{V_{in}}{2}$



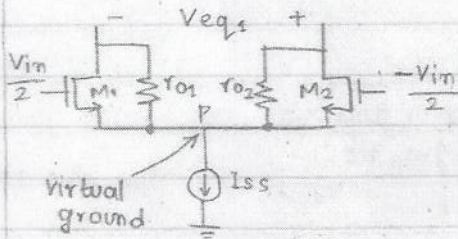Substitution of input differential pair by a Thevenin equivalent




We substitute the input source and M_1, M_2 by a Thevenin equivalent. Because of symmetry, node P is a virtual ground, & a half-circuit equivalent yields


$V_{eq1} = g_{m1,2} r_{o1,2} V_{in}$

Moreover $R_{eq} = r_{o1} + r_{o2} = 2 r_{o1,2}$

Simplified circuit :

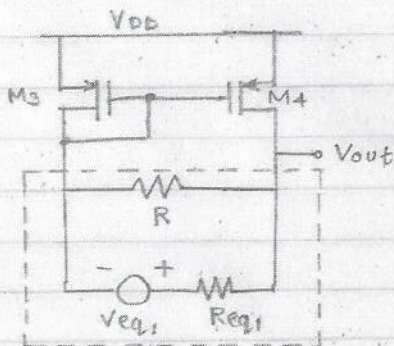

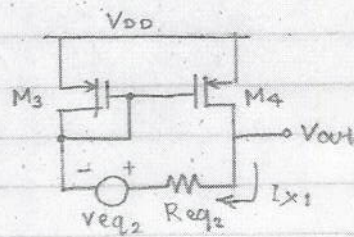Substituting a Thevenin equivalent for boxed circuit




$V_{eq2} = \frac{V_{eq1} R}{R + R_{eq1}} = \frac{g_{m1,2} r_{o1,2} V_{in} R}{R + 2 r_{o1,2}}$

$R_{eq2} = 2 r_{o1,2} \parallel R$

Total 4
2 marks if approach is correct

Simplified circuit:

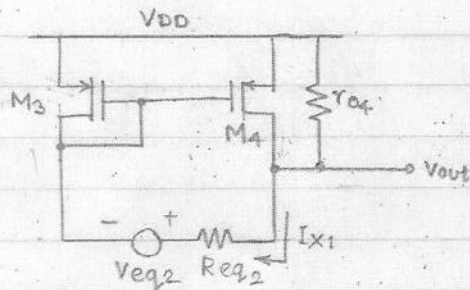

This circuit is similar to fig. 5.27(b) in the textbook.

Current through R_{eq2} is

$$I_{x1} = \frac{V_{out} - \frac{g_{m1,2} r_{o1,2} V_{in} R}{R + 2r_{o1,2}}}{2r_{o1,2} \parallel R + \frac{1}{g_{m3}} \parallel r_{o3}}$$

The fraction of this current that flows through $\frac{1}{g_{m3}}$ is mirrored into M_4 with unity gain,

$$\text{i.e. } 2 \left\{ \frac{V_{out} - \frac{g_{m1,2} r_{o1,2} V_{in} R}{R + 2r_{o1,2}} \cdot \frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}}}{2r_{o1,2} \parallel R + \frac{1}{g_{m3}} \parallel r_{o3}} \right\} = -\frac{V_{out}}{r_{o4}}$$

$$\therefore V_{out} \left[\frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}} \cdot \frac{1}{2r_{o1,2} \parallel R + \frac{1}{g_{m3}} \parallel r_{o3}} + \frac{1}{r_{o4}} \right] = -\frac{g_{m1,2} r_{o1,2} R}{R + 2r_{o1,2}} \cdot \frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}} \cdot \frac{1}{2r_{o1,2} \parallel R + \frac{1}{g_{m3}} \parallel r_{o3}} V_{in}$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{\frac{g_{m1,2} r_{o1,2} R \cdot r_{o3}}{(R + 2r_{o1,2})(r_{o3} + \frac{1}{g_{m3}})} \cdot \frac{1}{2r_{o1,2} \parallel R + \frac{1}{g_{m3}} \parallel r_{o3}}}{\frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}} \cdot \frac{1}{2r_{o1,2} \parallel R + \frac{1}{g_{m3}} \parallel r_{o3}} + \frac{1}{r_{o4}}}$$

$$\therefore A_v = -\frac{g_{m1,2} r_{o1,2} R r_{o3} r_{o4}}{R + 2r_{o1,2}} \left\{ \frac{1}{r_{o3} r_{o4} + \left(r_{o3} + \frac{1}{g_{m3}} \right) \left(2r_{o1,2} \parallel R + \frac{1}{g_{m3}} \parallel r_{o3} \right)} \right\}$$