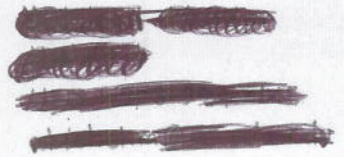



$$9 + 10 + 10 + 2 + 5 + 6 + 10 + 6 + 15$$

* Reduce ~~NO~~ marks for
small mistakes like final combining



(1) Problem 6.6

(a)

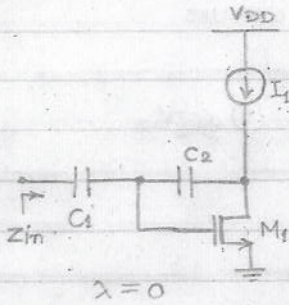


If $\lambda = 0$,
 $I_D = g_m V_1$
 $\therefore I_{in} = g_m V_1$

$$V_{in} - \frac{I_{in}}{sC_1} - V_1 = 0$$

AC equivalent circuit
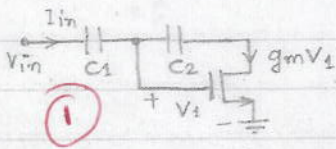
$$V_{in} - \frac{I_{in}}{sC_1} - \frac{I_{in}}{g_m} = 0$$




$$\frac{V_{in}}{I_{in}} = \frac{1}{sC_1} + \frac{1}{g_m}$$


$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{g_m + sC_1}{sC_1 g_m}$$

Eqvt ckt $\Rightarrow 1$
 correct ans $\Rightarrow 2$
 2 parts $\Rightarrow 13$
 total $\Rightarrow 3$

(b)

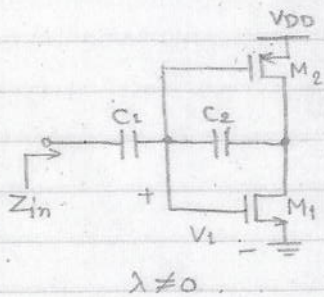

AC equivalent circuit

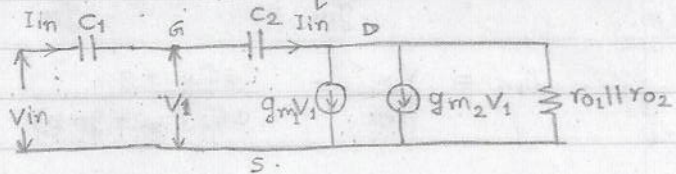

$$V_1 = V_{in} - \frac{I_{in}}{sC_1}$$

$$I_{in} = g_{m1} V_1 + g_{m2} V_1 + \frac{(V_1 - \frac{I_{in}}{sC_1})}{r_{o1} || r_{o2}}$$

$$I_{in} = (g_{m1} + g_{m2}) \left(V_{in} - \frac{I_{in}}{sC_1} \right) + \frac{1}{r_{o1} || r_{o2}} \left(V_{in} - \frac{I_{in}}{sC_1} - \frac{I_{in}}{sC_2} \right)$$


$$I_{in} \left\{ 1 + \frac{1}{sC_1} (g_{m1} + g_{m2}) + \frac{1}{r_{o1} || r_{o2}} \left(\frac{1}{sC_1} + \frac{1}{sC_2} \right) \right\}$$

$$= (g_{m1} + g_{m2} + \frac{1}{r_{o1} || r_{o2}}) V_{in}$$


$$\therefore Z_{in} = \frac{V_{in}}{I_{in}} = \frac{1 + \frac{1}{sC_1} (g_{m1} + g_{m2}) + \frac{1}{r_{o1} || r_{o2}} \left(\frac{1}{sC_1} + \frac{1}{sC_2} \right)}{g_{m1} + g_{m2} + \frac{1}{r_{o1} || r_{o2}}}$$

Eq ckt $= 1$
 correct ans $= 2$
 2 parts $\Rightarrow 13$
 total $\Rightarrow 3$

(c)

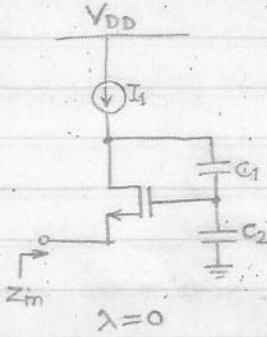

AC equivalent circuit

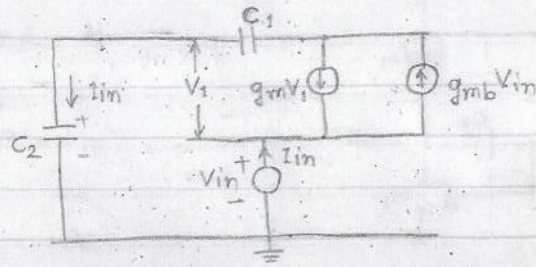

Exam Ckt \Rightarrow 1
 correct analysis \Rightarrow 2
 2 part (a) = 13
 total = 3.

$$I_{in} = -g_m V_1 + g_{mb} V_{in} \Rightarrow V_1 = \frac{-I_{in}}{g_m} + V_{in} \frac{g_{mb}}{g_m}$$


$$V_{C_2} = V_1 + V_{in} = \frac{I_{in}}{sC_2}$$

$$\therefore V_{in} + V_{in} \frac{g_{mb}}{g_m} - \frac{I_{in}}{g_m} = \frac{I_{in}}{sC_2}$$

$$\therefore V_{in} \left\{ 1 + \frac{g_{mb}}{g_m} \right\} = I_{in} \left\{ \frac{1}{g_m} + \frac{1}{sC_2} \right\}$$

$$\therefore Z_{in} = \frac{V_{in}}{I_{in}} = \frac{sC_2 + g_m}{sC_2 (g_m + g_{mb})}$$

Problem 6.8 (b)

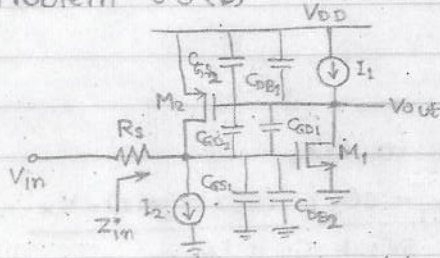


Let $C_1 = C_{gs2} + C_{db1}$

$C_2 = C_{gs1} + C_{db2}$

$C_3 = C_{gd1} + C_{gd2}$

Small signal AC equivalent model

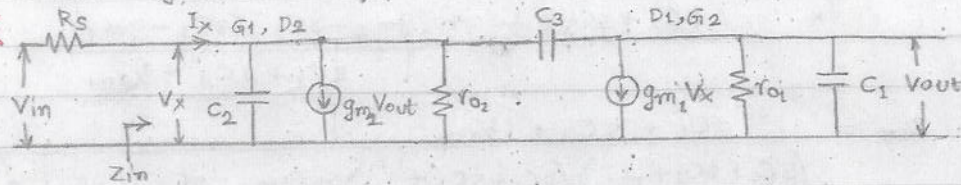

$$I_x = V_x \cdot sC_2 + g_{m2} V_{out} + \frac{V_x}{r_{o2}} + (V_x - V_{out}) sC_3 \dots (i)$$

$$V_x = V_{in} - I_x R_s \dots (ii)$$

$$V_{out} \cdot sC_1 + \frac{V_{out}}{r_{o1}} + g_{m1} V_x + (V_{out} - V_x) sC_3 = 0 \dots (iii)$$

(ii) in (i) \Rightarrow

$$\frac{V_{in} - V_x}{R_s} = V_x \cdot sC_2 + g_{m2} V_{out} + \frac{V_x}{r_{o2}} + (V_x - V_{out}) sC_3 \dots (iv)$$

$$(iii) \Rightarrow V_{out} \cdot \left\{ sC_1 + sC_3 + \frac{1}{r_{o1}} \right\} = V_x (sC_3 - g_{m1})$$

$$\therefore V_x = \frac{sC_1 + sC_3 + 1/r_{o1}}{sC_3 - g_{m1}} V_{out} \dots (v)$$

(iv) \Rightarrow

$$\frac{V_{in}}{R_s} = \left\{ sC_2 + \frac{1}{R_s} + \frac{1}{r_{o2}} + sC_3 \right\} \left\{ \frac{sC_1 + sC_3 + 1/r_{o1}}{sC_3 - g_{m1}} \right\} V_{out} + (g_{m2} - sC_3) V_{out}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{R_s} \frac{1}{\left(sC_2 + \frac{1}{R_s} + \frac{1}{r_{o2}} + sC_3 \right) \left(\frac{sC_1 + sC_3 + 1/r_{o1}}{sC_3 - g_{m1}} \right) + g_{m2} - sC_3}$$

$$\frac{V_{out}}{V_{in}} = \frac{(sC_3 - g_{m1}) / R_s}{s^2 (C_1 C_2 + C_2 C_3 + C_1 C_3) + s \left\{ (C_2 + C_3) \frac{1}{r_{o1}} + \left(\frac{1}{R_s} + \frac{1}{r_{o2}} \right) (C_1 + C_3) + (g_{m1} + g_{m2}) C_3 \right\} - g_{m1} g_{m2} + \frac{1}{r_{o1}} \left(\frac{1}{r_{o2}} + R_s \right)}$$

*Eqvt ckt \Rightarrow 1
Correct Analysis \Rightarrow 2
Total \Rightarrow 5
Give partial credit*

$$Z_{in} = \frac{V_x}{I_x}$$

Substitute for V_{out} from (v) in (i),


$$I_x = V_x \left(sC_2 + sC_3 + \frac{1}{r_{o2}} \right) + \frac{(g_{m2} - sC_3)(sC_3 - g_{m1}) \cdot V_x}{sC_1 + sC_3 + 1/r_{o1}}$$

$$\therefore Z_{in} = \frac{V_x}{I_x} = \frac{1}{sC_2 + sC_3 + \frac{1}{r_{o2}} + \frac{(g_{m2} - sC_3)(sC_3 - g_{m1})}{sC_1 + sC_3 + 1/r_{o1}}}$$

$$\therefore Z_{in} = \frac{sC_1 + sC_3 + 1/r_{o1}}{\left(sC_2 + sC_3 + \frac{1}{r_{o2}} \right) \left(sC_1 + sC_3 + \frac{1}{r_{o1}} \right) + (g_{m2} - sC_3)(sC_3 - g_{m1})}$$

$$\therefore Z_{in} = \frac{sC_1 + sC_3 + 1/r_{o1}}{s^2(C_2 + C_2C_3 + C_3) + s \left\{ \frac{1}{r_{o2}}(C_1 + C_3) + \frac{1}{r_{o1}}(C_2 + C_3) + (g_{m2} + g_{m1})C_3 \right\} - g_{m1}g_{m2} + \frac{1}{r_{o1}r_{o2}}}$$


Problem 6.8(e)

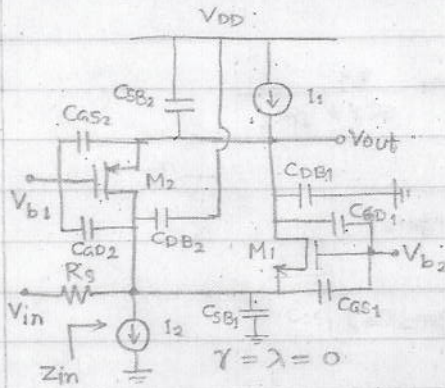

Let $C_1 = C_{DB1} + C_{GD1} + C_{SB2} + C_{GS2}$
 $C_2 = C_{GD2} + C_{DB2} + C_{SB1} + C_{GS1}$

Small signal AC equivalent model

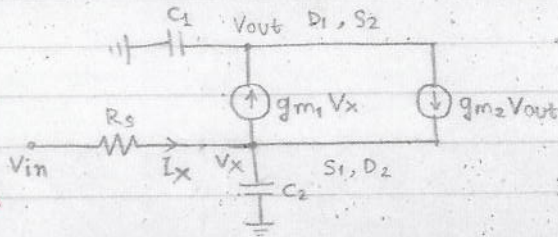Eqvt cut = 1
30011 eqm = 20
Final $\frac{V_{out}}{V_{in}} = 1$
Final $2m = 1$
total = 1.5



$V_x = V_{in} - I_x R_s \dots (i)$

$I_x = V_x \cdot sC_2 + g_{m1} V_x - g_{m2} V_{out} \dots (ii)$

$V_{out} \cdot sC_1 = g_{m1} V_x - g_{m2} V_{out}$

$\therefore V_{out} \cdot (sC_1 + g_{m2}) = g_{m1} V_x \dots (iii)$

(ii) in (i) \Rightarrow

$V_x = V_{in} - (V_x \cdot sC_2 + g_{m1} V_x - g_{m2} V_{out}) R_s$

(iii) \Rightarrow

$\frac{V_{out}}{g_{m1}} \cdot (sC_1 + g_{m2}) = V_{in} - (sC_2 + g_{m1}) R_s \cdot \frac{V_{out}}{g_{m1}} \cdot (sC_1 + g_{m2}) + g_{m2} R_s V_{out}$

$\therefore V_{out} \left\{ \frac{sC_1 + g_{m2}}{g_{m1}} + \frac{(sC_2 + g_{m1})(sC_1 + g_{m2}) R_s}{g_{m1}} - g_{m2} R_s \right\} = V_{in}$

$\frac{V_{out}}{V_{in}} = \frac{g_{m1}}{s^2 C_1 C_2 R_s + s \{ C_1 + (g_{m2} C_2 + g_{m1} C_1) R_s \} + g_{m2}}$

$Z_{in} = \frac{V_x}{I_x}$


Substitute V_{out} from (iii) in (ii),

$$I_x = V_x \cdot sC_2 + g_{m1}V_x - g_{m2} \cdot g_{m1} \frac{V_x}{sC_1 + g_{m2}}$$


$$\therefore \frac{V_x}{I_x} = \frac{sC_2 + g_{m2}}{(sC_2 + g_{m1})(sC_1 + g_{m2}) - g_{m1}g_{m2}}$$

$$\therefore Z_{in} = \frac{V_x}{I_x} = \frac{sC_2 + g_{m2}}{s^2C_1C_2 + s(g_{m1}C_1 + g_{m2}C_2)}$$

Problem 6.12

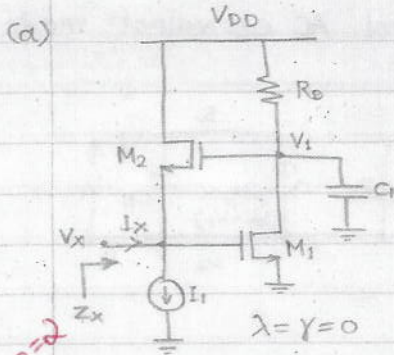

Small signal AC equivalent circuit

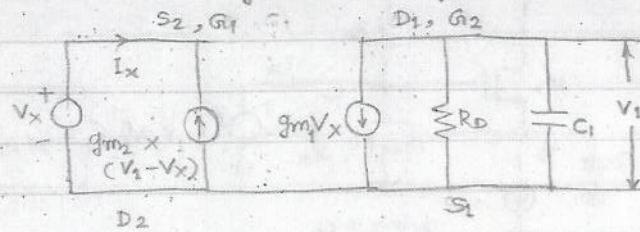

Eqvt.ckt - 1
 Basic equation m=2
 Zx = 1
 Plot - 1
 totw = 25

$$I_x = -g_{m2}(V_1 - V_x) \quad \dots (i)$$

$$g_{m2}V_x + \frac{V_1}{R_D} + V_1 \cdot s \cdot C_1 = 0$$

$$V_1 = \frac{-g_{m1}V_x}{\frac{1}{R_D} + sC_1} \quad \dots (ii)$$


(ii) in (i) \Rightarrow

$$I_x = +g_{m2}V_x + \frac{g_{m2}g_{m1}V_x}{\frac{1}{R_D} + sC_1}$$


$$\therefore Z_x = \frac{V_x}{I_x} = \frac{1}{g_{m2} + \frac{g_{m1}g_{m2}}{\frac{1}{R_D} + sC_1}} = \frac{1 + sR_D C_1}{g_{m2}(g_{m1}R_D + sR_D C_1 + 1)}$$

$$\text{At } s \rightarrow 0, Z_x = \frac{1}{g_{m2}(1 + g_{m1}R_D)}$$
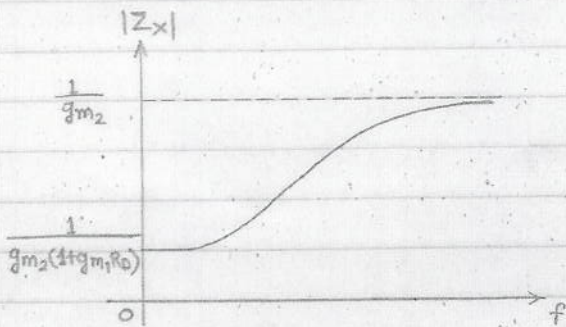
$$\text{At } s \rightarrow \infty, Z_x = \frac{1}{g_{m2}}$$



(b)

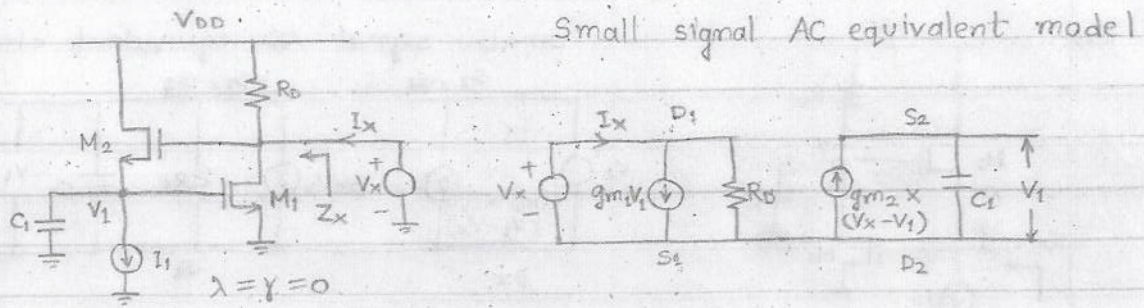

$$V_1 = \frac{g_{m2} (V_x - V_1)}{sC_1}$$

$$\therefore (sC_1 + g_{m2}) V_1 = g_{m2} V_x \quad \dots (i)$$


$$I_x = g_{m1} V_1 + \frac{V_x}{R_D}$$

$$(i) \Rightarrow I_x = g_{m1} g_{m2} \frac{V_x}{sC_1 + g_{m2}} + \frac{V_x}{R_D}$$

$$\therefore Z_x = \frac{V_x}{I_x} = \frac{(sC_1 + g_{m2}) R_D}{R_D g_{m1} g_{m2} + sC_1 + g_{m2}}$$


$$\text{At } s \rightarrow 0, Z_x = \frac{R_D}{1 + g_{m1} R_D}$$
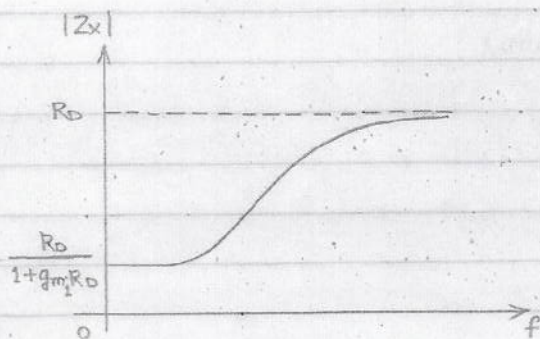
$$\text{At } s \rightarrow \infty, Z_x = R_D$$



Eqn 1 (K=1)
 Ben 11 eqn 2
 2x=1
 Plot 2/1
 Total=5

(2) Problem 7.5

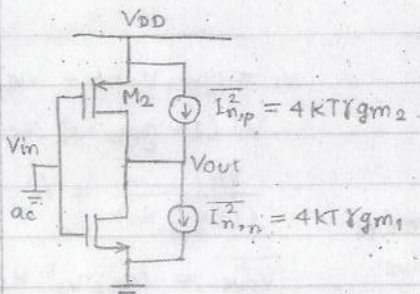

$$\overline{V_{n,out}^2} = (\overline{I_{n,p}^2} + \overline{I_{n,n}^2}) (r_{o1} \parallel r_{o2})^2$$

$$= 4KT \cdot \frac{2}{3} (g_{m1} + g_{m2}) (r_{o1} \parallel r_{o2})^2$$

$$|A_v| = (g_{m1} + g_{m2}) (r_{o1} \parallel r_{o2})$$

Input referred noise:

$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{|A_v|^2} = 4KT \left(\frac{2}{3}\right) \cdot \frac{1}{g_{m1} + g_{m2}} \quad (1)$$




$\overline{V_{n,in}^2}$ decreases with increase in g_{m2}

whereas in equation (7.59) $\overline{V_{n,in}^2} = 4KT \cdot \left(\frac{2}{3}\right) \left\{ \frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right\}$

i.e. $\overline{V_{n,in}^2}$ increases with increase in g_{m2} . (1)

Total = 3

Problem 7.6(c)

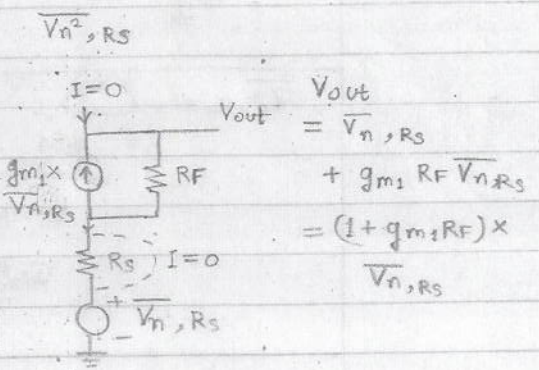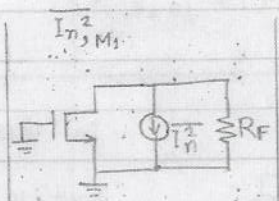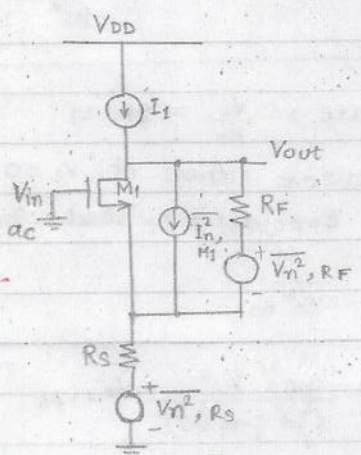

$$V_{out} = \overline{V_{n,RS}} + g_{m1} RF \overline{V_{n,RS}}$$

$$= (1 + g_{m1} RF) \overline{V_{n,RS}}$$

$$|A_v| = g_{m1} RF \quad (1)$$

$$\overline{V_{n,out}^2} = \overline{V_{n,RF}^2} + (1 + g_{m1} RF)^2 \overline{V_{n,RS}^2} + \overline{I_{n,M1}^2} \cdot RF^2$$


$$= 4KT RF + 4KT RS (1 + g_{m1} RF)^2 + 4KT \left(\frac{2}{3}\right) \cdot g_{m1} RF^2$$

Input referred noise:

$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{|A_v|^2} = \frac{4KT}{g_{m1}^2 RF} + \frac{4KT RS (1 + g_{m1} RF)^2}{g_{m1}^2 RF^2} + \frac{4KT}{g_{m1}} \left(\frac{2}{3}\right)$$

one noise comp.
 1 for gain
 1 for final amp.
 Total = 3

Problem 7-6 (F)

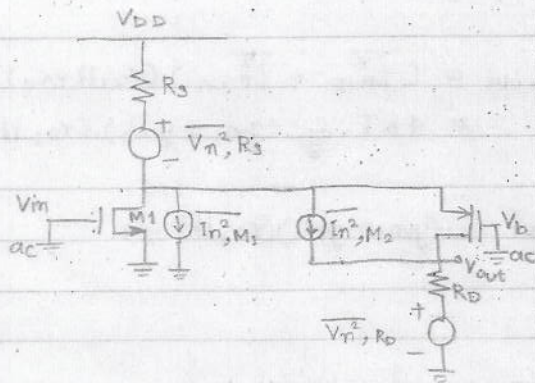




$$V_1 = -(g_{m2} V_1 R_S + V_n)$$

$$\dots V_1 (1 + g_{m2} R_S) = -V_n$$

$$\therefore \frac{-V_n}{(1 + g_{m2} R_S)} = V_1$$

$$V_{out}^2 = g_{m2}^2 V_1^2 R_D^2$$
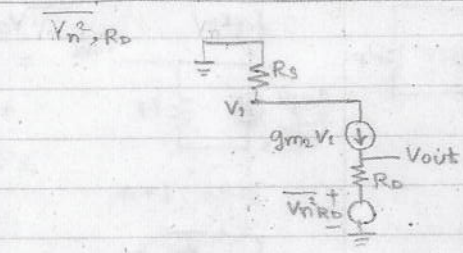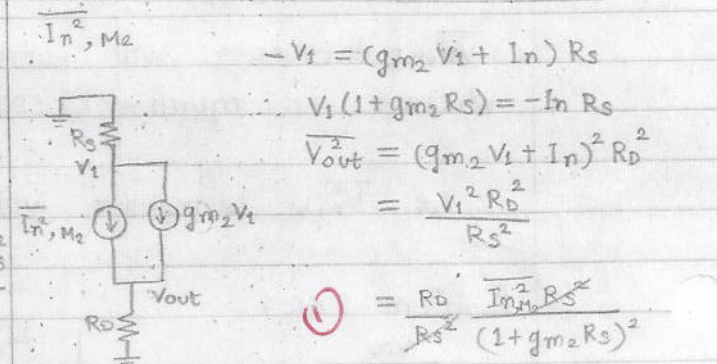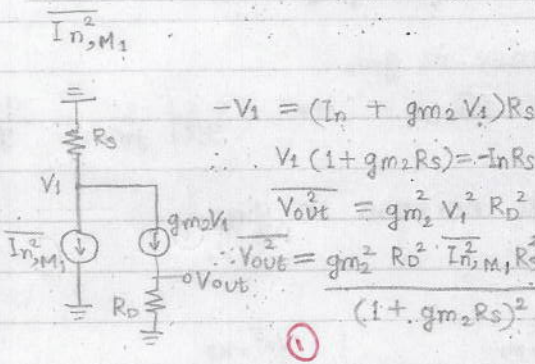
$$= \frac{g_{m2}^2 R_D^2 \overline{V_{n,R_S}^2}}{(1 + g_{m2} R_S)^2} \quad (1)$$




$$\overline{V_{n,out}^2} = \overline{V_{n,R_D}^2} + \frac{g_{m2}^2 R_D^2}{(1 + g_{m2} R_S)^2} \overline{I_{n,M_1}^2} R_S^2 + \frac{g_{m2}^2 R_D^2}{(1 + g_{m2} R_S)^2} \overline{V_{n,R_S}^2}$$

$$+ \frac{R_D}{(1 + g_{m2} R_S)^2} \overline{I_{n,M_2}^2}$$

$$\therefore \overline{V_{n,out}^2} = 4KT R_D + 4KT \left(\frac{2}{3}\right) g_{m1} \frac{g_{m2}^2 R_S^2 R_D^2}{(1 + g_{m2} R_S)^2}$$

$$+ 4KT R_S \frac{g_{m2}^2}{(1 + g_{m2} R_S)^2} R_D^2 + 4KT \left(\frac{2}{3}\right) \frac{g_{m2} R_D^2}{(1 + g_{m2} R_S)^2}$$

To calculate gain:

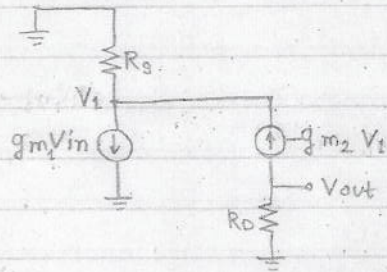

$$\frac{V_1}{R_s} + g_{m1} V_{in} = -g_{m2} V_1$$

$$V_1 \left(\frac{1}{R_s} + g_{m2} \right) = -g_{m1} V_{in}$$

$$V_{out} = -g_{m2} V_1 R_D$$

$$\therefore V_{out} = \frac{g_{m2} g_{m1} R_D \cdot V_{in}}{\left(\frac{1}{R_s} + g_{m2} \right)}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_{m1} g_{m2} R_D \cdot R_D}{(1 + g_{m2} R_s)} \quad (1)$$

Input referred noise:


$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{|A_v|^2}$$

$$\overline{V_{n,in}^2} = \frac{4kT(1 + g_{m2}R_s)^2}{g_{m1}^2 g_{m2}^2 R_D} + \frac{4kT}{g_{m1}} \left(\frac{2}{3} \right) + \frac{4kT}{g_{m1}^2 R_s} + \frac{4kT}{g_{m1}^2 g_{m2} R_s^2} \left(\frac{2}{3} \right) \quad (1)$$

total $\Rightarrow 6$

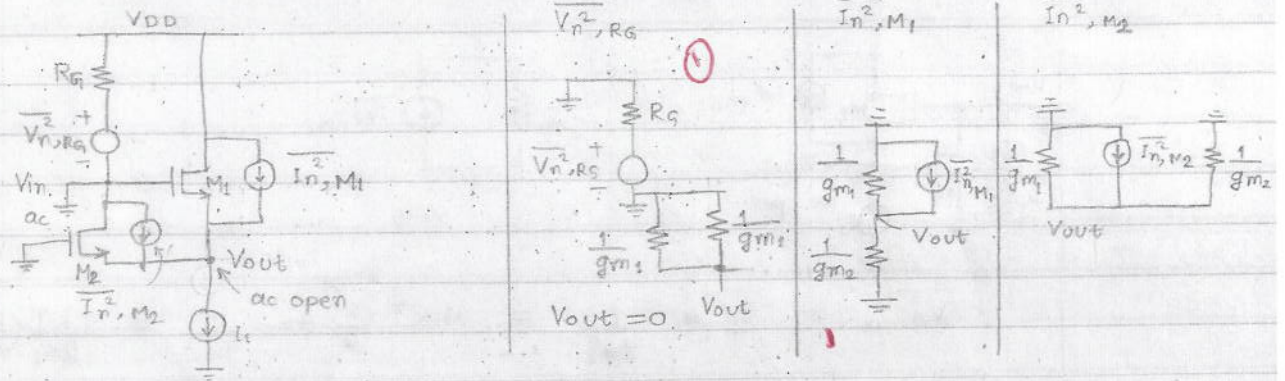
Problem 7.9(e)

For input referred noise voltage: $V_{in} = 0$



$$\begin{aligned} \overline{V_{n,out}^2} &= \overline{I_{n,M1}^2} \left(\frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}} \right)^2 + \overline{I_{n,M2}^2} \left(\frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}} \right)^2 \\ &= 4kT \cdot \frac{2}{3} g_{m1} \cdot \frac{1}{(g_{m1} + g_{m2})^2} + 4kT \cdot \frac{2}{3} g_{m2} \cdot \frac{1}{(g_{m1} + g_{m2})^2} \\ &= 4kT \cdot \frac{2}{3} \cdot \frac{1}{g_{m1} + g_{m2}} \end{aligned}$$

To calculate gain:

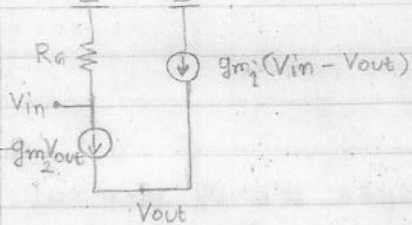


$$-g_{m2}V_{out} = -g_{m1}(V_{in} - V_{out})$$

$$g_{m2}V_{out} = g_{m1}V_{in} - g_{m1}V_{out}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{m1} + g_{m2}}$$

$$\text{Input referred noise voltage: } \overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{|A_v|^2} = 4kT \cdot \frac{2}{3} \frac{g_{m1} + g_{m2}}{g_{m1}^2}$$

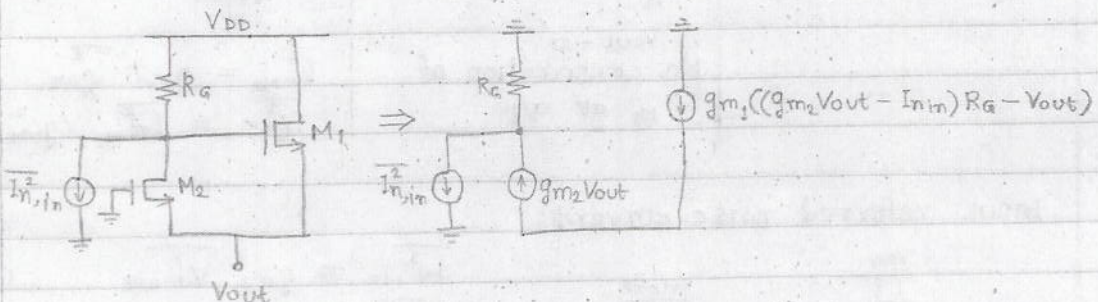
For input referred noise current: We open input terminal




$$g_{m1}((g_{m2}V_{out} - I_{n,in})R_G - V_{out}) = g_{m2}V_{out}$$

$$(g_{m1}g_{m2}R_G - g_{m1} - g_{m2})V_{out} = g_{m1}R_G I_{n,in}$$
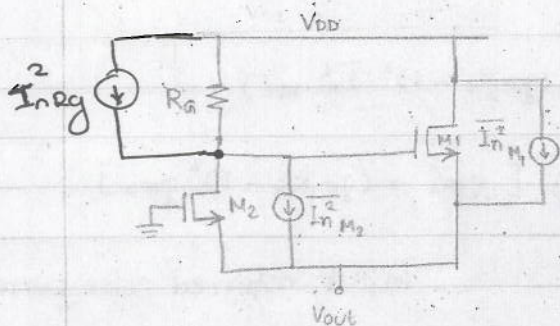
$$\overline{I_{n,in}^2} = \frac{\overline{V_{n,out}^2} (g_{m1}g_{m2}R_G - g_{m1} - g_{m2})^2}{g_{m1}^2 R_G^2} \quad \dots (i)$$



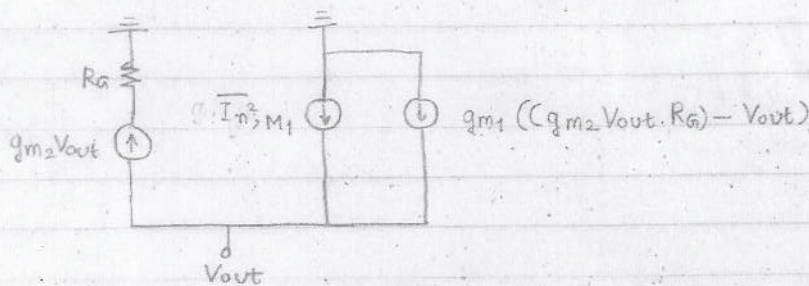Considering effect of $\overline{I_{n,M1}^2}$ on $\overline{V_{n,out}^2}$




$$g_{m2} V_{out} = I_{n,M1} + g_{m1}(g_{m2}R_G - 1) V_{out}$$

$$I_{n,M1} = (g_{m1} + g_{m2} - g_{m1}g_{m2}R_G) V_{out}$$

$$\overline{V_{n,out}^2}^I = \frac{\overline{I_{n,M1}^2}}{(g_{m1} + g_{m2} - g_{m1}g_{m2}R_G)^2} \quad (1)$$

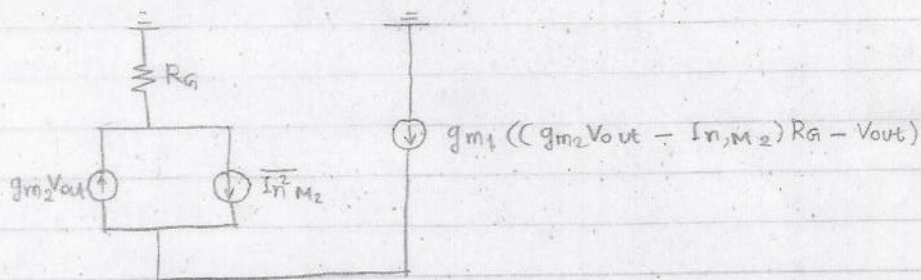Considering effect of $\overline{I_{n,M2}^2}$ on $\overline{V_{n,out}^2}$



$$R_G g_{m1} g_{m2} V_{out} - g_{m1} I_{n,M2} R_G - g_{m1} V_{out} = g_{m2} V_{out} - I_{n,M2}$$

$$V_{out} (g_{m1} g_{m2} R_G - g_{m1} - g_{m2}) = I_{n,M2} (g_{m1} R_G - 1)$$

$$\overline{V_{n,out}^2}^{II} = \frac{\overline{I_{n,M2}^2} (g_{m1} R_G - 1)^2}{(g_{m1} g_{m2} R_G - g_{m1} - g_{m2})^2} \quad (2)$$

Considering the effects of both noise sources together

$$\overline{V_{n,out}^2} = \frac{1}{(g_{m1} g_{m2} R_G - g_{m1} - g_{m2})^2} [\overline{I_{n,M1}^2} + \overline{I_{n,M2}^2} (g_{m1} R_G - 1)^2] \quad \dots (ii)$$

Put (ii) in (i),

$$\therefore \bar{I}_{n, in}^2 = \frac{1}{g_{m1}^2 R_G^2} (\bar{I}_{n, M1}^2 + (g_{m1} R_G - 1)^2 \bar{I}_{n, M2}^2)$$

$$\therefore I_{n, in}^2 = \frac{1}{g_{m1}^2 R_G^2} 4kT \left(\frac{2}{3}\right) [g_{m1} + (g_{m1} R_G - 1)^2 g_{m2}]$$

∴ input referred noise current

Input referred contribution due to $I_{n, R_G}^2 = I_{n, R_G}^2$ ①


total = 10.

So total input referred noise current

$$\Rightarrow \frac{4kT}{R_G} + \frac{1}{g_{m1}^2 R_G^2} 4kT \cdot \frac{2}{3} (g_{m1} + (g_{m1} R_G - 1)^2 g_{m2})$$
 ①

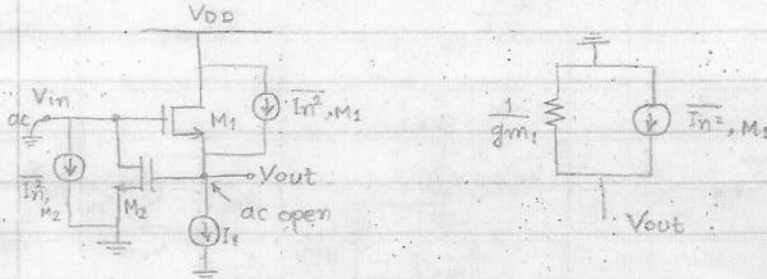(3) Problem 7.9(f)


For input referred noise voltage: $V_{in} = 0$.



Noise due to $M_2 = 0$ (1)

$$\overline{V_{n,out}^2} = \overline{I_{n^2, M_1}^2} \cdot \frac{1}{g_{m_1}^2} = 4kT \frac{2}{3} g_{m_1} \cdot \frac{1}{g_{m_1}^2} = \frac{4kT}{g_{m_1}} \left(\frac{2}{3}\right) \quad (1)$$

To calculate gain:

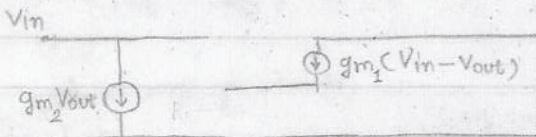

$$g_{m_1} (V_{in} - V_{out}) = 0$$

$$V_{in} = V_{out}$$




$$A_v = 1 \quad (1)$$

Input referred noise voltage:


$$\overline{V_{n,in}^2} = \overline{V_{n,out}^2} = \frac{4kT}{g_{m_1}} \left(\frac{2}{3}\right) \quad (1)$$

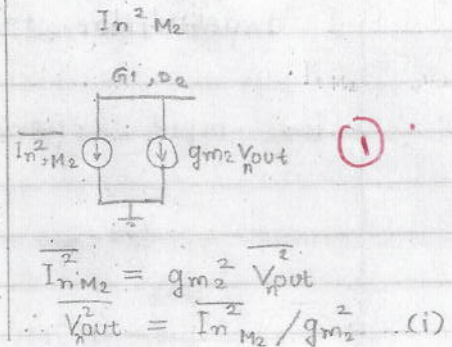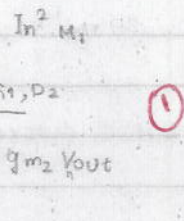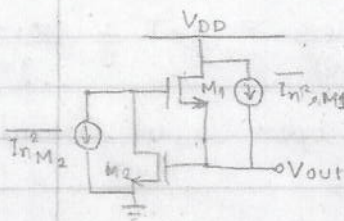(2)

For input referred current: We open the V_p terminal



Input referred noise current:

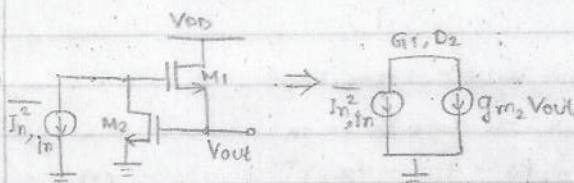

$$\overline{I_{n,in}^2} = g_{m_2}^2 \overline{V_{n,out}^2} \quad (ii)$$

$$\overline{I_{n,in}^2} = \overline{I_{n^2, M_2}^2} = 4kT \frac{2}{3} g_{m_2} \quad (1)$$

④ NMOS param

$$V_{th} = 0.476$$

$$\mu n \mu_{ox} = 248 \text{ cm}^2/\text{Vs}$$

PMOS param

$$V_{th} = 0.488$$

$$\mu p \mu_{ox} = 102 \text{ cm}^2/\text{Vs}$$

① $I_1 = I_2 = I_3 = 150 \mu\text{A}$

$$\frac{1}{2} \cdot \mu n \mu_{ox} \frac{W}{L} \cdot (0.15)^2 = 150 \mu\text{A}$$

① $W_{1,2,3} = 9.67 \mu\text{m}$

②

$$V_{b1}$$

Simulation

For M_2 to be in saturation its drain voltage has to be greater than $0.8 - V_{th}$.

$$\Rightarrow V_{b1} = V_{th} + V_{DD, M3} + 0.8 - V_{th}$$

① $= 0.95 \text{V}$

Total $\Rightarrow 7 + 8 = 15$

$$V_{b2}$$

$$V_{DD, M4,5,6} = \sqrt{\frac{2 \times 150}{102 \times \frac{30}{0.18}}} = \sqrt{\frac{2I}{\mu n \mu_{ox} W/L}}$$

$$= 0.133 \text{V}$$

For M_5 to be in saturation

$$V_{b2 \text{ max}} = V_{DD} - \frac{3}{2} V_{DD, M5} + V_{DD, M4} + |V_{thp}|$$

① $= 1.046 \text{V}$

Simulation

- ① Netlist $\Rightarrow 1$
- ② Proper setup for gain & offset $\Rightarrow 3$
- ③ Results $\Rightarrow 4$

Swing

$$V_{out\ min} = (0.8 - V_{th}) + 0.15 = 0.474$$

$$V_{out\ max} = V_{DD} - 2 \times 0.133 = 1.534$$

① maximum swing = 1.06V

② mirror pole is at

$$= \frac{g_{m6}}{C_{gs5} + C_{gs6} + C_{db6} + C_{db1}} \approx \frac{g_{m6}}{2C_{gs5}}$$

③


$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 8.6 \text{ fF}/\mu\text{m}^2$$

$$C_{gs5} \approx \frac{2}{3} C_{ox} W L = 31 \text{ fF}$$

$$g_{m6} = \sqrt{2 \times \mu_n C_{ox} \frac{W}{L} I} = 2.25 \text{ mS}$$

mirror pole = 3.52×10^{10} rad/s


④ $G_{m1} = G_{m\text{out}}$

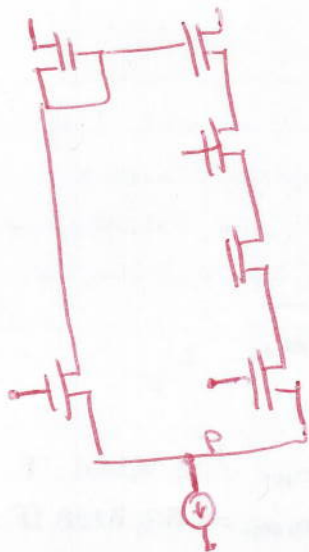


Assuming virtual ground at P

$$G_m = g_{m1,2} = \sqrt{2 \times \mu_n C_{ox} \frac{W}{L} I_D} = 2 \text{ mS}$$

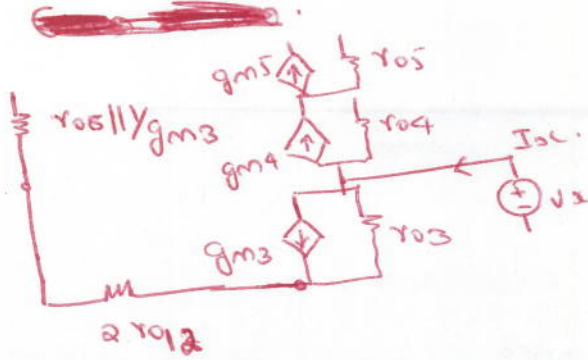~~Output~~
~~=~~
~~1~~
~~100 fF~~
~~100 fF~~
~~100 fF~~



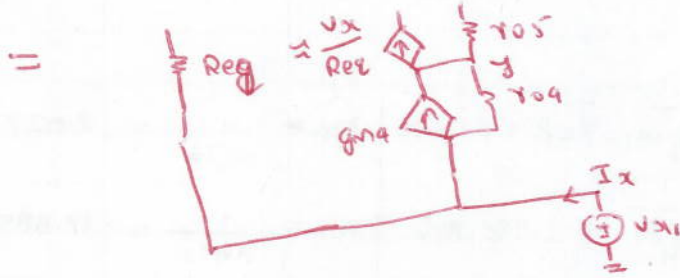Req = $[2r_{o1,2} + r_{o6} \parallel g_{m6}] g_{m3} r_{o3}$
 $\approx 2r_{o1,2} g_{m3} r_{o3}$



At y.

$$\frac{V_x}{Req} + \frac{V_y}{r_{o5}} = g_{m4}(0 - V_y) + \frac{(V_{DC} - V_y)}{r_{o4}}$$

$$V_y \left(\frac{1}{r_{o5}} + \frac{1}{r_{o4}} + g_{m4} \right) = \frac{V_x}{r_{o4}} - \frac{V_x}{Req}$$

$\approx \frac{V_x}{r_{o4}}$

$$V_y g_{m4}$$

$$V_y = \frac{V_x}{g_{m4} r_{o4}}$$

$$I_{DC} = \frac{2V_{DC}}{Req} + \frac{V_y}{r_{o5}}$$

$$= \frac{V_x}{g_{m3} r_{o3} r_{o1,2}} + \frac{V_x}{g_{m4} r_{o4} r_{o5}}$$

$$R_{out} = g_{m3} r_{o3} r_{o1,2} \parallel g_{m4} r_{o4} r_{o5}$$

$$\approx 2m \parallel \frac{1}{63H} \approx 2.25m \parallel \frac{1}{(58H)^2}$$

(1)

$$= 503k \parallel 669k = 287k \Rightarrow \text{Gain } \approx 560$$

u_{gb}

Circuit has one dominant pole at o/p given by
 $\frac{1}{R_{out} C_L}$ rad/s. Assuming single pole roll off with
this dominant pole.

$$u_{GB} = g_m R_{out} = \frac{1}{R_{out} C_L}$$

① $= \frac{g_m}{C_L} \Rightarrow \frac{2\pi}{1P}$

$\Rightarrow 2$ rad/s.