


# EE 215D

## Midterm Exam

Spring 2003



Name: ..... *Solutions* .....

 **Time Limit: 2 Hours**  
**Open Book, Open Notes**






  
1. Two unity-gain samplers appear in a pipeline as shown below. When the first stage is in the acquisition mode, the second is in the hold mode and vice versa. Suppose  $V_{in} = 1\text{ V}$  and model the op amp as shown below. With the initial condition shown in the second stage, determine the time it takes  $V_{out}$  to reach within 0.1% of its final value. You can assume the second op amp creates a good virtual ground at its inverting input in this mode. Sketch the waveform for  $V_{out}$  as the first stage goes from sampling to hold. Assume  $C_1 = C_2 = 1\text{ pF}$ . (5)



Hold mode :

 

at  $V_{in} = -2\text{ V}$ .

 


$$V_{in} = V_{out} - 1$$

$V_{out}$  reaches 0.75 V at 1.75 nsec

where  $V_{in} = -0.25\text{ V}$ .


at this point  $V_{out}$  starts to

\* linearly settle to its final value.

 

$$V_{in} = V_{out} - 1$$

$$V_{out}(0) = 0.75\text{ V}$$

 

$$-G_m(V_{out} - 1) = \frac{V_{out}}{R_{out}} + C_2 \frac{dV_{out}}{dt}$$

$$\therefore \left(-G_m - \frac{1}{R_{out}}\right)V_{out} + G_m = C_2 \frac{dV_{out}}{dt}$$

$$G_m = 0.02$$

$$R_{out} = 50 \text{ k}$$

$$C_2 = 1 \text{ pF}$$

$$\therefore C_2 \frac{dV_{out}}{dt} + \left(G_m + \frac{1}{R_{out}}\right) V_{out} = + G_m \cdot 1 \quad \text{--- (1)}$$

$$V_{out}(0) = 0.75$$

Solving Eqn (1)

$$\therefore V_{out}(t) = \frac{G_m \cdot 1}{G_m + \frac{1}{R_{out}}} + \left( \frac{-G_m}{G_m + \frac{1}{R_{out}}} + \overset{V_{out}(0)}{\downarrow} 0.75 \right) e^{-\frac{t}{C_2} \cdot \left(G_m + \frac{1}{R_{out}}\right)}$$

$$V_{out}(\infty) = \frac{G_m}{G_m + \frac{1}{R_{out}}} = 0.999 \text{ v.}$$


$$\therefore \text{Error} = 0.1\% V_{out}(\infty) \approx 0.999 \text{ mV.} = 0.249 e^{-\frac{t_2}{C_2} \left(G_m + \frac{1}{R_{out}}\right)}$$

$$\therefore t_2 = 0.2758 \text{ nsec}$$

$\therefore$  The time it takes  $V_{out}$  to reach 0.1% of its final value =

$$t_1 + t_2 = 1.75 + 0.2758 = \boxed{2.0258 \text{ nsec}}$$

 2. A resistor-ladder DAC incorporates MOS switches as resistors in a secondary ladder. The diagram below shows how the secondary ladder slides up and down along the primary one. Is this DAC monotonic for any value of the MOS on-resistance,  $R_{on}$ ? Why or why not? Use detailed analysis to support your claim. (5)



$x, y$  are the same point but in two diff. situations :

$$V_x = \frac{(j-1)r + r // (nR_{on})}{(n-1)r + r // (nR_{on})}, \quad V_y = \frac{j r}{(n-1)r + r // nR_{on}}$$

to be monotonic  $\rightarrow V_x \leq V_y$

$$\therefore (j-1)r + r // (nR_{on}) \leq j r$$

$$\rightarrow r // (nR_{on}) \leq r$$

which is always true for any value of  $R_{on}$ .

$\rightarrow$  This DAC is unconditionally monotonic for any value of  $R_{on}$ .




3. Consider the two nominally-equal capacitors shown below. The initial condition at node  $X$  is zero.

(a) Assuming each capacitor can be expressed as  $C = C_0(1 + \alpha_1 V)$ , determine the value of  $V_X$  after the transitions shown in the figure occur.

(b) Repeat part (a) if  $C = C_0(1 + \alpha_1 V + \alpha_2 V^2)$ .

(5)

 

From conservation of charge  $\rightarrow q_1 = q_2$

$$\therefore \int_0^{V_0 - V_X} C_1 dV_1 = \int_0^{V_X - (-V_0)} C_2 dV_2$$

$$\therefore C_0 \left( (V_0 - V_X) + \frac{\alpha_1}{2} (V_0 - V_X)^2 \right) = C_0 \left( (V_X + V_0) + \frac{\alpha_1}{2} (V_0 + V_X)^2 \right)$$

$$\therefore 2(\alpha_1 V_0 + 1) V_X = 0 \rightarrow \boxed{V_X = 0}$$

(b) if  $C = C_0(1 + \alpha_1 V + \alpha_2 V^2)$

similarly,

$$\therefore C_0 \left[ (V_0 - V_X) + \frac{\alpha_1}{2} (V_0 - V_X)^2 + \frac{\alpha_2}{3} (V_0 - V_X)^3 \right] = C_0 \left[ (V_X + V_0) + \frac{\alpha_1}{2} (V_X + V_0)^2 + \frac{\alpha_2}{3} (V_X + V_0)^3 \right]$$

$$\therefore V_X \left( 1 + \alpha_1 V_0 + \alpha_2 V_0^2 + \frac{\alpha_2}{3} V_X^2 \right) = 0$$

$$\therefore \boxed{V_X = 0} \quad \text{or} \quad V_X^2 = -\frac{3}{\alpha_2} (1 + \alpha_1 V_0 + \alpha_2 V_0^2)$$







4. Consider a 10-bit two-step ADC similar to that in Homework #4. Each stage resolves 5 bits and the subtractor has a voltage gain of unity. The reference voltage for the first-stage ladder is nominally equal to 1024 LSB and that for the second-stage ladder equal to 32 LSB.

(a) Suppose the reference voltage for the first-stage ladder is accidentally chosen to be 2048 LSB but that for the second stage is still equal to 32 LSB. Plot the residue and the overall input-output characteristic and determine critical errors. Assume DAC output varies between 0 and 1024 LSB.

(b) Suppose the reference voltage for the second-stage ladder is accidentally chosen to be 64 LSB but that for the first stage is still equal to 1024 LSB. Plot the residue and the overall input-output characteristic and determine critical errors.



(5)

  (a) If the reference voltage of 1<sup>st</sup> stage is 2048 LSB



$$DNL = 32 \text{ LSB}$$

  (b) ref. voltage of the 2<sup>nd</sup> stage ladder = 64 LSB



$$DNL = 1 \text{ LSB}$$