

Homework #1

Due Thur., April 12, 2012

Problems 12.10, 12.11, 12.12, 12.15, 12.16, and 12.21 of analog CMOS book. In 12.12, assume all of the switches are NMOS devices.

Chapter 12 is also available at:

<http://www.ee.ucla.edu/~brweb/teaching.html>

It is called AIC_Ch12.