 


EE 215D

Midterm Exam

Spring 2012

Name: *Solutions*



1. 10

2. 10

3. 10

4. 10


Total: 40

1. Consider the bootstrapped sampling circuit shown below, where the body of M_1 is tied to ground and the rest of the bootstrap network is not shown.


(a) If body effect is not neglected, *sketch* the on-resistance of M_1 as a function of V_{in} . You need not write equations.

(b) Approximating the characteristic in (a) by a straight line passing through its end points, sketch R_{on} as a function of time. Assume $V_{in}(t) = V_0 \cos \omega_0 t + V_0$.

 
(c) Calculate the second harmonic amplitude at the output arising from phase distortion. Assume that the phase shift is much less than 1 radian.



 
a)
$$R_{on} = \frac{1}{k \frac{W}{L} \left\{ V_{GS} - V_{th0} - \gamma (\sqrt{\phi + V_{SB}} - \sqrt{\phi}) \right\}}$$
 $\nabla V_{SB} = V_{in}$



 $V_{th} \uparrow$ as $V_{in} \uparrow$ and
hence, R_{on} increases


 
$$R_{on} = R_0 + \alpha (V_0 + V_0 \cos \omega_0 t)$$



c)

$$V_{out} \approx V_0 + V_0 \cos(\omega_0 t - \tan^{-1}(\omega_0 R_{on} C_H))$$

$$\approx V_0 + V_0 \cos(\omega_0 t - \omega_0 R_{on} C_H)$$

$$\approx V_0 + V_0 \cos(\omega_0 t) + V_0 \sin(\omega_0 t) \{ \omega_0 R_{on} C_H \}$$

$$(\text{for } \omega_0 R_{on} C_H \ll 1 \text{ rad})$$

$$= V_0 + V_0 \cos(\omega_0 t) + V_0 \sin(\omega_0 t) \{ \omega_0 R_0 C_H + \omega_0 \alpha V_0 C_H \}$$

$$+ \frac{1}{2} V_0^2 \alpha \omega_0 C_H \sin(2\omega_0 t)$$

2nd Harmonic Amplitude \rightarrow

$$\boxed{\frac{1}{2} V_0^2 \alpha \omega_0 C_H}$$


where α is given by

$$R_{on} = R_0 + \alpha V_{in}$$

2. A segmented current-steering DAC consists of N current sources and is followed by a transimpedance amplifier as shown below. Assume the op amp has a gain of A_1 but is otherwise ideal.

(a) Estimate the INL at node X . (1pt)

 (b) Estimate the INL at the output. (3pt)



$$V_{out} = -A_1 V_X$$

KCL at Node X when n switches are on;

$$\frac{V_{out} - V_X(n)}{R_F} = n I_u + n \frac{V_X}{r_o}$$

$$\Rightarrow V_X(n) = - \frac{n I_u r_o R_F}{n R_F + (A_1 + 1) r_o}$$

$$\therefore V_X(0) = 0, V_X(N) = - \frac{N I_u r_o R_F}{N R_F + (A_1 + 1) r_o}$$

$$\Rightarrow V_{X, ideal}(n) = - \frac{n I_u r_o R_F}{N R_F + (A_1 + 1) r_o}$$

$$(a) INL_X(n) = V_X(n) - V_{X, ideal}(n) = \frac{I_u r_o R_F^2}{N R_F + (A_1 + 1) r_o} \cdot \frac{n(n-N)}{n R_F + (A_1 + 1) r_o}$$

(b) Since $V_{out} = -A_1 V_X$


$$INL_{out}(n) = -A_1 \cdot INL_X(n) = \frac{A_1 I_u r_o R_F^2}{N R_F + (A_1 + 1) r_o} \cdot \frac{n(N-n)}{n R_F + (A_1 + 1) r_o}$$

3. Consider the flash ADC shown below. Assume V_{in} is provided by an ideal voltage source.

(a) If the kickback noise currents of all comparators are equal and denoted by $I(t)$, determine the largest perturbation voltage on the ladder. Assume $I(t)$ is small.

(b) Now assume that V_{in} is provided through a source impedance of R_S . Compute the differential voltage experienced by the comparator tied to $V_{REF}/2$. Assume that the kickback noise currents drawn by the two inputs of each comparator are equal.

 (c) Suppose we choose the total ladder resistance equal to $8R_S$. Which comparator does now experience the largest differential error?



(a) The perturbation at node j :

$$\Delta V_j = -\frac{I}{2} \cdot R_u \cdot (j(N-j))$$

$$\Rightarrow \frac{\partial \Delta V_j}{\partial j} = 0 \Rightarrow j = \frac{N}{2}$$

$$\text{and } \Delta V_{\max} = -\frac{I}{8} \cdot R_u \cdot N^2$$

(b) The perturbation at input is $-I \cdot N \cdot R_S$

Diff. voltage at $j = \frac{N}{2}$:

$$-I \cdot N \cdot R_S + \frac{I}{8} \cdot R_u \cdot N^2 = -I \cdot N \left(R_S - \frac{R_u \cdot N}{8} \right)$$

(c) With $R_u = \frac{8R_S}{N}$,

Differential error is $-I \cdot N \cdot R_S + \frac{I}{2} \cdot \frac{8R_S}{N} (j(N-j))$

$$= I \cdot R_S \left(-N + \frac{4(j(N-j))}{N} \right) = f(j), \quad j = 0 \sim N-1$$

$$\frac{\partial f(j)}{\partial j} = 0 \Rightarrow j = \frac{N}{2}, \quad \text{but } f\left(\frac{N}{2}\right) = 0$$

\Rightarrow The first and the last comparator experience the largest error.

4. Consider the 10-bit two-step ADC studied in Homework 4, where each stage resolves 5 bits. Assume that the DAC employs a resistor ladder as shown below. Analyze the following two cases independently.

(a) Suppose the outputs of NAND gates j and $j + 1$ are accidentally swapped. Construct the residue plot and the input/output characteristic.

(a) Suppose the outputs of NAND gates j and $j + 2$ are accidentally swapped. Construct the residue plot and the input/output characteristic.

