

# EE215C

## Final Exam

Winter 2009

Name: ..... *Solutions* .....

**Time Limit: 3 Hours**

**Open Book, Open Notes**

1. 20


2. 10

3. 10

4. 10

5. 15


Total: 65

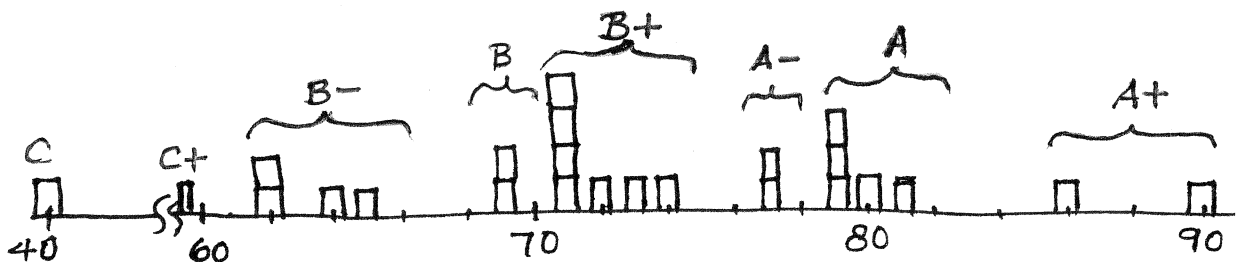

1. Consider the active mixer shown below, where all other capacitances are neglected and no transistor enters the triode region. Also, channel-length modulation and body effect are negligible.

(a) Suppose  $M_2$  is on and  $M_3$  is off. Derive an expression for the small-signal drain current of  $M_2$  due to the thermal noise of  $M_2$ . Plot the spectrum of the drain current. Neglect all other sources of noise.

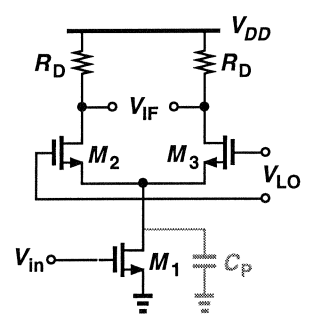
(b) Now suppose the impedance of  $C_P$  is much larger than  $1/g_{m2}$  at the frequencies of interest, and the LO is applied with 50% duty cycle. If  $M_2$  and  $M_3$  switch abruptly, and only the first and third harmonics of the LO are considered, explain in detail how the thermal noise of  $M_2$  appears at IF. Sketch the IF noise spectrum due to the first and third harmonics of the LO. Neglect all other sources of noise.




$$\overline{i_{dn}}^2 = 4kTg_{m2} \left| \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{sC_P}} \right|^2$$

$$= 4kTg_{m2} \frac{\omega^2 C_P^2}{\omega^2 C_P^2 + g_{m2}^2} \quad (6)$$


spectrum:

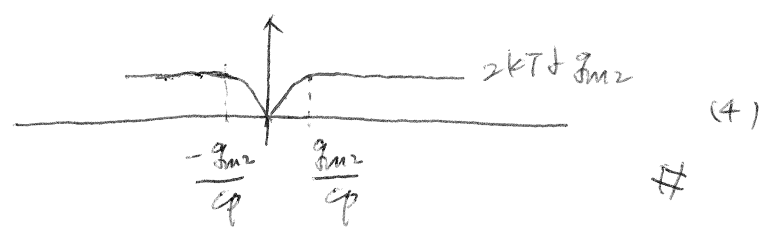


b) time domain: square wave x noise

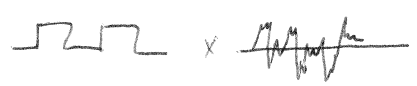

⇒ frequency domain:

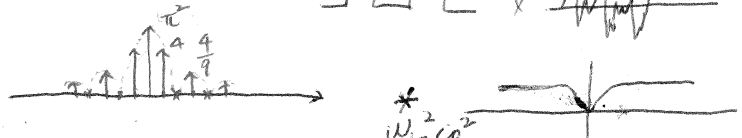

for  $+f_{lo}$

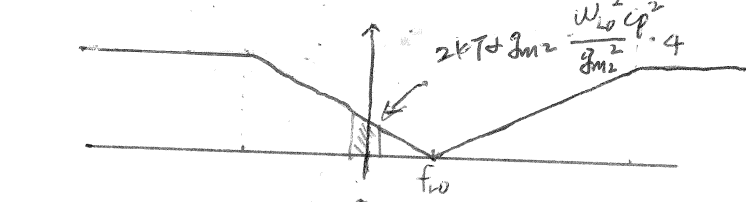


$$\frac{1}{\omega C_P} \gg \frac{1}{g_{m2}}$$


$$\Rightarrow \omega C_P \ll g_{m2}$$

$$\overline{i_{dn}}^2 = 4kTg_{m2} \frac{(\omega C_P)^2}{g_{m2}^2}$$


for  $-f_{lo}$

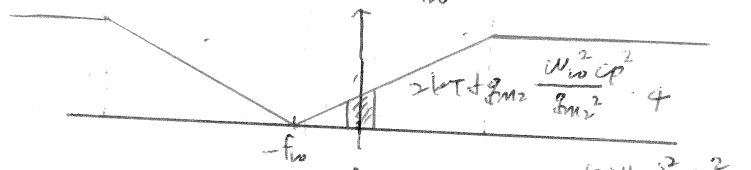

for  $3f_{lo}$

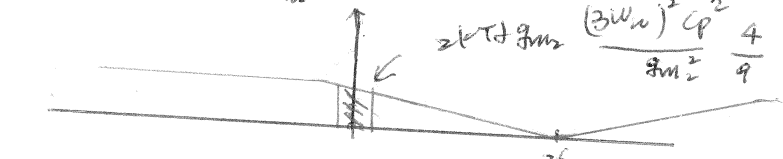

for  $-3f_{lo}$

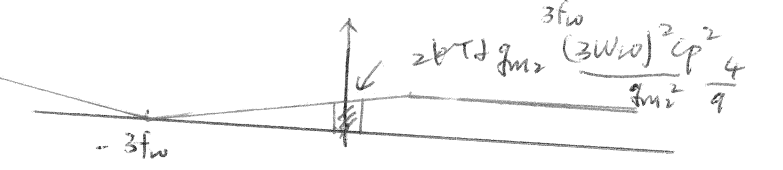

∴ the total noise at IF  $\approx 2kTg_{m2} \frac{\omega_{lo}^2 C_P^2}{g_{m2}^2} \cdot 16$  #



the 3rd harmonic contributes the same noise as the 1st one


2. A student considers the arrangement shown on the left, where  $C_{GS}$  introduces LO leakage at the input and hence a dc component at the output. (Note that the capacitor does not carry a dc current.) The student then decides that the arrangement on the right is *free* from dc offsets, reasoning that a dc voltage,  $V_{ds}$ , at the output would require a dc current,  $V_{dc}/R_L$ , through  $R_L$  and hence an equal current through  $R_S$ . But this is impossible because a dc current through  $R_S$  gives rise to a negative voltage at node  $X$ .

5

(a) Explain in detail whether the student's conjecture is correct and why.

5

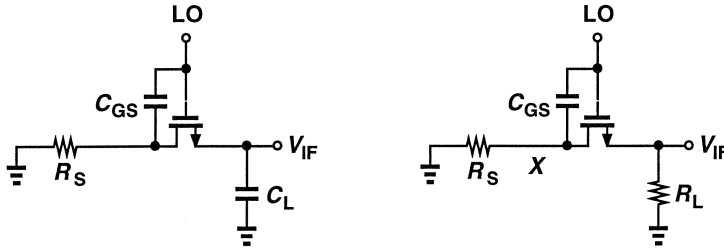
(b) Neglecting  $C_{GS}$ , calculate the voltage conversion gain of the circuit on the right. Assume a square-wave LO with 50% duty cycle. Also, assume the switch has an on-resistance of  $R_{on}$ .



(a) The flaw in the student's reasoning is that a dc current at the output requires a dc current at the input. In other words, KCL only holds for all of the frequency components summed together - not for each individual component. Thus, both circuits suffer from dc offsets.

(b) The mixer operates as an ideal return-to-zero topology, except that  $R_{on}$  and  $R_L$  attenuate the signal when the switch is on. That is, the input signal is multiplied by a square wave toggling between 0 and  $\frac{R_L}{R_L + R_{on} + R_S}$ . The conversion gain is therefore equal to  $\frac{1}{\pi} \frac{R_L}{R_L + R_{on} + R_S}$ .

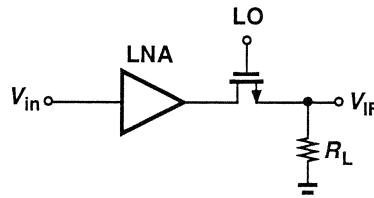3. Shown below is part of a direct-conversion receiver. Suppose the LNA input-output characteristic can be expressed as  $y(t) = \alpha_1 x(t) + \alpha_2 x^2(t)$ . If the mixer switches abruptly with a 50% duty cycle and if  $R_L$  is much greater than the on-resistance of the switch and the output resistance of the LNA, compute the  $IP_2$  of the receiver.



The LO signal can be represented as  $\frac{1}{2} + \sum_{n=1}^{\infty} \frac{2}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\omega t)$

for a two tone test we have  $V_{in} = A(\cos \omega_1 t + \cos \omega_2 t)$

$\therefore$  we have  $V_{IF} = \left[ \alpha_1 A (\cos \omega_1 t + \cos \omega_2 t) + \alpha_2 A^2 (\cos \omega_1 t + \cos \omega_2 t)^2 \right] \left[ \frac{1}{2} + \frac{2}{\pi} \cos(\omega_{LO} t) + \dots \right]$

for  $\omega_2$  slightly higher than  $\omega_1$ ,  $(\omega_2 - \omega_1)$  component at the output of the LNA appears at the output of the mixer multiplied by its DC gain and located close to DC.

$\omega_2 - \omega_1$ : @ LO output  $\alpha_2 A^2 \cos(\omega_2 - \omega_1)$

@ Mixer output  $\frac{1}{2} \alpha_2 A^2 \cos(\omega_2 - \omega_1)$

This resides in the same band as the converted RF signal  $\frac{\alpha_1 A}{\pi}$


At the  $IP_2$  point  $\frac{\alpha_1 A_{IP_2}}{\pi} = \frac{\alpha_2 A_{IP_2}^2}{2}$

$\therefore A_{IP_2} = \frac{\alpha_1}{\alpha_2} \frac{2}{\pi}$


4. Consider the simple type-I PLL shown below. Assume the loop is locked.

(a) If the input frequency is known, describe in detail how you compute the control voltage and the phase error (between the two inputs of the PD).

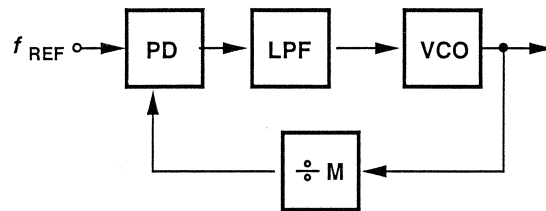(b) If the input frequency changes by  $\Delta\omega$ , compute the change in the phase error.




(a)

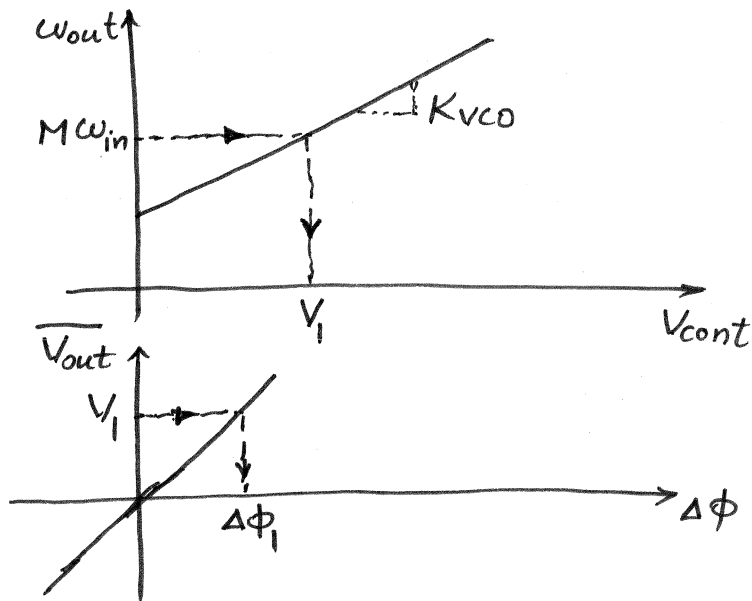

(b) If the input frequency changes by  $\Delta\omega$ ,  $\omega_{out}$  changes by  $M\Delta\omega$  and the control voltage by  $\frac{M\Delta\omega}{K_{VCO}}$ . Thus, the input phase error changes by  $\frac{M\Delta\omega}{K_{VCO}K_{PD}}$ .

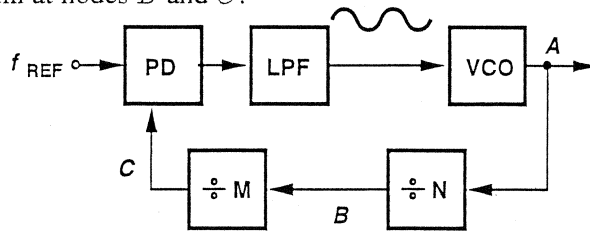5. A type-I PLL is shown below, where the control voltage experiences a sinusoidal ripple with a frequency of  $f_{REF}$  and a peak amplitude of  $V_r$ . Assume the loop is locked.

- Explain the difference between a harmonic and a sideband.
- Using the narrow-band FM approximation, determine the spectrum at point A.
- Now determine the spectrum at nodes B and C.



(a) HARMONICS - A frequency component in a spectrum that is an integer multiple of the fundamental frequency. Appears when a sinusoid is applied to a non-linear system.

SIDEBANDS - Deterministic frequency component that appears around the carrier frequency. A generic example are tones produced by a modulation process of the original signal.

(b) (NOTE) Narrowband FM Approx.


$$x_{FM}(t) = A_c \cos \left[ \omega_c t + m \int_{-\infty}^t x_{BB}(t) dt \right] \approx A_c \cos \omega_c t - A_c \sin \omega_c t \int x_{BB}(t) dt.$$

given  $x_{BB}(t) = V_r \cos(\omega_{REF} t)$ ,  $\omega_{REF} = 2\pi f_{REF}$

$$x_{FM}(t) \approx A_c \cos(\omega_c t) - \frac{A_c V_r m}{\omega_{REF}} \sin(\omega_c t) \sin(\omega_{REF} t)$$

$$= A_c \cos(\omega_c t) - \frac{A_c V_r m}{2\omega_{REF}} \cos(\omega_c - \omega_{REF})t + \frac{A_c V_r m}{2\omega_{REF}} \cos(\omega_c + \omega_{REF})t$$

(SPECTRUM @ A)

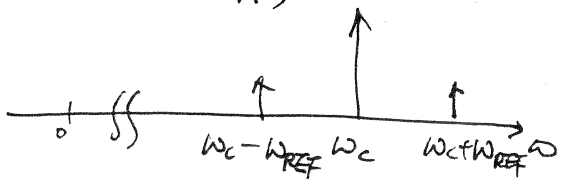


(c) When FM modulated signal is applied to a divider, ( $\div N$ )

fundamental: freq  $\div N$

sideband: Amp  $\div N$

$$x_{FM} = A_c \cos \left( \omega_c t + m \int x_{BB}(t) dt \right) \div N$$

$\therefore$  @ B

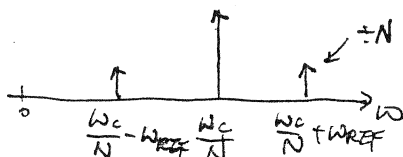

@ C

