

Sample HW solution

EE215C Homework 1

Problem 2:

(a)

1: 15
2: 35

Current mirror provides $I=2.5\text{mA}$ for M1. I applied $I=2.5\text{mA}$ with an ideal current source and by sweeping the W1 from $20\mu\text{M}$ to $100\mu\text{M}$ I found voltage at input node. Next I change I to 2.6mA and repeat the same steps. This gives me ΔV for different W1 values and since $\Delta I = 0.1\text{mA}$ and resistance is $50\ \Omega$, I selected the W1 that has ΔV equals to 5mV .

$$I_1 = 2.5\text{mA}, I_2 = 2.6\text{mA} \Rightarrow \Delta I = 0.1\text{mA}$$

$$R_{in} = \frac{1}{g_m + g_{mb}} = 50\ \Omega$$

$$\Rightarrow \Delta V = R_{in} \times \Delta I = 5\text{mV}$$

The data resulted from simulation shows W1 is around $43\mu\text{M}$ to $46\mu\text{M}$. Next, I select $W1=43\mu\text{M}$ and $W1=46\mu\text{M}$ and run DC simulation and extract the g_m and g_{mb} . The results are as following:


$$W_1 = 40\ \mu\text{M} \Rightarrow g_m = 15.99\text{mS}, g_{mb} = 2.91\text{mS}, \Rightarrow R_{in} = \frac{1}{(15.99 + 2.91) \times 10^{-3}} = 52.91$$

$$W_1 = 43\ \mu\text{M} \Rightarrow g_m = 16.88\text{mS}, g_{mb} = 3.063\text{mS}, \Rightarrow R_{in} = \frac{1}{(16.88 + 3.063) \times 10^{-3}} = 50.14\ \Omega$$

Therefore the Width for M1 is $43\mu\text{M}$.

$$(b) \quad Q = \frac{R_p}{L\omega} = 4 \Rightarrow R_p = 4 \times 2\pi \times 5.2\text{GHz} \times L = L \times 130.7\text{G}\Omega$$

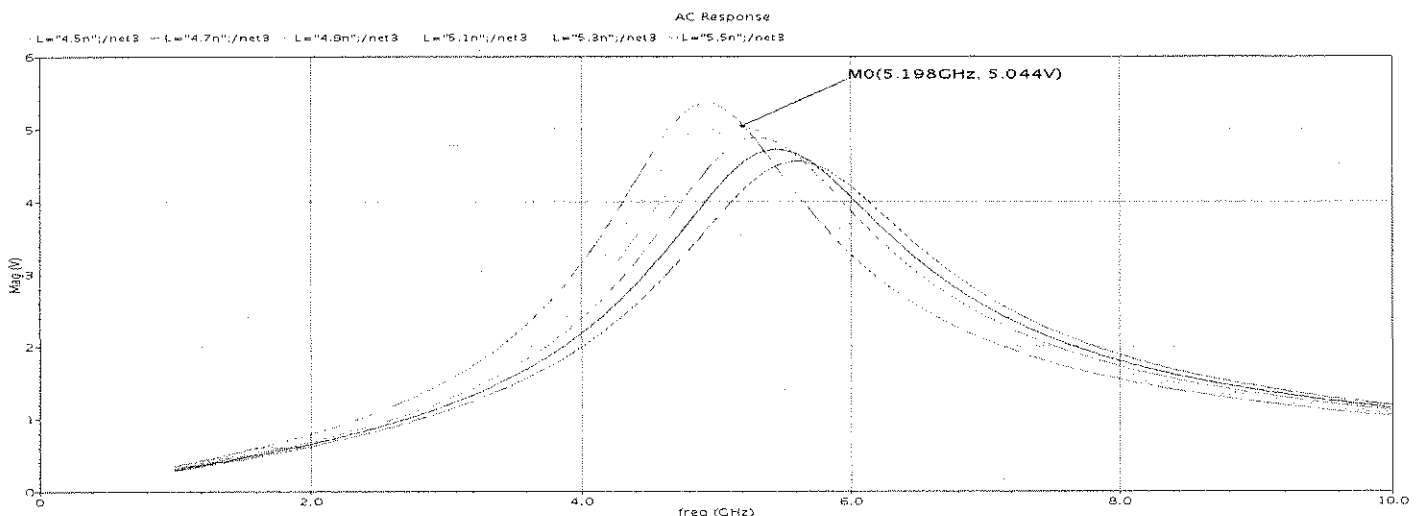
C_p is 10fF for each nanohenry of inductance so C_p is $10L\ \text{fF}$ for L nanohenry. Using the inductor model and running the AC simulation while sweeping the L value we found the family of plots as below:



As the plots show the resonance frequency at 5.2GHz happens for $L=5.1\text{nH}$.

(c)

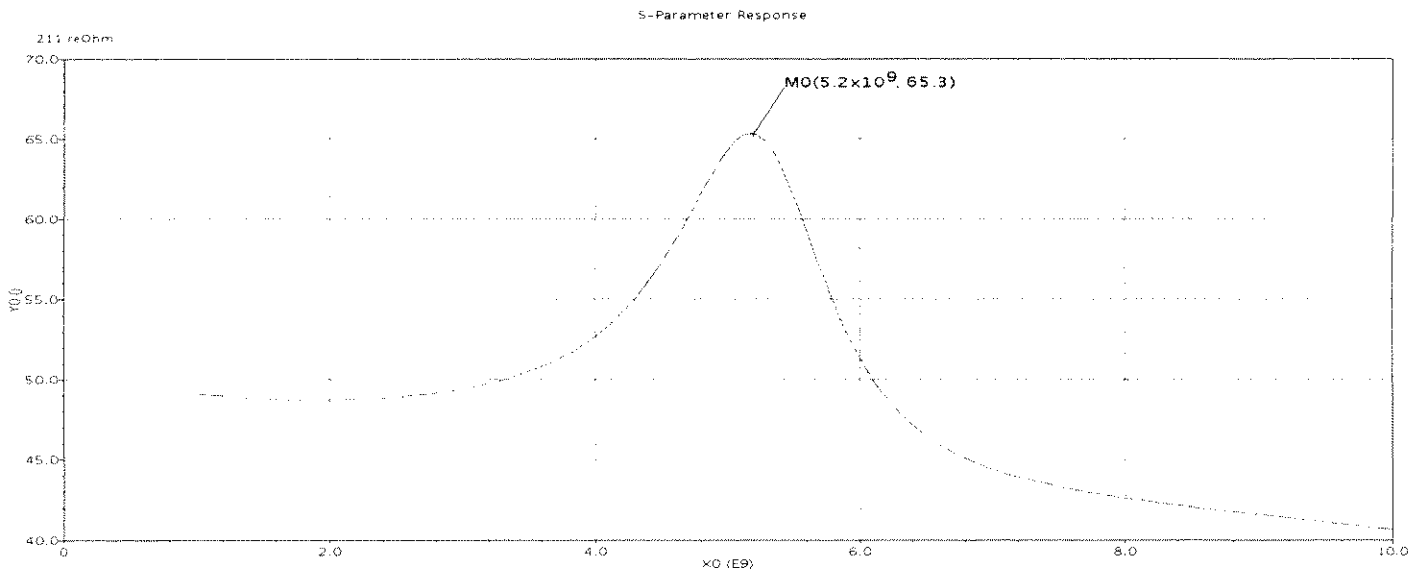For this part I used the S-parameter analysis on cadence and Plot the real part of input impedance while sweeping the frequency from 1kHz to 100MHz. The following graph shows the result. At DC (i.e. the low frequency) the resistance is 50 ohms as expected. At resonant frequency $f=5.2\text{GHz}$ the resistance equals to 65.3 ohms.




The reason for this is that as we use the non-ideal inductor model there exists an internal resistance for inductor. At low frequency this resistance gets shorted by inductor but at resonance frequency this appears as a pure resistance at Drain of M1 and therefore the input resistance increases.

$$R_{in} = \frac{1 + \frac{R_D}{r_o}}{\frac{1}{r_o} + g_m + g_{mb}}$$

At DC R_D is zero and Input resistance is $(g_m + g_{mb})^{-1}$ but at resonance frequency R_D is not zero

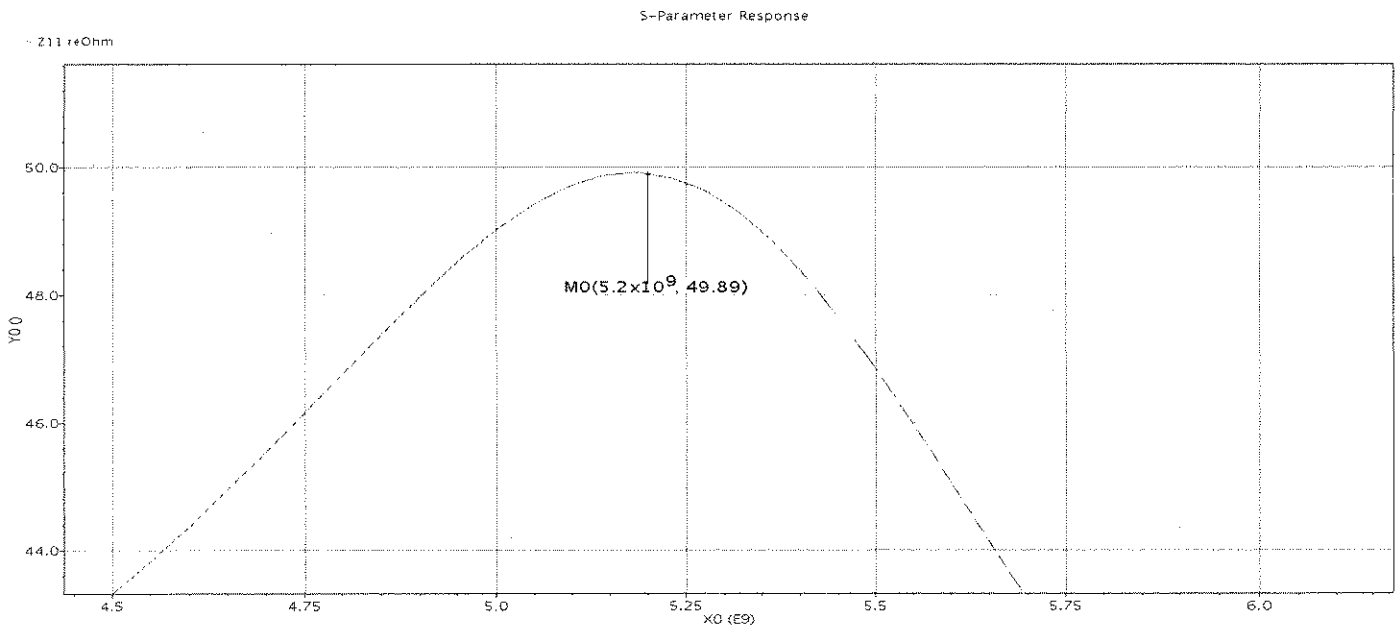and therefore input resistance is higher. Adjusting the Width of M1 to get the input resistance as 50 ohms results that resonance frequency change too, therefore by adjusting the width to $W1=65\ \mu\text{M}$ we need to adjust the L to 4.1nH so that we get resonance frequency equal to 5.2 GHz and resistance of 50 ohms. The results are shown below:





(d)

Using PSS analysis and applying two tones at 5.19GHz and 5.2GHz with $P_{in} = -30dBm$, I plot the output Power in dBm and calculate the differenc between them, and find IIP3 in dbm from shortcut method. I also used the IPN curve method of input power extrapolation and find the same result. The plots are shown below:

$$\Delta P|_{dB} = (-123.5dBm) - (-192dBm) = 68.5dB \Rightarrow \Delta P|_{dB} / 2 = 34.25$$

$$IIP3|_{dBm} = \frac{\Delta P|_{dB}}{2} + P_{in}|_{dBm} = 34.25 - 30 = 4.25dBm$$

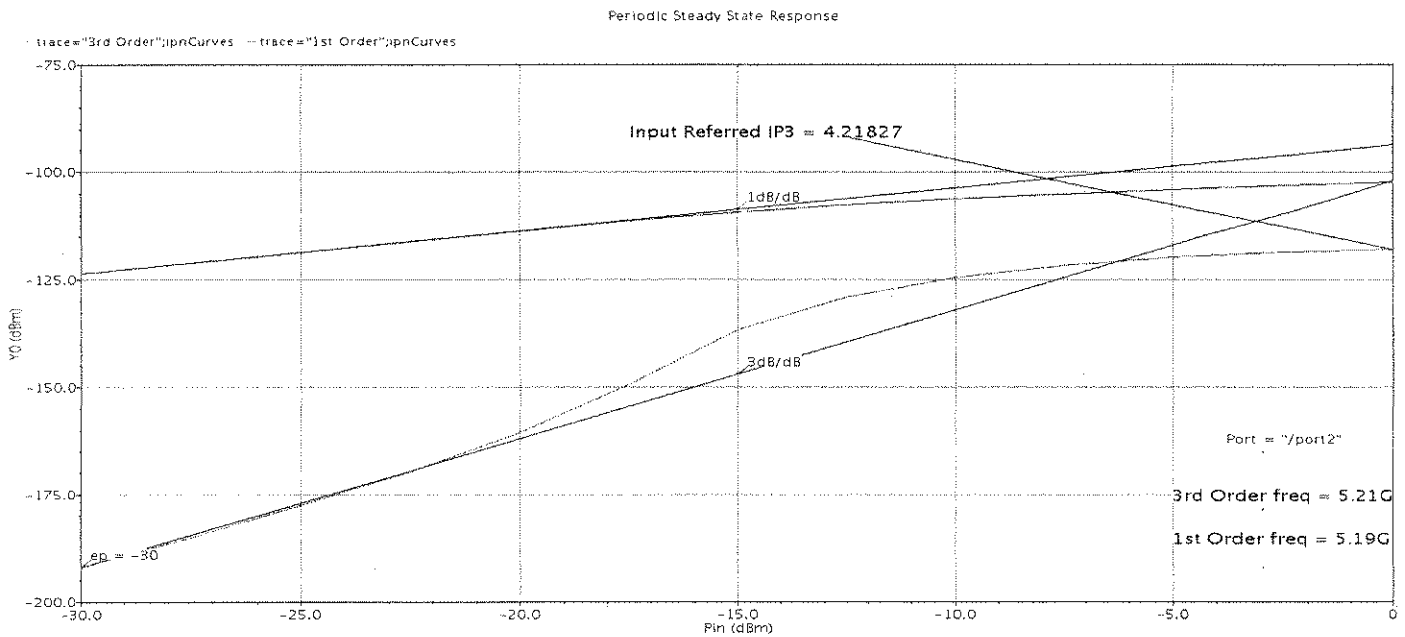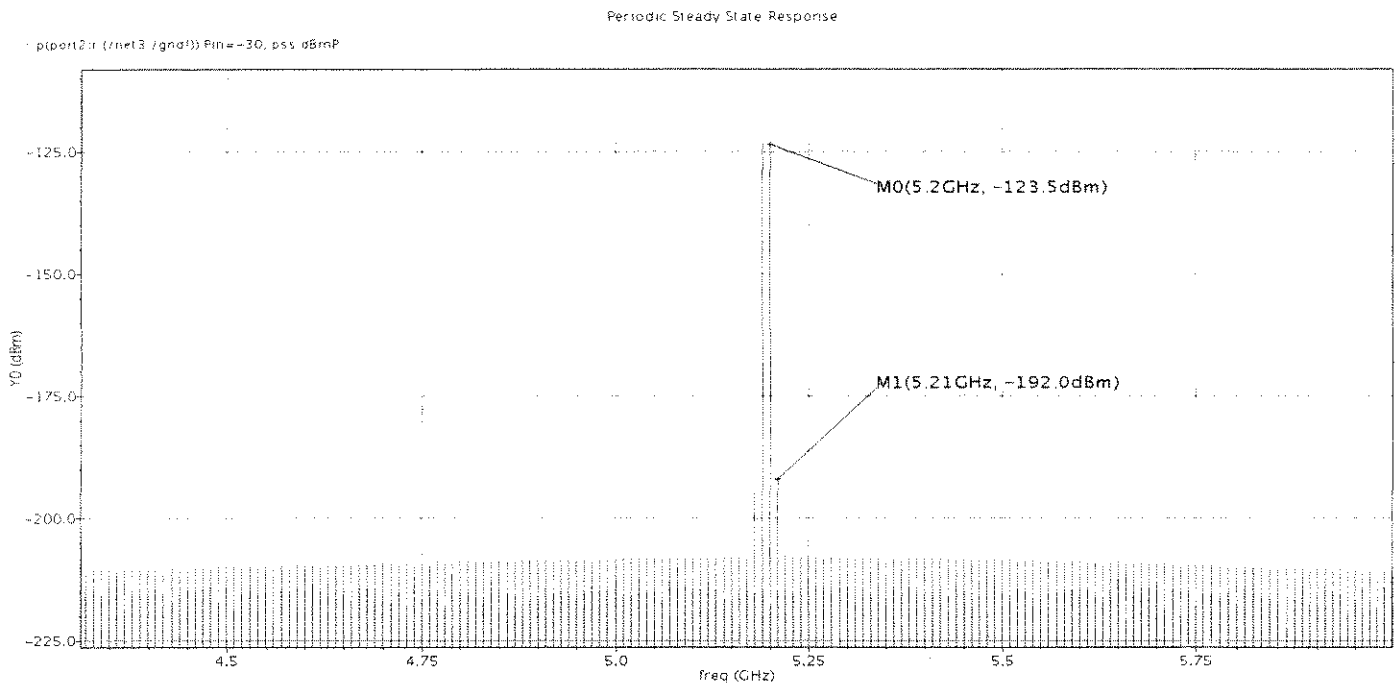


IIP3 = 4.25dBm.


The Voltage gain from AC simulation at 5.2GHz equals to 19.36dB = 9.3

(e)

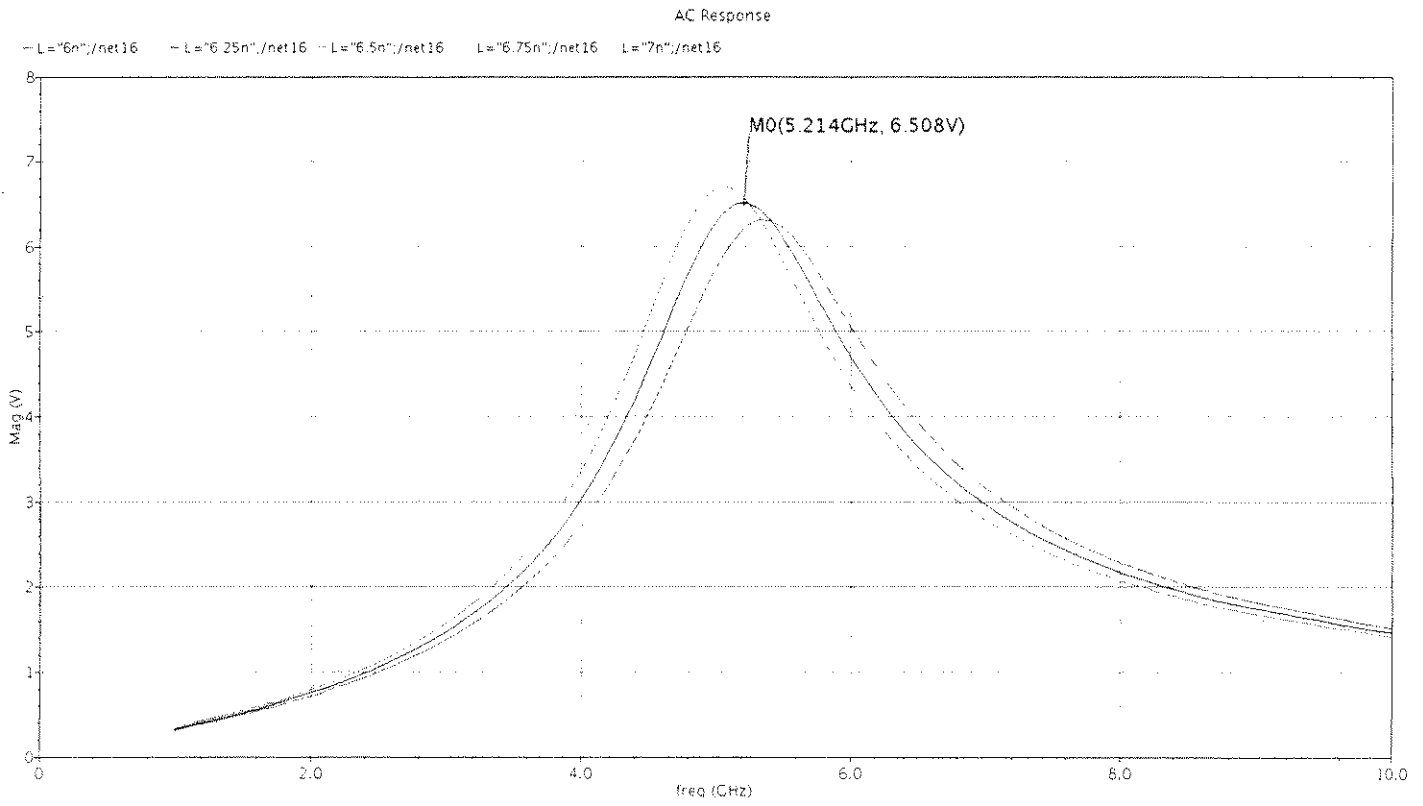Following the same method as part b at first iteration I found that L2 is between 6nH and 7nH, by second simulation and sweeping L2 from 6nH to 7nH we found L2=6.25nH



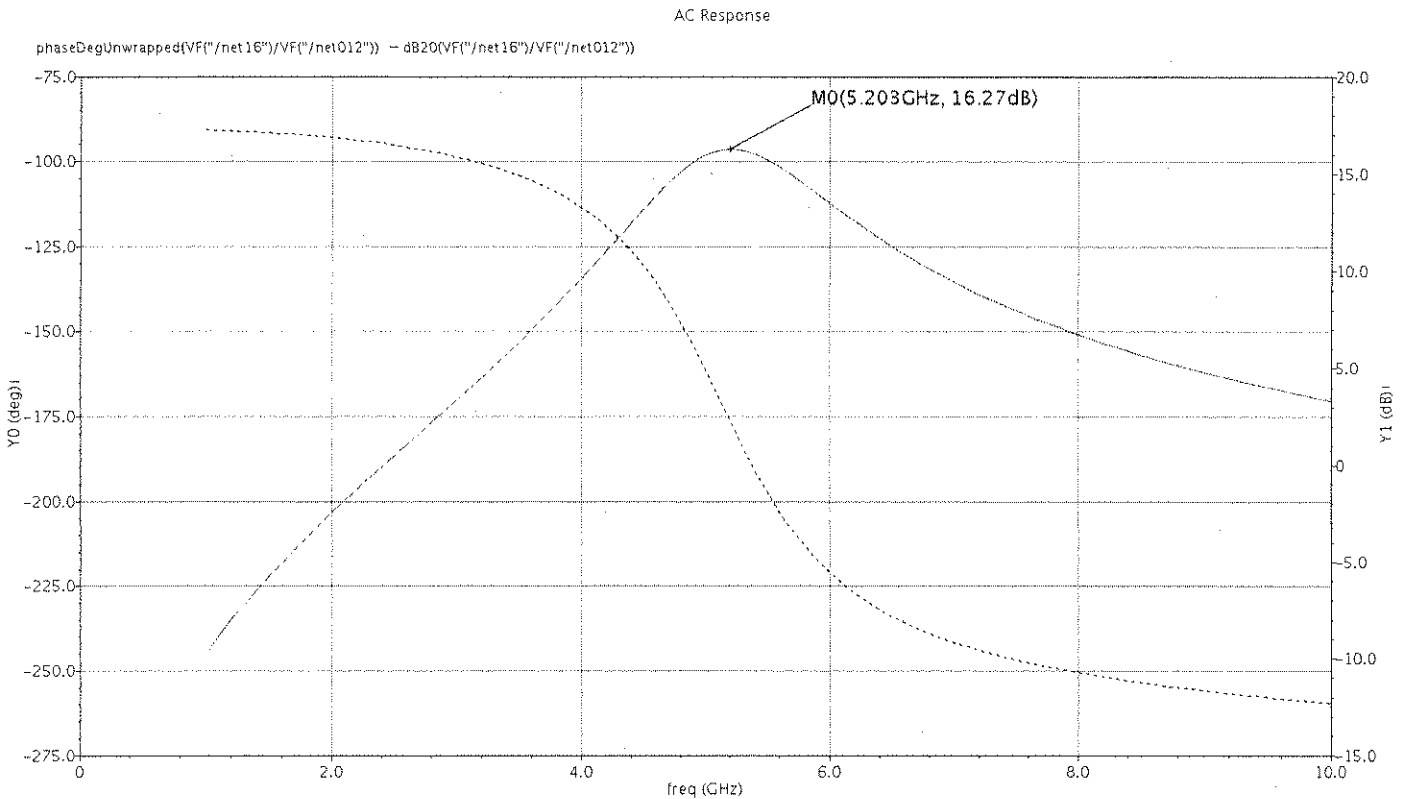
The voltage gain from AC simulation was found as: 16.27dB




Using same method for calculating IIP3 I found the following results:

$$\Delta P|_{dB} = (-121.2dBm) - (-165.6dBm) = 44.4dB \Rightarrow \Delta P|_{dB} / 2 = 22.2dB$$

$$IIP3|_{dBm} = \frac{\Delta P|_{dB}}{2} + P_{in}|_{dBm} = 22.2 - 20 = 2.2dBm$$

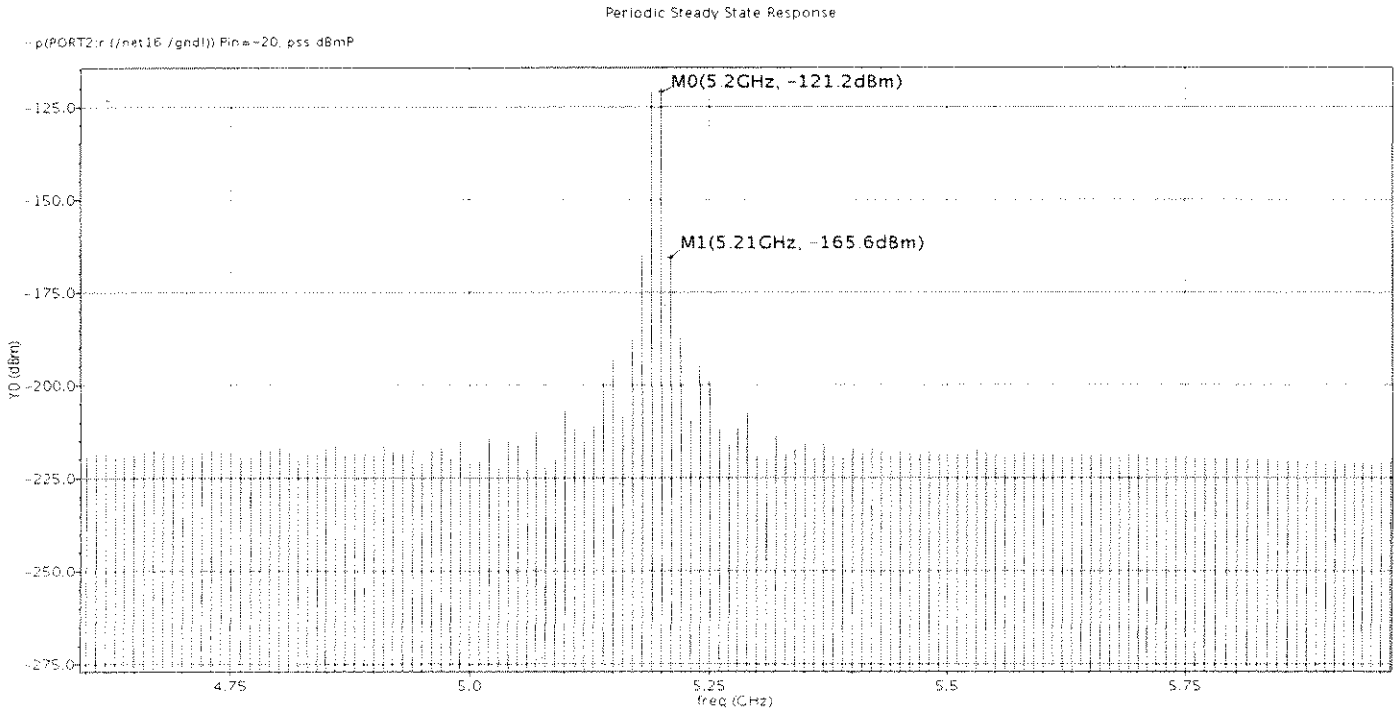

Periodic Steady State Response

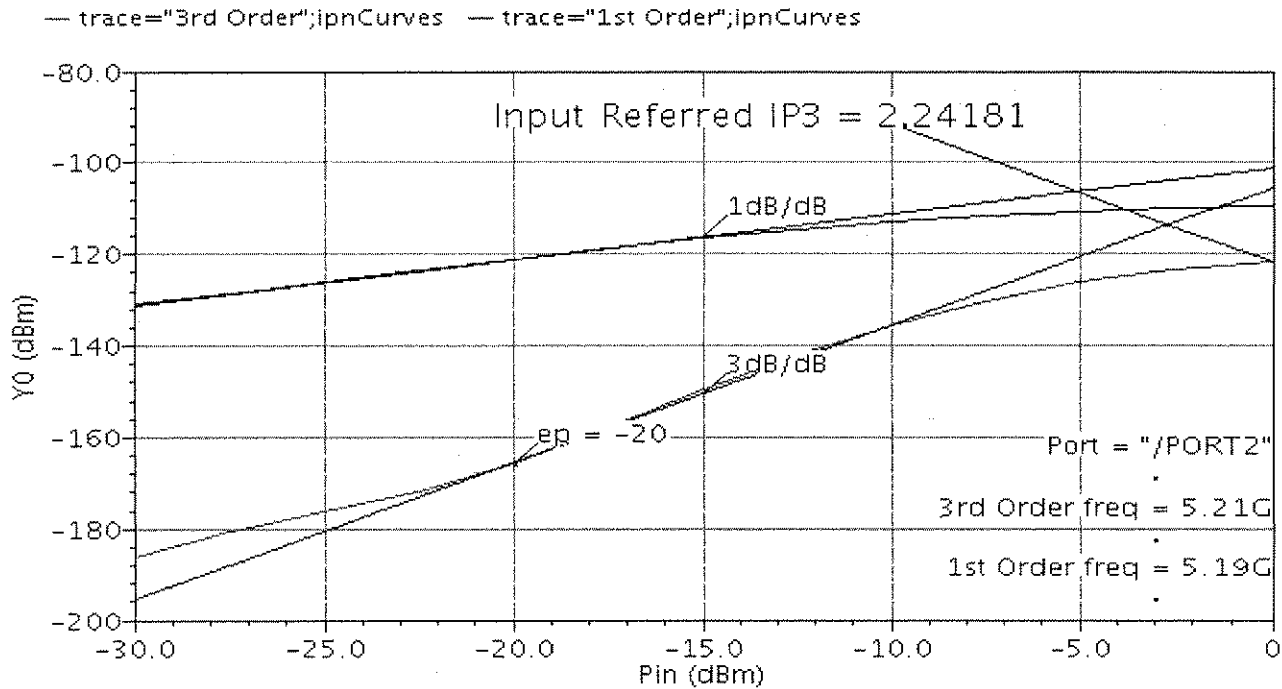

IIP3 = 2.2 dBm


(f)

By placing the second amplifier as the load of the first amplifier the resonance frequency changes to 4.6GHz which is a result of change in the load of the first amplifier As a result a I changed the value of L1 to have the resonance frequency equal to 5.2GHz while kept all other parameters (i.e. W1, L2) fixed.


$$\Delta P|_{dB} = (-120dBm) - (-142.5) = 22.5dB \Rightarrow \Delta P|_{dB} / 2 = 11.25$$

$$IIP3|_{dBm} = \frac{\Delta P|_{dB}}{2} + P_{in}|_{dBm} = 11.25 - 25 = -13.75dBm$$

Periodic Steady State Response

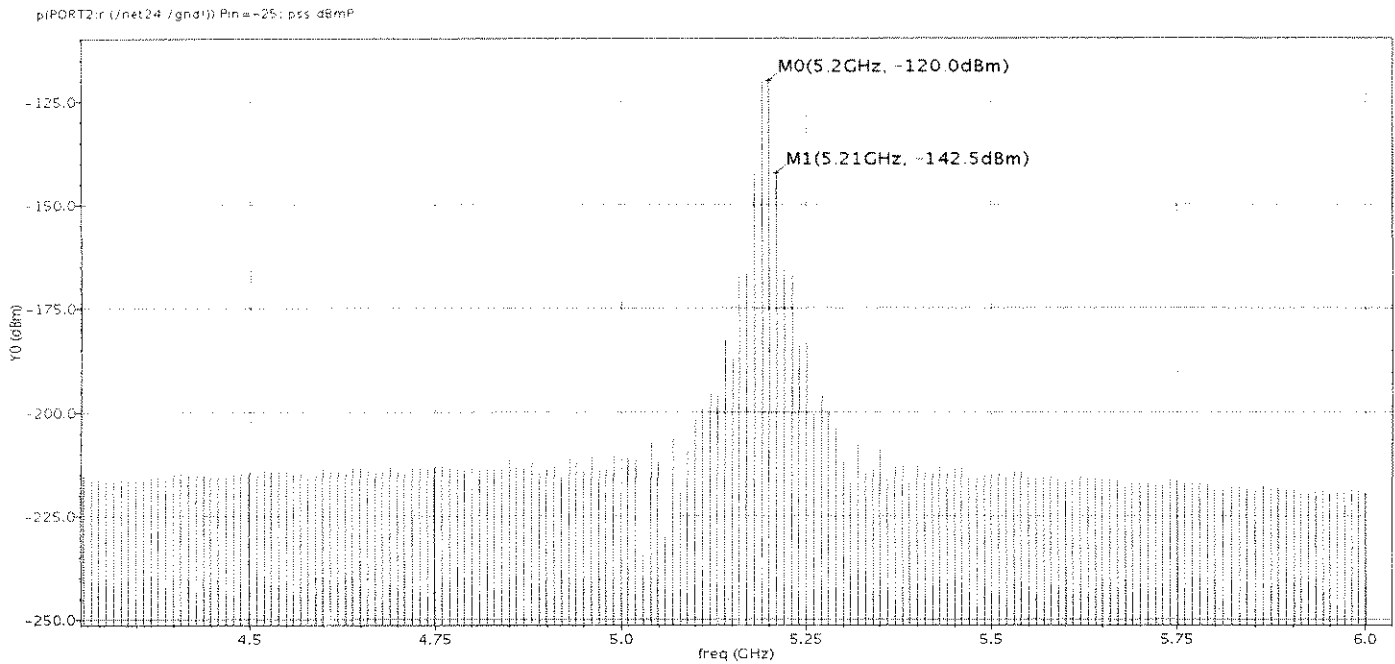


Periodic Steady State Response

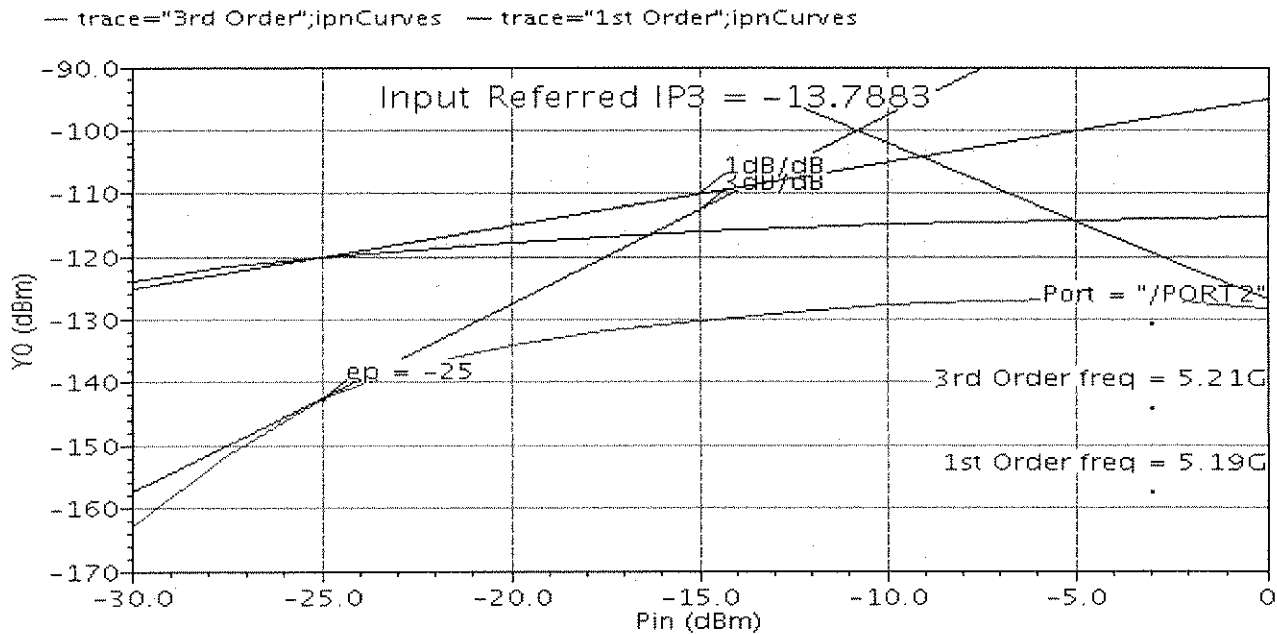

IIP3 = -13.78 dBm

AC Response

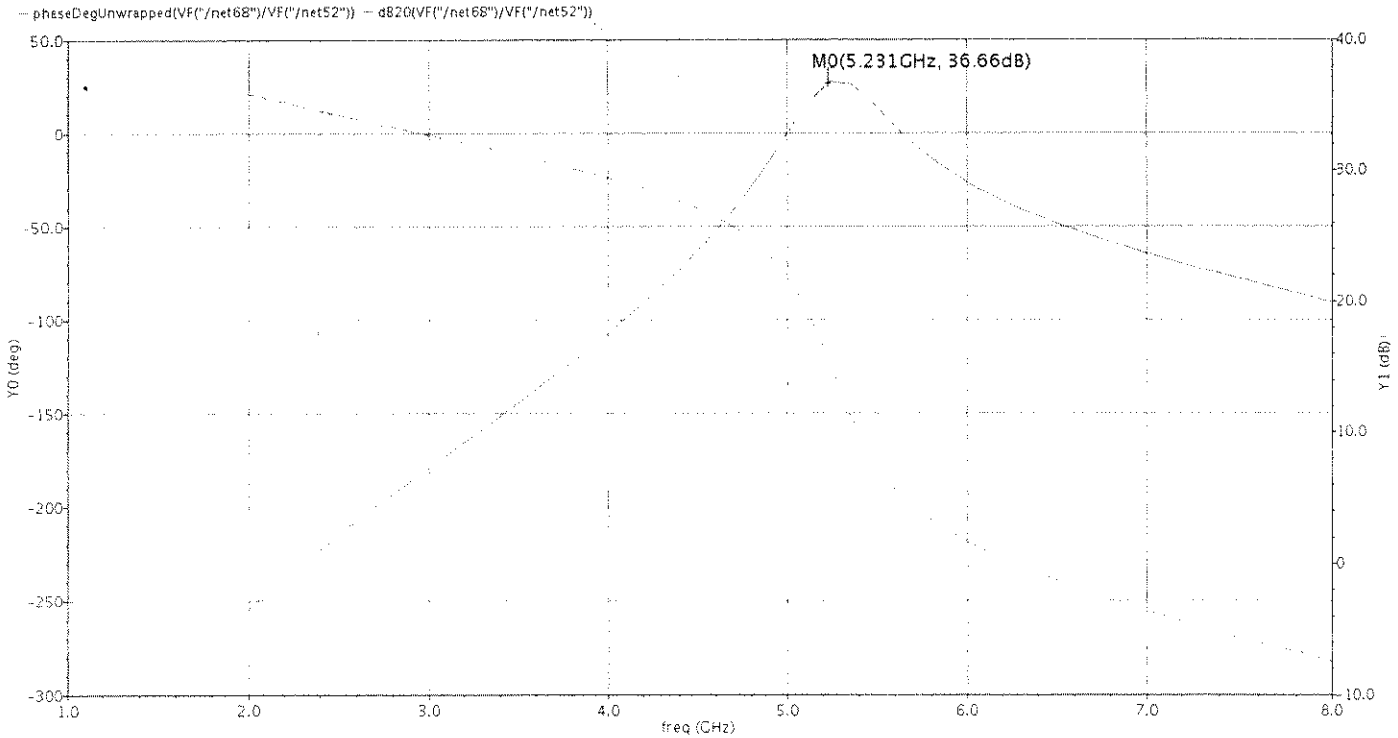

And the overall Voltage gain is: 36.66 dB which matches to the gain of stage 1 in dB + gain of stage 2 in dB.

In order to use equation (2.46) we have to change the dBm and dB values of IIP3's and Voltage gain to real numbers.

$$\Rightarrow 4.25 \text{ dBm} \Rightarrow A_{IP_{3-1}} = (632 \text{ mV}) \times 10^{\frac{4.25}{20}} = 1030.9 \text{ mV}$$

$$IIP_{3-2} = 2.2 \text{ dBm} \Rightarrow A_{IP_{3-2}} = (632 \text{ mV}) \times 10^{\frac{2.2}{20}} = 814.2 \text{ mV}$$

$$\alpha = 19.36 \text{ dB} = 10^{\frac{19.36}{20}} = 9.3$$


$$\frac{1}{A_{IP_3}^2} = \frac{1}{A_{IP_{3-1}}^2} + \frac{\alpha^2}{A_{IP_{3-2}}^2} = \frac{1}{(1.0309 \text{ V})^2} + \frac{(9.3)^2}{(0.8142 \text{ V})^2} \Rightarrow A_{IP_3} = 87.24 \text{ mV}$$

$$\Rightarrow IIP_3 = 20 \times \log\left(\frac{87.24 \text{ mV}}{632 \text{ mV}}\right) = -17.20 \text{ dBm}$$

The result from the simulation and calculation are close but they don't match exactly, the reason could be a result of neglecting the effect of IM2 of the first amplifier which will increase the IM3 at the output of the second stage and also changing the value of L each times we want to match the resonant frequency to 5.2GHz. Nevertheless, the amount of error is not huge and this shows the simulation was successful.

(g)

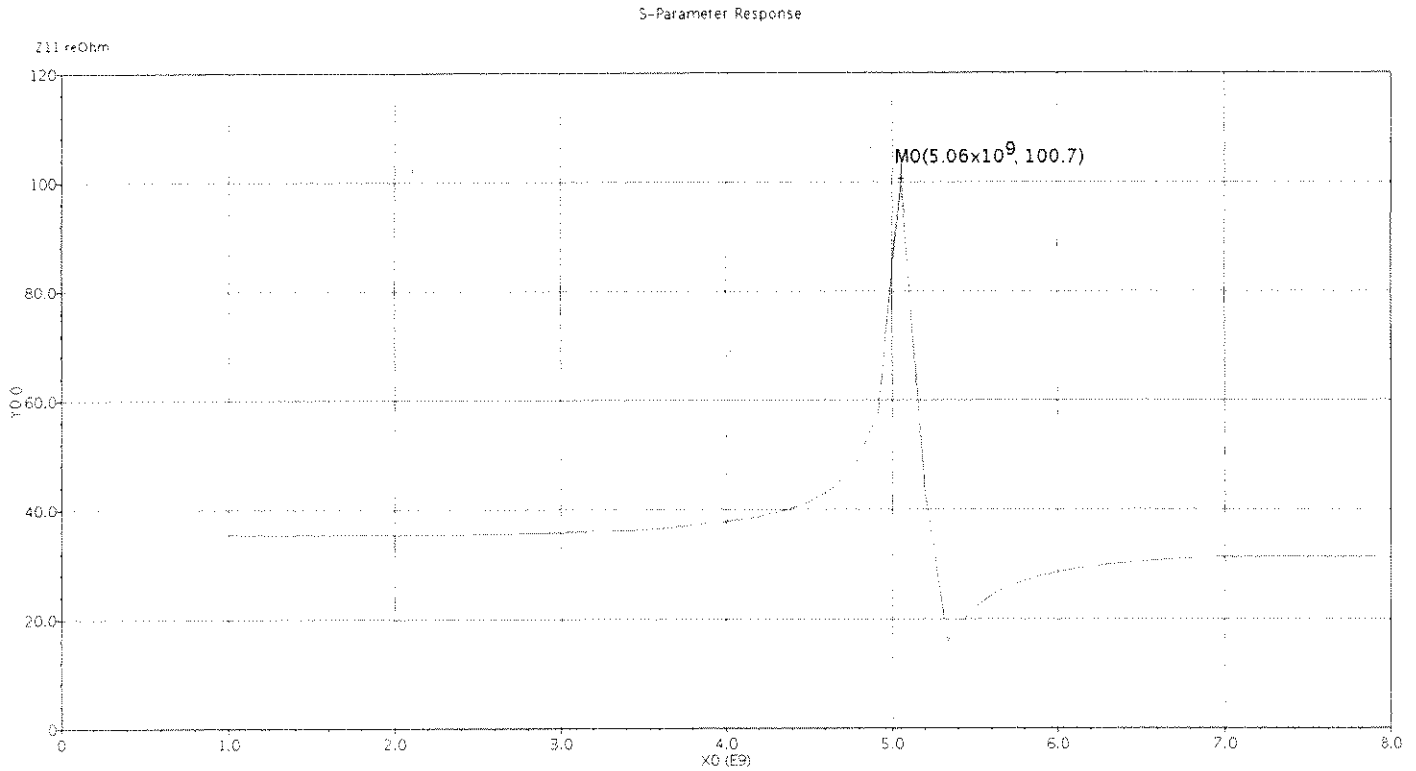From the plot below, it can be seen that the input resistance changes by a significant amount. It is now almost 100 ohms. This is because there is now a much larger load on the first stage, thus affecting the input impedance. Also, the adjustments in the inductor model to achieve resonance at 5.2GHz will have some effect on the input impedance.



(h)

The second stage limits the IIP3 because of the large gain in the first stage.

1)

x) Using eq (4.28): $NF = \frac{\overline{V_{n,out}^2}}{A^2} \cdot \frac{1}{4kTR_S}$

$$NF_1 = \frac{\overline{V_{n,amp}^2} + 4kTR_S A^2}{A^2} \times \frac{1}{4kTR_S} \Rightarrow \overline{V_{n,amp}^2} = (NF_1 - 1) \times 4kTR_S A^2$$

$$\rightarrow NF_{tot} = \frac{\overline{V_{n,amp}^2} + 4kT(R_S \parallel R_P) A^2}{\left(\frac{1}{2}A\right)^2} \times \frac{1}{4kTR_S} = \frac{(NF_1 - 1)4kTR_S A^2 + 4kT \frac{R_S}{2} A^2}{\left(\frac{1}{2}A\right)^2} \times \frac{1}{4kTR_S} = 4NF_1 - 4 + 2$$

$$\Rightarrow NF_{tot} = 4NF_1 - 2$$

b) Here the first stage is a loss stage with the gain of $\frac{1}{2}$.

Fri's equation: $NF_{tot} = 1 + (NF_1 - 1) + \frac{NF_2 - 1}{A_{P_1}}$

$$\Rightarrow NF_{tot} = 1 + (2 - 1) + \frac{NF_1 - 1}{\left(\frac{1}{2}\right)^2} = 4NF_1 - 4 + 2 = 4NF_1 - 2$$