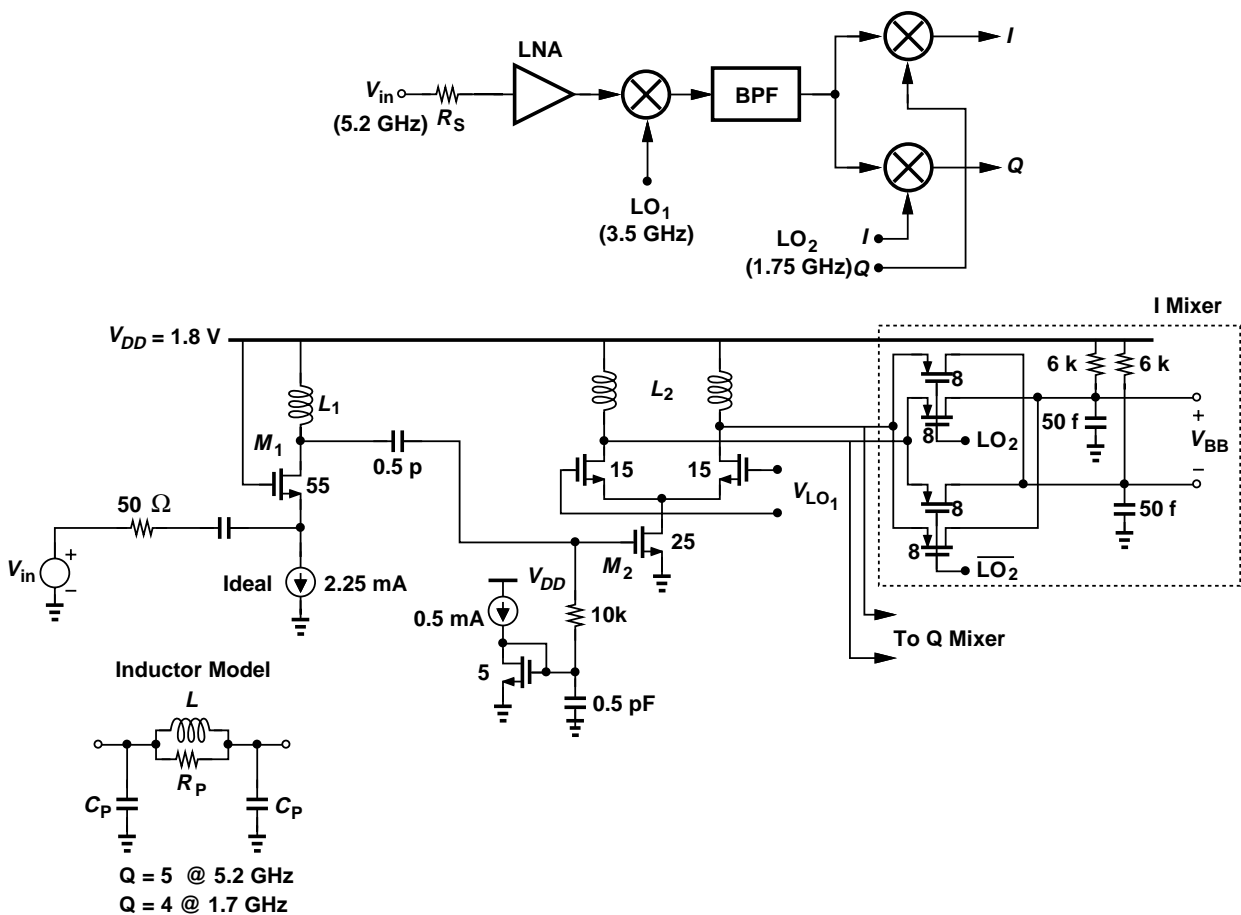


## Homework #4

Due Wed., Feb. 10, 2010

In this homework, we use SPICE or Cadence to study a single-VCO heterodyne receiver. The architecture and circuit implementation are shown below. The IF mixers are realized as passive switches. For simplicity, the divide-by-two stage that would generate  $LO_2$  from  $LO_1$  is omitted from this homework. All transistors have a channel length of  $0.18 \mu\text{m}$ . For  $LO_1$ , assume a frequency of 3.5 GHz, a common-mode level of 1.6 V, and a peak-to-peak differential amplitude of 0.75 V. For  $LO_2$ , these numbers will be 1.75 GHz, 0.9 V, and 3.6 V, respectively. The inductors must be modeled as shown, where  $C_P = 8 \text{ fF}$  for every nanohenry of inductance.



- Determine the values of  $L_1$  and  $L_2$  to obtain resonance at 5.2 GHz and 1.7 GHz at the LNA output and RF mixer output, respectively.
- Compute the total voltage gain of the receiver, with the input level defined as  $V_{in}/2$ .
- Determine the image-reject ratio of the receiver.
- Identify two mechanisms through which the receiver translates an interferer at 8.7 GHz to baseband. Assume no mismatches or even-order harmonics. Determine the gain experienced by such a component and normalize the result to the gain found in (a).