

Basic Concepts in Oscillator Design


Behzad Razavi

**Electrical Engineering Department
University of California, Los Angeles**


Outline

- Small–Signal View**
- Ring and LC Oscillators**
- One–Port View**
- Quadrature Oscillators**
- Frequency Tuning**



Small-Signal View

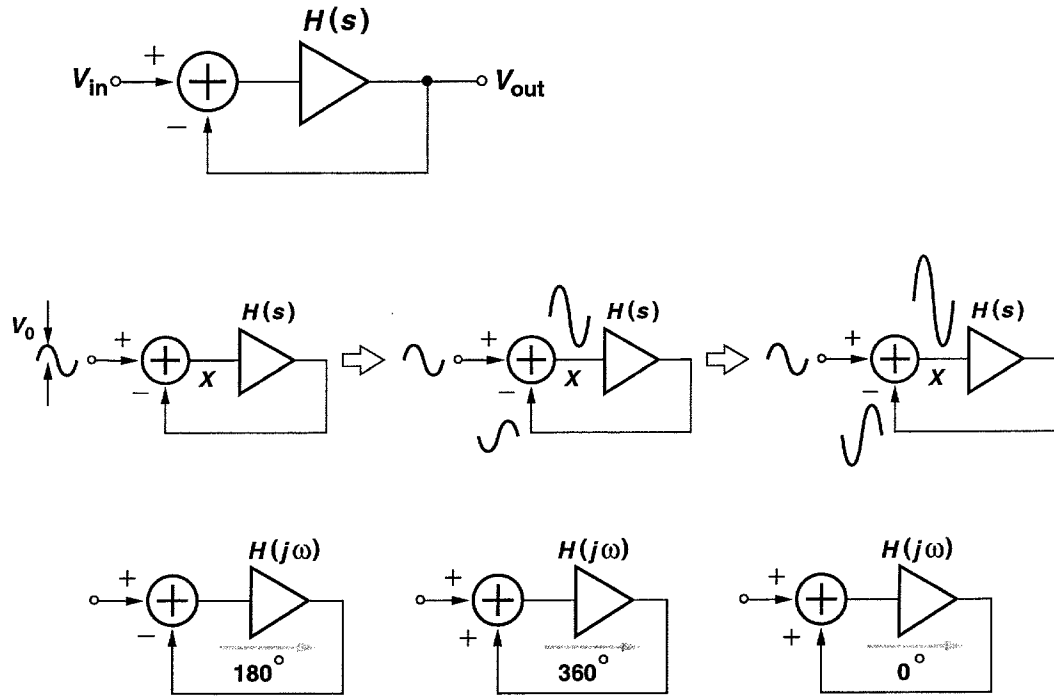

Ring Oscillators (I)

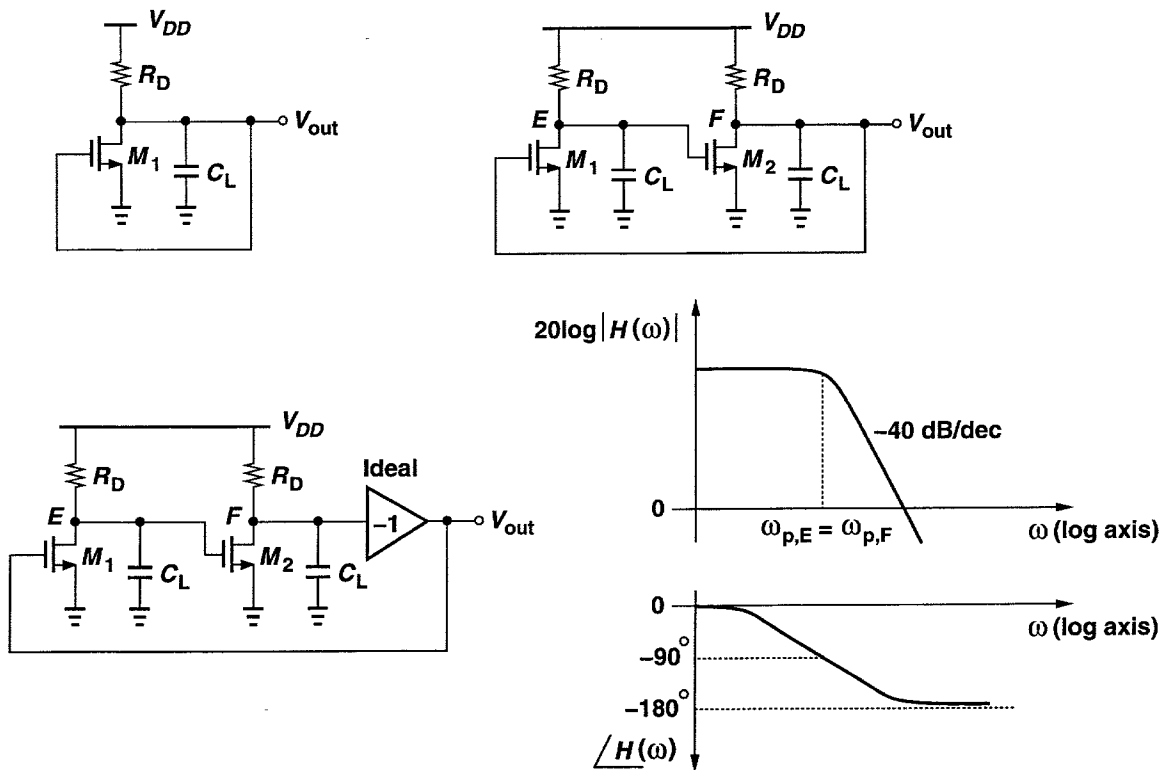


Ring Oscillators (II)

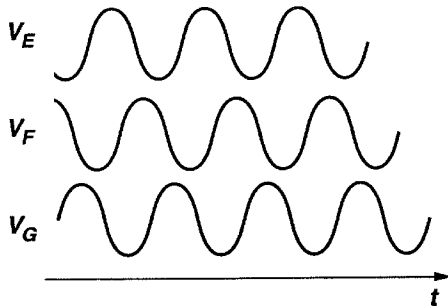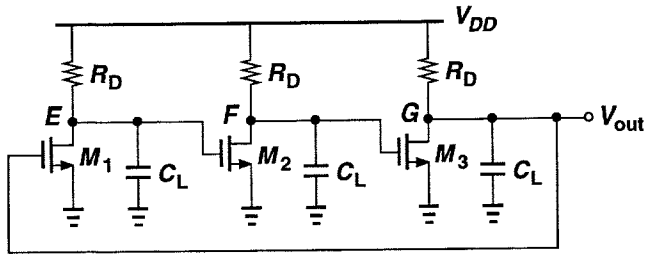


LC Oscillators

- Much lower phase noise than ring and relaxation oscillators (for given power and frequency)
- Much narrower tuning range
- Need high-Q inductors and varactors.
- Control input is usually single-ended.
- Voltage swings may exceed the supply voltage; good because relative phase noise decreases, bad because device reliability suffers.



Basic LC Concepts

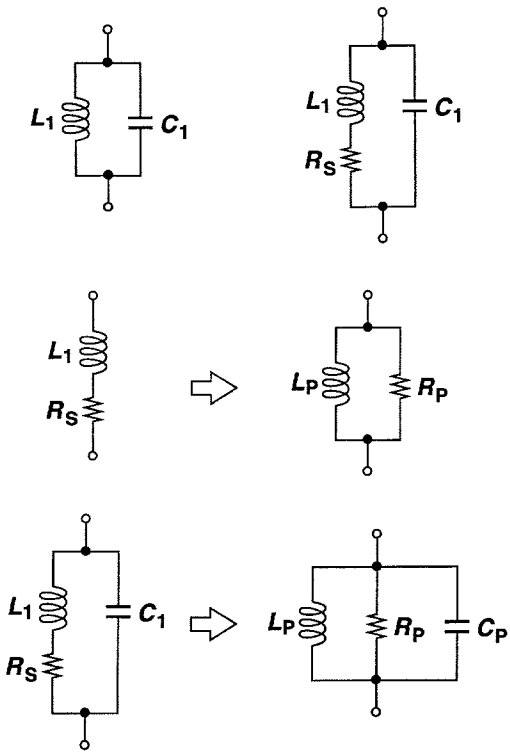



Basic Tuned Stage

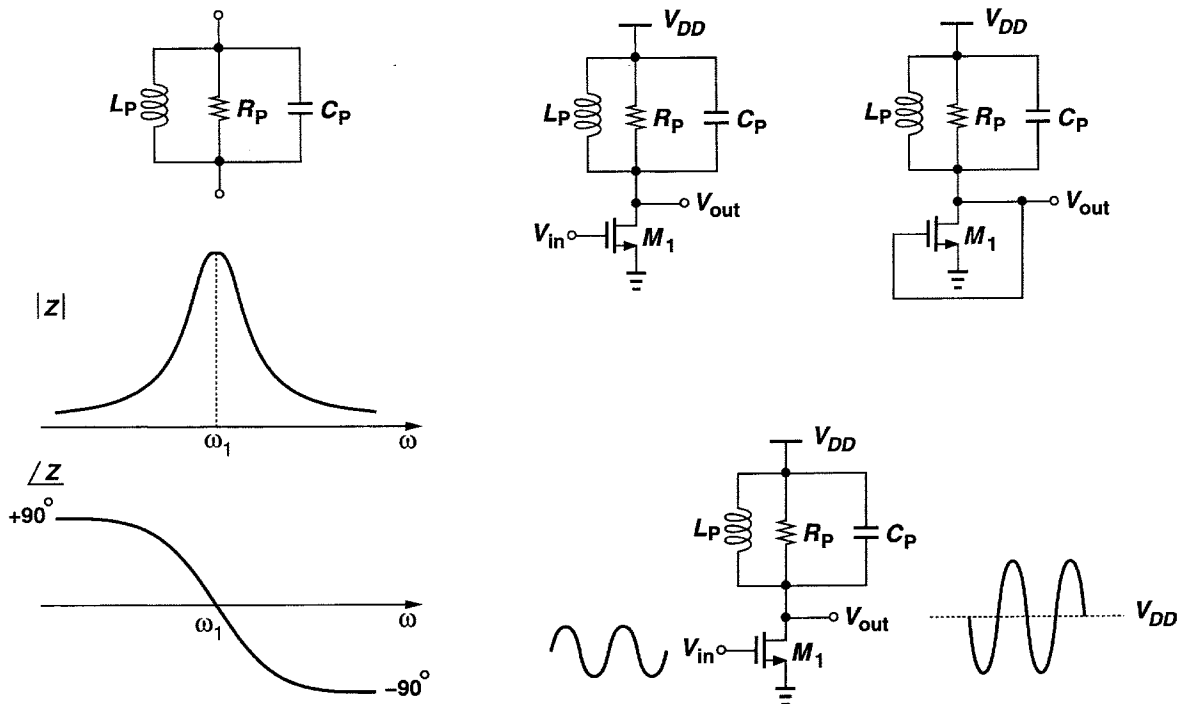


Cross-Coupled LC Oscillator

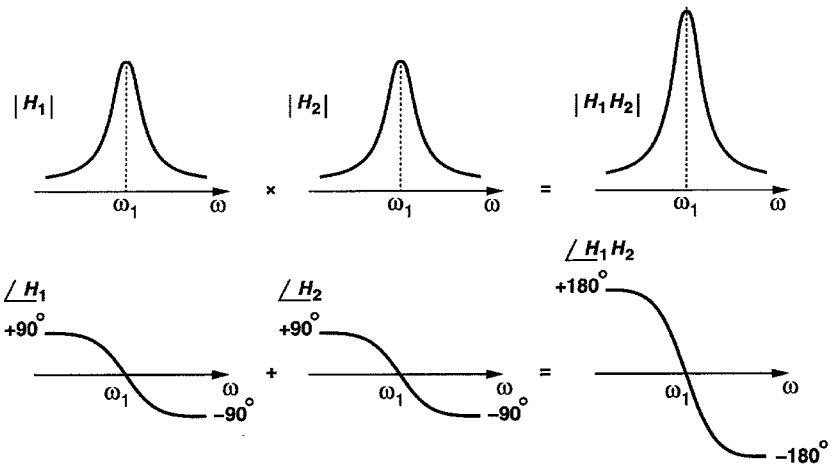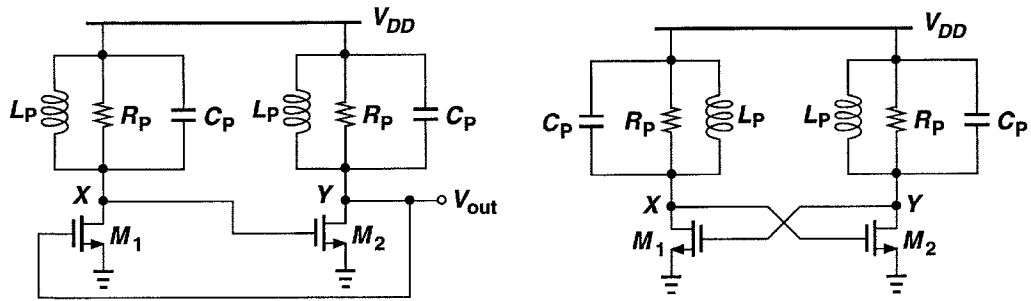


Cross-Coupled LC Oscillator

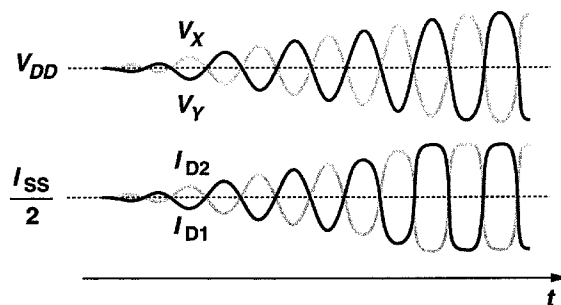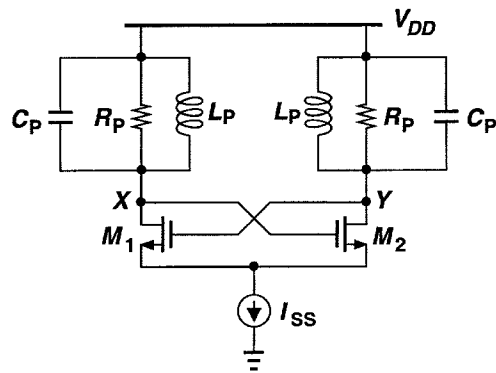







One-Port Oscillators

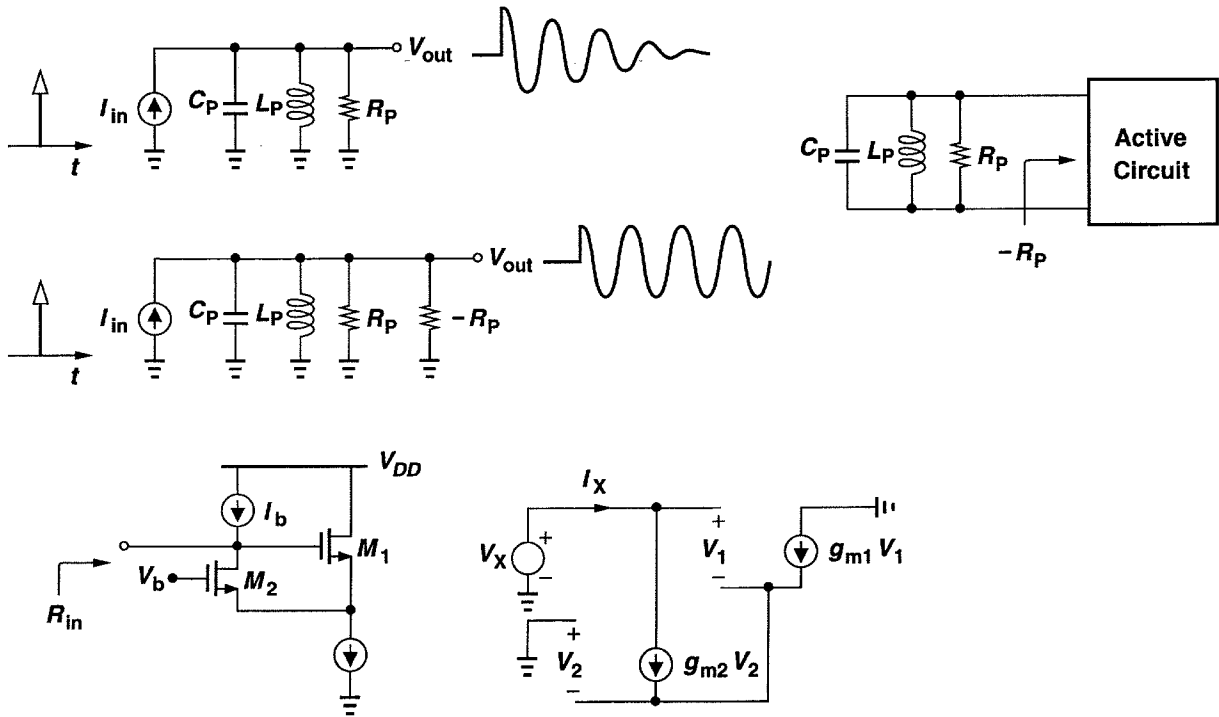

Negative-Gm Oscillator

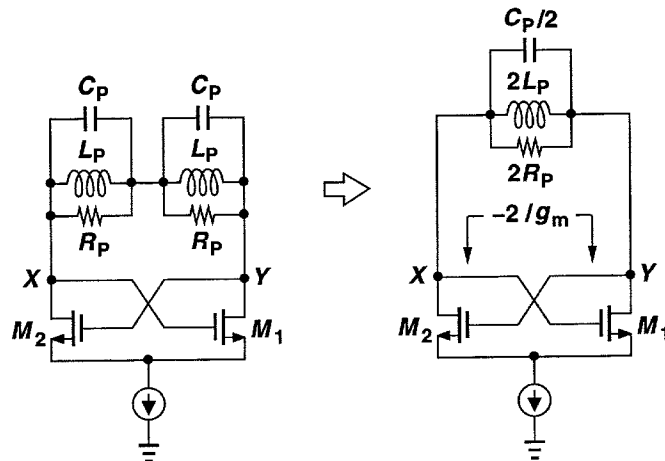


"Three-Point" Oscillator

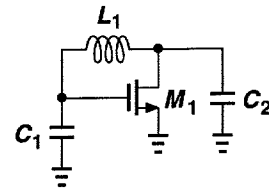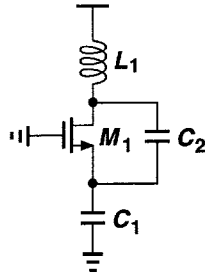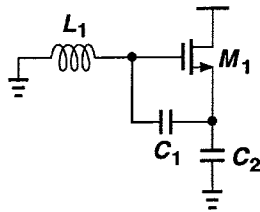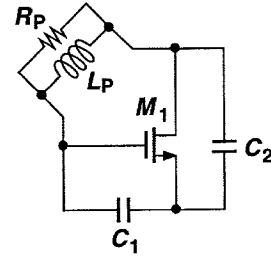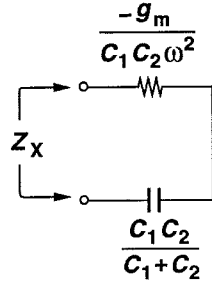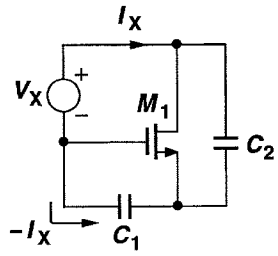

Quadrature Signal Generation


- RC-CR Network
- Polyphase Network
- Divide-by-Two Circuit
- LO with Quadrature Outputs

RC-CR Network

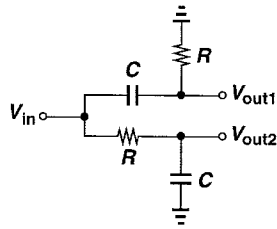

- Absolute tolerance causes gain mismatch.
- Device mismatch causes phase imbalance.
- Requires sinusoidal input.
- Sensitive to load capacitance


Quadrature Oscillators

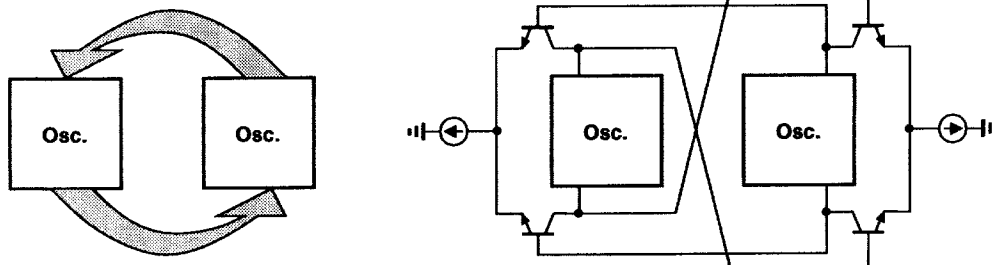



(Verhoeven, JSSC, July'92)
(Rofougaran et al, ISSCC'96)

- Inherently quadrature outputs
- Somewhat higher power dissipation
- Q's add but more devices contribute noise.





Quadrature Oscillators

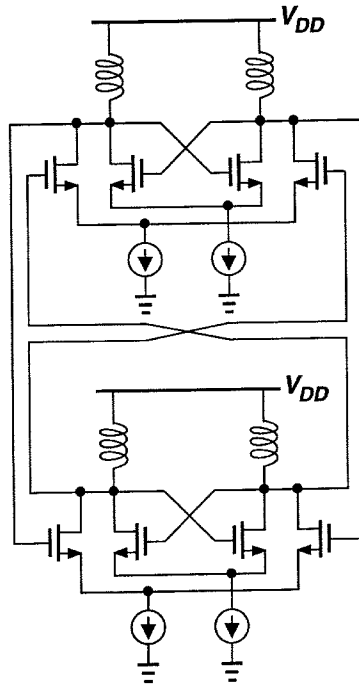

Quadrature Oscillator

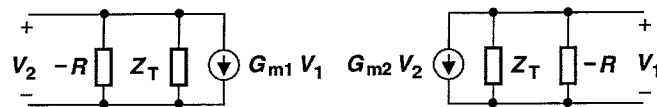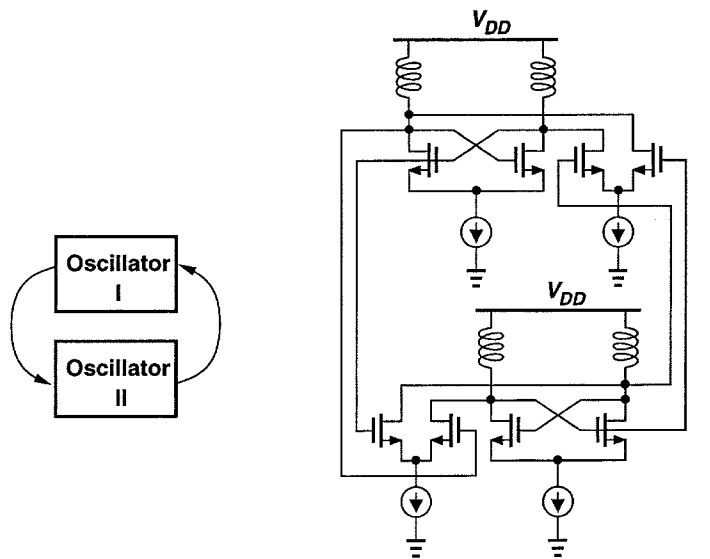


Quadrature Oscillator

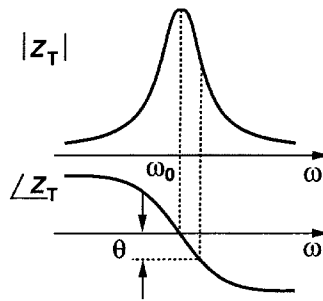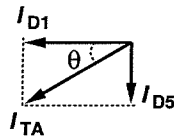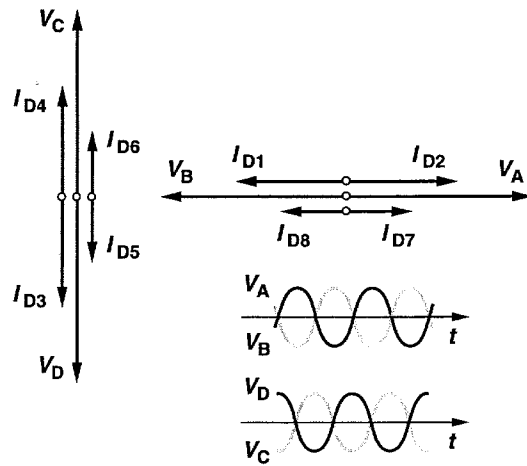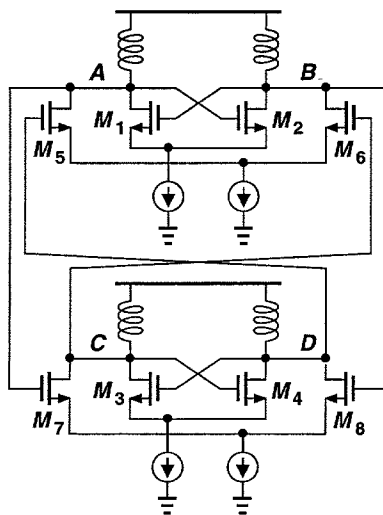

VCO Design Issues


- Center Frequency
- Tuning Range
- Phase Noise
- Tuning Linearity
- Output Amplitude
- Power Dissipation
- Supply and CM Rejection

Oscillator Type I

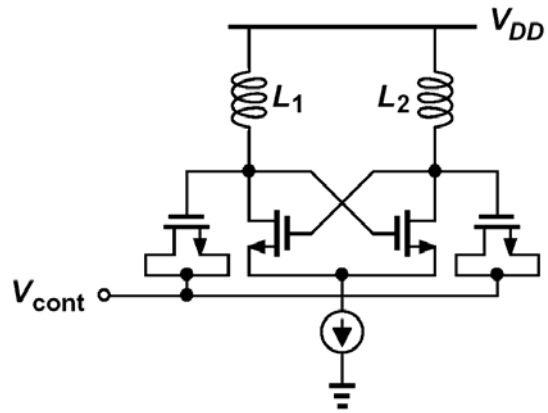


54

Oscillator Type II

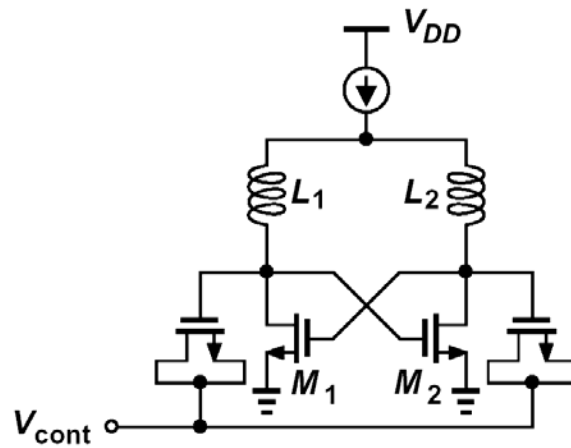



55

Oscillator Type III

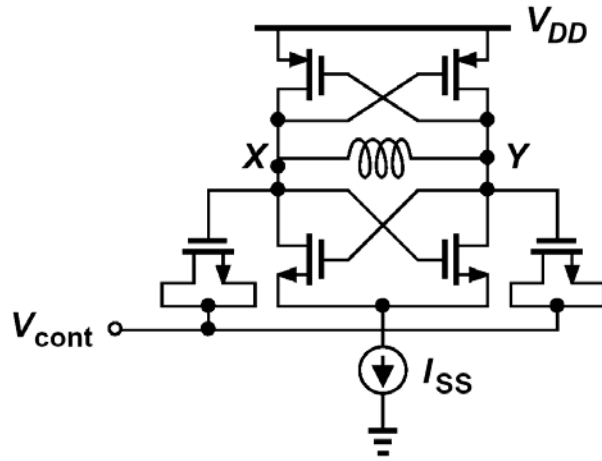


56

Oscillator Type IV

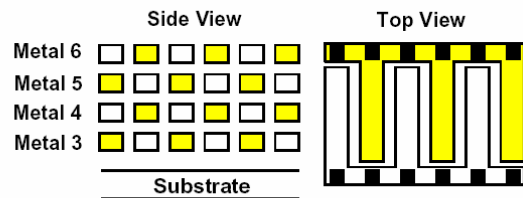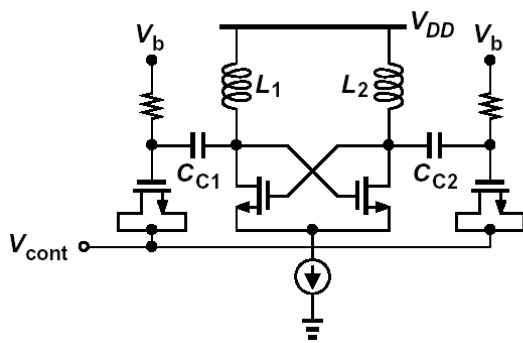


57

Tuning Range Limitations

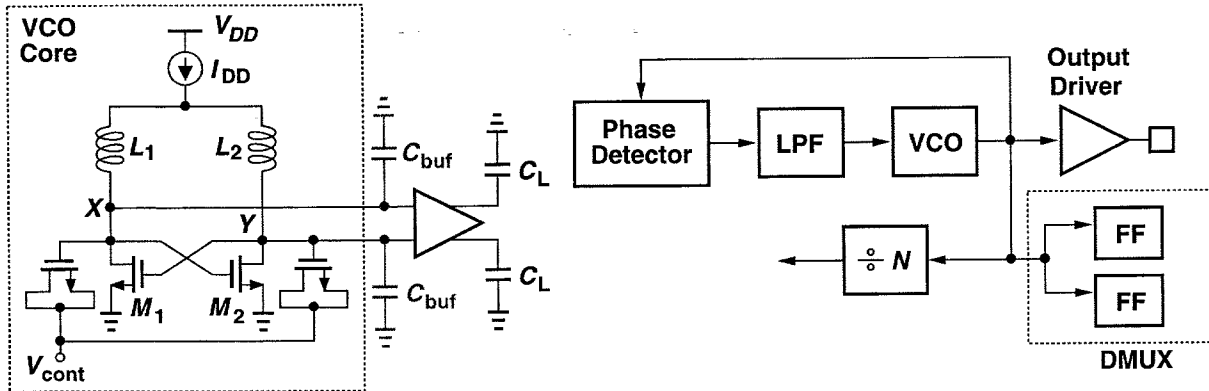

- Charge pump output voltage range
- Capacitance of cross-coupled pair
- Capacitance of inductors
- Constant component of varactors
- Buffer input capacitance

VCO Design Procedure

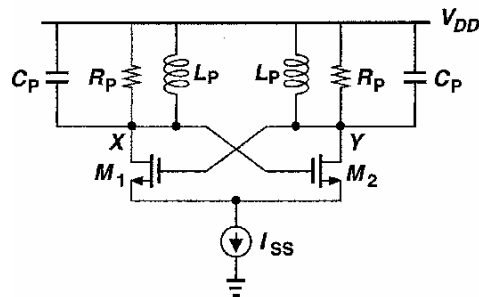

- Begin with (1) power budget, (2) output swing, (3) load capacitance.
→ Required tail current and R_p known.
- Find the smallest inductance that provides R_p .
- Determine transistor width for nearly complete switching with given swing.
- Determine varactor capacitance.
- Check resulting tuning range. → Iterate.